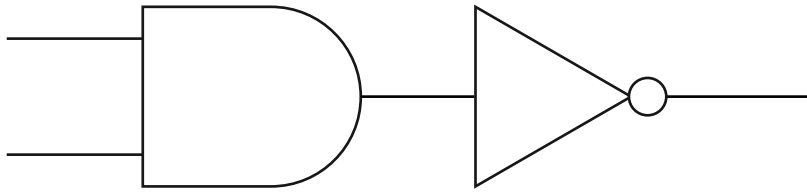


# QUESTION 6.

6




4 (a) (i) Complete the truth table for this logic circuit:



A	B	Working space	X
0	0		
0	1		
1	0		
1	1		

[1]

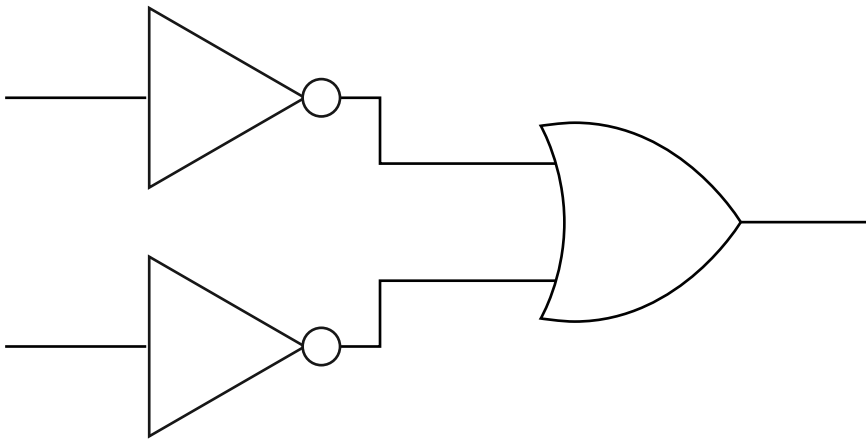(ii) Complete the truth table for this logic circuit:



A	B	Working space	X
0	0		
0	1		
1	0		
1	1		


[1]


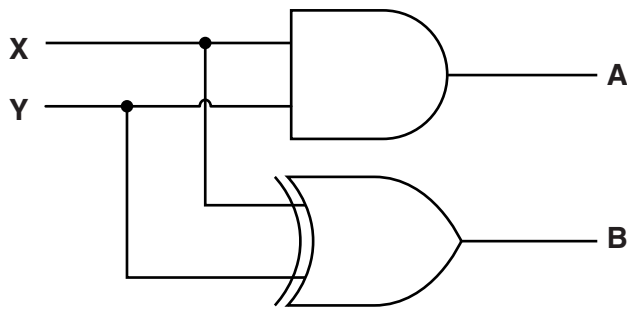
# QUESTION 7.



4 (a) (i) Complete the truth table for this logic circuit.



Input		Output	
X	Y	A	B
0	0		
0	1		
1	0		
1	1		

[2]

(ii) State the name given to this logic circuit.

..... [1]

(iii) Name the labels usually given to **A** and **B**.

Label **A** .....


Label **B** .....

Explain why your answers are more appropriate for the **A** and **B** labels.

.....  
 .....  
 .....  
 ..... [4]



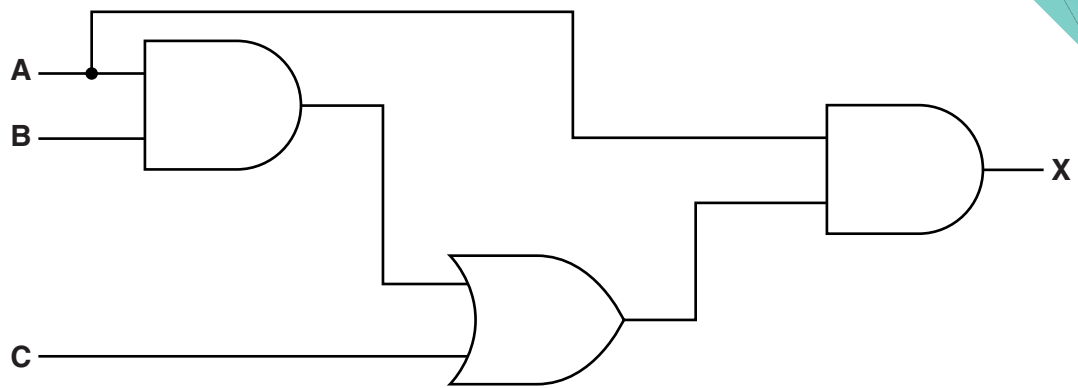(b) (i) Write the Boolean expression corresponding to the following logic circuit.



..... [2]

(ii) Use Boolean algebra to simplify the expression that you gave in **part (b)(i)**.

Show your working.

.....  
 .....  
 .....  
 .....  
 .....  
 .....  
 ..... [3]


# QUESTION 8.



5 (a) (i) A half adder is a logic circuit with the following truth table.

Input		Output	
X	Y	A	B
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

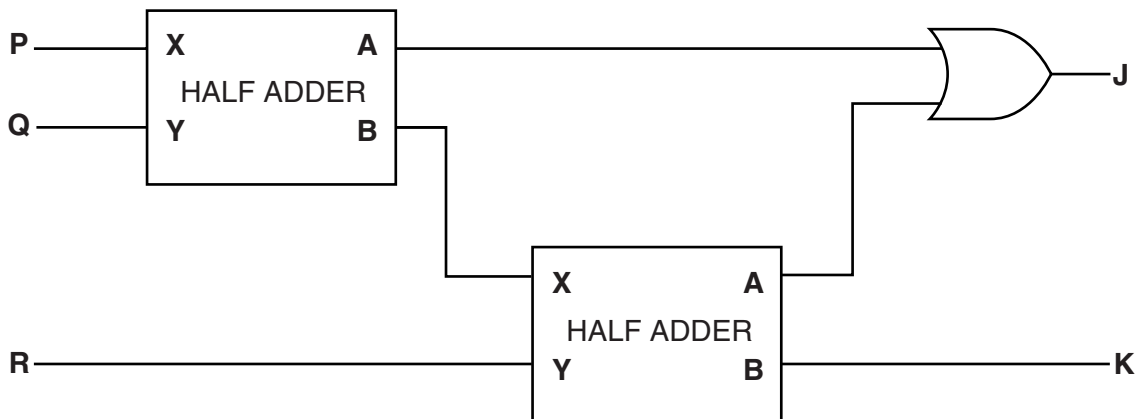The following logic circuit is constructed.



Complete the following truth table for this logic circuit.

Input			Working space	Output	
P	Q	R		J	K
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

[2]

(ii) State the name given to this logic circuit.

..... [1]



(iii) Name the labels usually given to **J** and **K**.

Label **J** .....

Label **K** .....

Explain why your answers are appropriate labels for these outputs.


.....

.....

.....

..... [4]

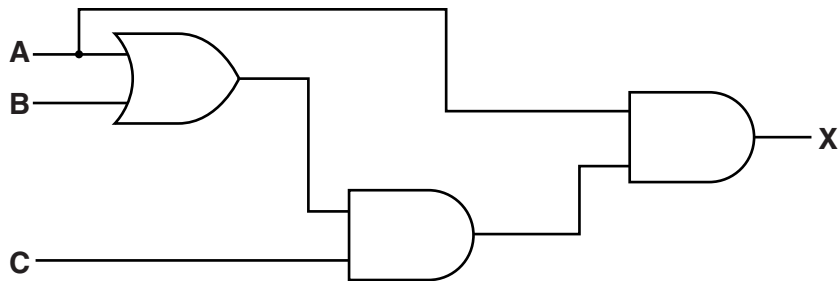(b) (i) Write down the Boolean expression corresponding to the following logic circuit:



..... [2]

(ii) Use Boolean algebra to simplify the expression given in **part (b)(i)**.

Show your working.

.....

.....

.....

.....


.....

..... [4]
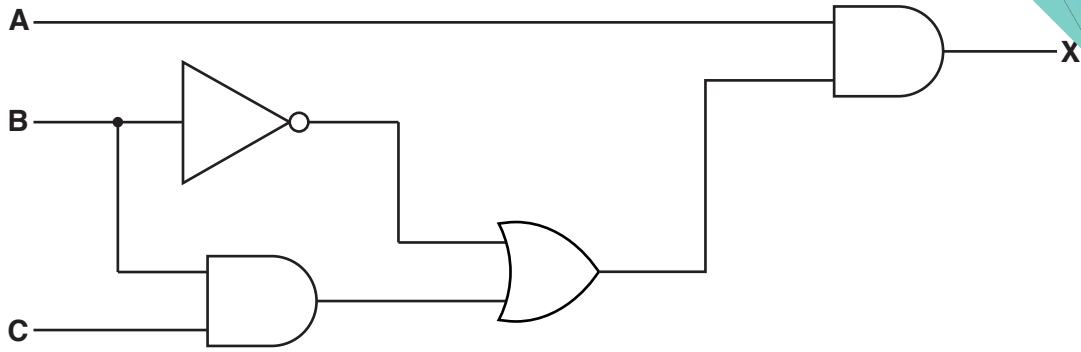
# QUESTION 9.



3 Consider the following logic circuit, which contains a redundant logic gate.



(a) Write the Boolean algebraic expression corresponding to this logic circuit.

X = .....[3]

(b) Complete the truth table for this logic circuit.

A	B	C	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[2]

(c) (i) Complete the Karnaugh Map (K-map) for the truth table in part (b).

		<b>AB</b>			
		00	01	11	10
<b>C</b>	<b>0</b>				
	<b>1</b>				

[1]

The K-map can be used to simplify the expression in part (a).

(ii) Draw loop(s) around appropriate groups to produce an optimal sum-of-products. [2]

(iii) Write a simplified sum-of-products expression, using your answer to part (ii).

X = .....[2]



(d) One Boolean identity is:

$$A + \bar{A}.B = A + B$$

Simplify the expression for X in **part (a)** to the expression for X in **part (c)(iii)**. You should use the given identity.

.....

.....

.....


.....[2]



# QUESTION 10.



3 A logic circuit is shown:

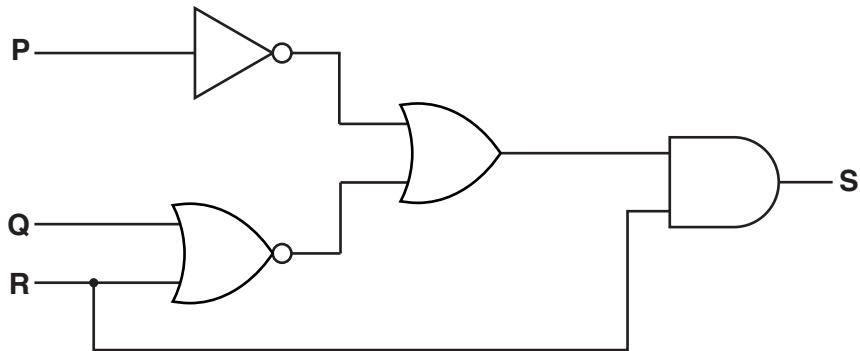

(a) Write the Boolean algebraic expression corresponding to this logic circuit:


S = .....[4]







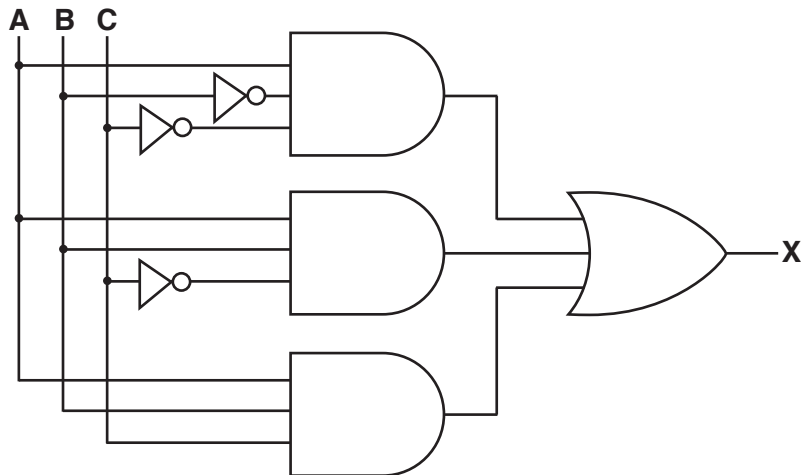(b) (i) Complete the truth table for the following logic circuit.



A	B	C	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[2]

(ii) Complete the Karnaugh Map (K-map) for the truth table in **part (b)(i)**.

		<b>AB</b>			
		00	01	11	10
<b>C</b>	<b>0</b>				
	<b>1</b>				

[1]

(iii) Draw loops around appropriate groups of 1s in the table in **part (b)(ii)** to produce an optimal sum-of-products. [2]

(iv) Using your answer to **part (b)(iii)**, write a simplified sum-of-products Boolean expression.

X = ..... [2]



(c) The truth table for a logic circuit with four inputs is shown.

INPUT				OUTPUT
A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

(i) Complete the K-map for the truth table in **part (c)**.

		<b>AB</b>			
<b>CD</b>					

[4]

(ii) Draw loops around appropriate groups of 1s in the table in **part (c)(i)** to produce an optimal sum-of-products. [2]


(iii) Using your answer to **part (c)(ii)**, write a simplified sum-of-products Boolean expression.

**X** = ..... [2]
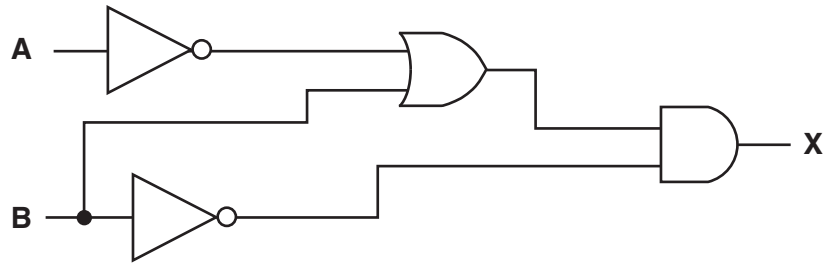
# QUESTION 12.




3 (a) The following logic circuit can be simplified to use only one gate.



Give the name of this single gate.

..... [1]

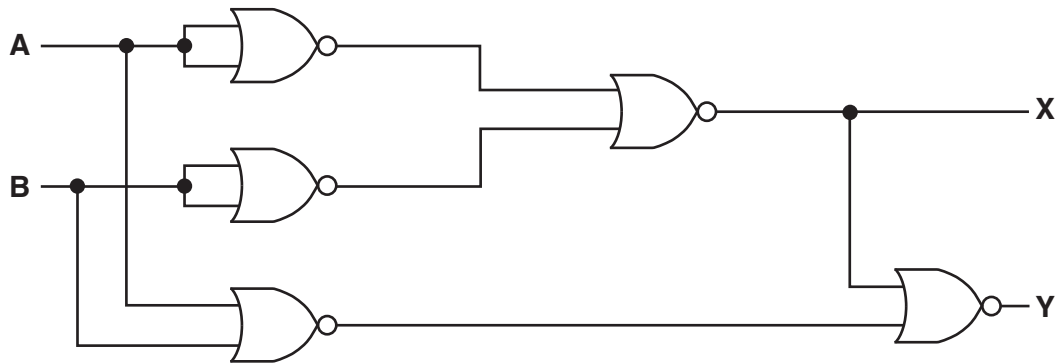(b) (i) Complete the truth table for the logic circuit.



A	B	Working space	X	Y
0	0			
0	1			
1	0			
1	1			

[2]

(ii) Give the name of the logic circuit that has this truth table.

..... [1]

(iii) Give the uses for outputs X and Y.

X .....

Y .....

[2]



(c) Consider the following Boolean algebraic expression:

$$\bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot \bar{D} + \bar{A} \cdot B \cdot \bar{C} \cdot \bar{D}$$

Use Boolean algebra to simplify the expression. Show your working.

Working .....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

Simplified expression ..... [5]

# QUESTION 13.



3 (a) A Boolean algebraic expression produces the following truth table.

INPUT			OUTPUT
A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

(i) Complete the Karnaugh Map (K-map) for the truth table.

		<b>AB</b>			
		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>C</b>	<b>0</b>				
	<b>1</b>				

[1]

The K-map can be used to simplify the expression that produced the truth table in **part (a)**.

(ii) Draw loops around appropriate groups of 1s in the K-map to produce an optimal sum-of-products. [2]

(iii) Write the simplified sum-of-products Boolean expression for the truth table.

**X** = ..... [2]





(b) A logic circuit with four inputs produces the following truth table.

INPUT				OUTPUT
A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

(i) Complete the K-map for the truth table.

		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

[4]

(ii) Draw loops around appropriate groups of 1s in the K-map to produce an optimal sum-of-products. [2]

(iii) Write the simplified sum-of-products Boolean algebraic expression for the truth table.

$X = \dots\dots\dots$  [2]

## QUESTION 14.



- 2 (a) A Boolean expression produces the following truth table.

INPUT			OUTPUT
A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- (i) Write the Boolean expression for the truth table by applying the sum-of-products.

X = .....  
 ..... [3]

- (ii) Complete the Karnaugh Map (K-map) for the truth table in **part (a)**.

		AB			
		00	01	11	10
C	0				
	1				

[1]

The K-map can be used to simplify the function in **part (a)(i)**.

- (iii) Draw loop(s) around appropriate groups in the table in **part (a)(ii)**, to produce an optimal sum-of-products. [2]
- (iv) Write, using your answer to **part (a)(iii)**, a simplified Boolean expression for your Karnaugh map.

X = ..... [2]

(b) Simplify the following expression using De Morgan's laws. Show your working.

$$\overline{(\overline{W + X}) \cdot (Y + \overline{Z})}$$

.....

.....

.....

.....

.....

.....

..... [3]

