

Cambridge International AS & A Level

CANDIDATE NAME	Solved Papers		
CENTRE NUMBER		CANDIDATE NUMBER	
PHYSICS		970	02/52

Paper 5 Planning, Analysis and Evaluation

February/March 2020

1 hour 15 minutes

You must answer on the question paper.

No additional materials are needed.

INSTRUCTIONS

- Answer all questions.
- Use a black or dark blue pen. You may use an HB pencil for any diagrams or graphs.
- Write your name, centre number and candidate number in the boxes at the top of the page.
- Write your answer to each question in the space provided.
- Do not use an erasable pen or correction fluid.
- Do not write on any bar codes.
- You may use a calculator.
- You should show all your working and use appropriate units.

INFORMATION

- The total mark for this paper is 30.
- The number of marks for each question or part question is shown in brackets [].



1 Fig. 1.1 shows a bar magnet attached to a spring.

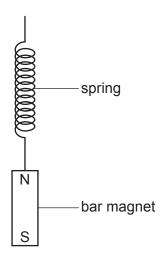


Fig. 1.1

The bar magnet is displaced a distance x from its equilibrium position and released. It then oscillates vertically.

A student investigates how the maximum induced electromotive force (e.m.f.) *E* in a coil placed below the magnet depends on *x*.

It is suggested that the relationship between E and x is

$$E = \alpha BNx \sqrt{\frac{k}{m}}$$


where \underline{B} is the magnetic flux density at one of the poles of the bar magnet, \underline{N} is the number of turns on the coil, \underline{k} is the spring constant, \underline{m} is the mass of the magnet and α is a constant.

Design a laboratory experiment to test the relationship between \underline{E} and \underline{x} . Explain how your results could be used to determine a value for α .

You should draw a diagram, on page 3, showing the arrangement of your equipment. In your account you should pay particular attention to:

- the procedure to be followed
- the measurements to be taken
- the control of variables
- the analysis of the data
- any safety precautions to be taken.

© UCLES 2020 9702/52/F/M/20

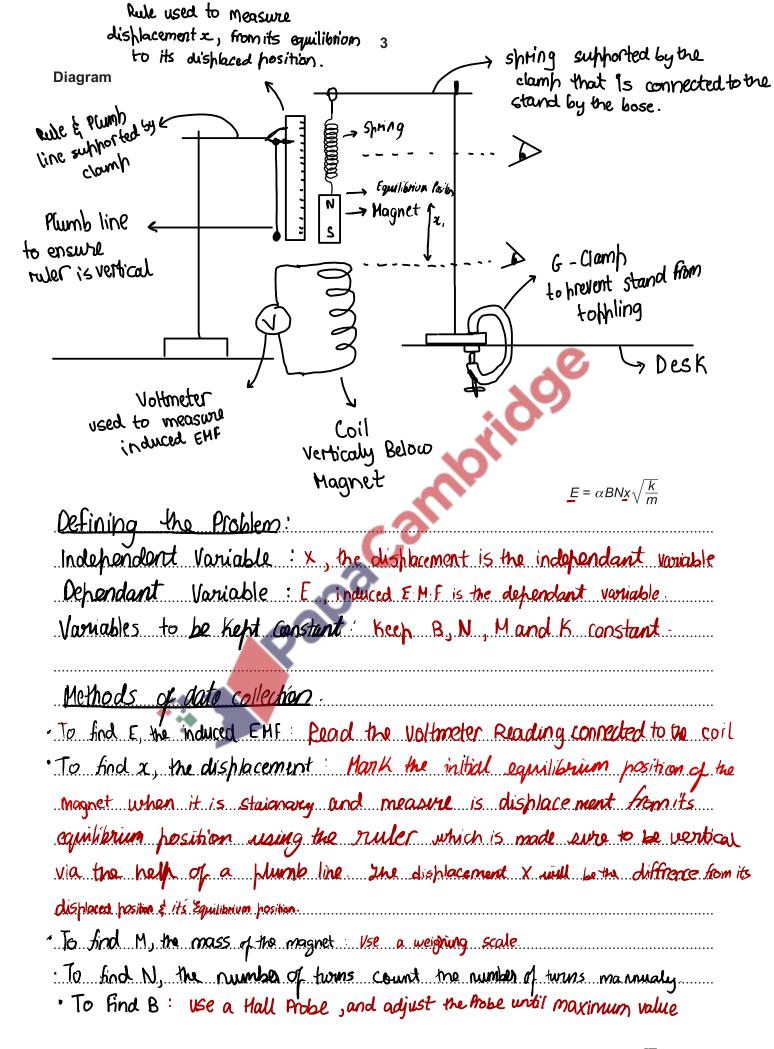

Method of Analysis:	
Plot a graph of F/V (y orais) against X/m (x axis)	
Plot a graph of E/V (yours) against x/m (x axis) The relationship will be valid if a straight line passing throught	he
orgin isproduced	
$\underline{\underline{E}} = \alpha B N \underline{x} \sqrt{\frac{k}{m}}$	
$F = \alpha BN / K $	
y my y	
gradient $\therefore \alpha = BN \int M$ gradient \sqrt{K}	
gradient / K	
Additional Petails	
* Use safety goggles to prevent injury to eyes from detached spring.	
· Use sandbox incase magnet falls	
· G-Clamp on stand to prevent it from toppling	
· Keeh distance from equilibrium position & coil constant	
· Check unstreached length of Magnet has not changed	
F=KX, to determine determine F (weight of the magnet) use F	-ma
and determine K by $K = F/x$	
· B can be measured using a Mall Probe	
· Use a vedio camera to determine the max value on the voltmet	er
play it back in slow motion & view it to get the max value.	
Reploot the experiment for each x & average E.	
·	
[1	51

2 A student investigates the discharge of a capacitor through a resistor as shown in Fig. 2.1.

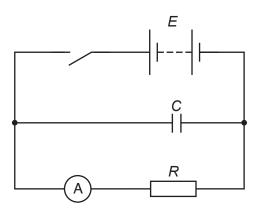


Fig. 2.1

The student initially closes the switch and charges the capacitor. The switch is then opened and a stop-watch is started. The capacitor discharges through the resistor. At different times *t* the current *I* is measured.

It is suggested that *I* and *t* are related by the equation

$$I = \frac{E}{R} e^{-\left(\frac{t}{RC}\right)}$$

where E is the e.m.f. of the power supply, C is the capacitance of the capacitor and R is the resistance of the resistor.

(a) A graph is plotted of $\ln I$ on the y-axis against t on the x-axis.

Determine expressions for the gradient and the *y*-intercept.

$$lnI = ln(E/R) + ln(e^{-C^{+}/RC})$$

$$lnI = -\frac{t}{RC} + ln(E/R)$$

$$lnI = t \times -\frac{l}{RC} + ln(E/R)$$

$$y-intercept = ln(E/R)$$
[1]

(b) Values of *t* and *I* are given in Table 2.1.

and I did given	Table 2.1	1 Use 3SF	for value 1-2 sf for uncertainity
t/s	Ι/μΑ	ln (I/μA)	
0	46 ± 2	3.83 ± 0.04	$\ln (49) - \ln (46)$ ≈ 0.04
12	40 ± 2	3.69 ± 0.05	in (a2) - In (40) ≈ 0.05
24	34 ± 2	3.53 ± 0.06	in (36) - In (34) ~ 0.06
36	28 ± 2	3.33 ± 0.07	
48	24 ± 2	3.18 + 0.08	
60	20 ± 2	3.00 ± 0.1	

Calculate and record values of $\ln (I/\mu A)$ in Table 2.1. Include the absolute uncertainties in $\ln (I/\mu A)$.

[2]

(c) (i) Plot a graph of $\ln(I/\mu A)$ against t/s. Include error bars for $\ln(I/\mu A)$.

[2]


- (ii) Draw the straight line of best fit and a worst acceptable straight line on your graph. Both lines should be clearly labelled. [2]
- (iii) Determine the gradient of the line of best fit. Include the absolute uncertainty in your answer.


Gradient of Line of Best Fit: Gradient of line of Worst Fit:

Points:
$$(10,3.71)$$
 $(45,3.2)$ Points: $(0,3.79)$ $(38,3.35)$
 $m_B = \frac{3.2 - 3.71}{45 - 10} = -0.01457$
 $m_B = \frac{3.2 - 3.71}{45 - 10} = -0.01457$

uncertainity = Gradient of line of Best fit - Gradient of line of worst fit = -0.01457 - (-0.01578)= ± 0.003 aradient = -0.0146 ± 0.003

© UCLES 2020

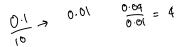

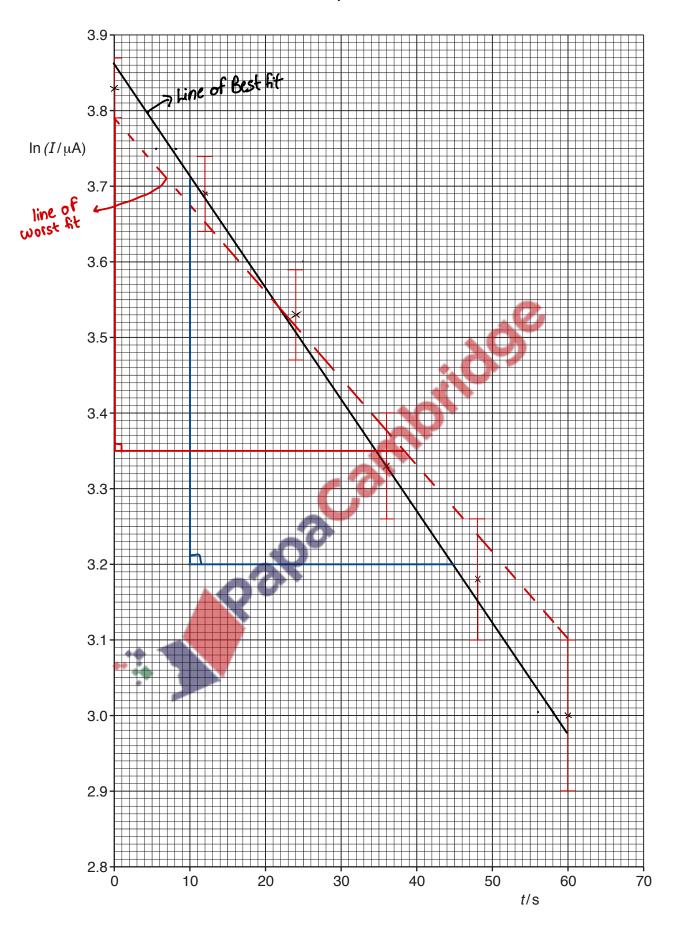

(iv) Determine the *y*-intercept of the line of best fit. Do **not** include the absolute uncertainty in your answer.

(d) (i) Using your answers to (a), (c)(iii) and (c)(iv), determine the values of C and E. Include appropriate units.

Data:
$$R = 150 \text{ k}\Omega$$

gradient = $\frac{-1}{CR}$
 $-0.0146 = \frac{-1}{C \times 150 \times 10^3}$
 $C = \frac{-1}{-0.0146 \times 150} \times 10^3$
 $C = \frac{-1}{-0.0146 \times 150}$

(ii) The percentage uncertainty in the resistance R of the resistor is 5%.

Determine the absolute uncertainty in C.

7. Uncertainty = 0.05 + (uncertainty gradient gradient x100) =
$$\left(5 + \left(\frac{0.003}{0.0146} \times 100\right)\right)$$

Absolute uncertainty = $C \times 7$ uncertainty

absolute uncertainty in $C = 1.17 \times 10^{-4} \text{ CV}^{-1}$

[1]

(e) Using your results, determine the value of *I* after the capacitor has discharged through the resistor for 2.0 minutes.

$$I = \frac{E}{R}e^{-\left(\frac{t}{RC}\right)} \qquad I = \frac{7 \cdot 12}{150 \times 10^{3}} \times C \qquad \frac{2 \times 60}{150 \times 10^{3} \times 4 \cdot 57 \times 10^{-4}}$$

$$= 8 \cdot 244 \times 10^{-6}$$

$$\approx 8 \cdot 24 \times 10^{-6}$$

$$I = \frac{8 \cdot 24 \times 10^{-6}}{150 \times 10^{3}} \times C \qquad A = 10$$
[Total: 15]

Permission to reproduce items where third-party owned material protected by copyright is included has been sought and cleared where possible. Every reasonable effort has been made by the publisher (UCLES) to trace copyright holders, but if any items requiring clearance have unwittingly been included, the publisher will be pleased to make amends at the earliest possible opportunity.

To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced online in the Cambridge Assessment International Education Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download at www.cambridgeinternational.org after the live examination series.

Cambridge Assessment International Education is part of the Cambridge Assessment Group. Cambridge Assessment is the brand name of the University of Cambridge Local Examinations Syndicate (UCLES), which itself is a department of the University of Cambridge.