

## Alternating current - 2021 A2 Physics

### 1. Nov/2021/Paper\_41/No.9

- (a) State, by reference to the power dissipated in a resistor, what is meant by the root-mean-square (r.m.s.) value of an alternating voltage.


Is the value of constant voltage (or current)  
that produces the same power in a resistor  
as the mean power of the alternating  
voltage (or current). [2]

- (b) A coil is rotating freely, on frictionless bearings, at constant speed in a uniform magnetic field. This rotation causes an induced alternating electromotive force (e.m.f.) across the open terminals of the coil. The induced e.m.f. has r.m.s. value 12 V and frequency 50 Hz.

The speed of rotation of the coil is now doubled.

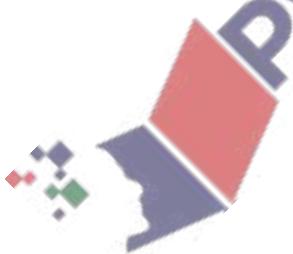- (i) State and explain, with reference to the principles of electromagnetic induction, the effect of the increased speed of rotation on the r.m.s. value of the induced e.m.f.

- At high speed, the rate of cutting of flux will double. This doubles the r.m.s. and thus doubles the induced e.m.f. [2]



- (ii) On Fig. 9.1, sketch the variation with time  $t$  of the induced e.m.f.  $E$  across the terminals of the coil at the **increased** speed of rotation. Your line should extend from time  $t = 0$  to time  $t = 20\text{ ms}$ . Assume that  $E = 0$  when  $t = 0$ .

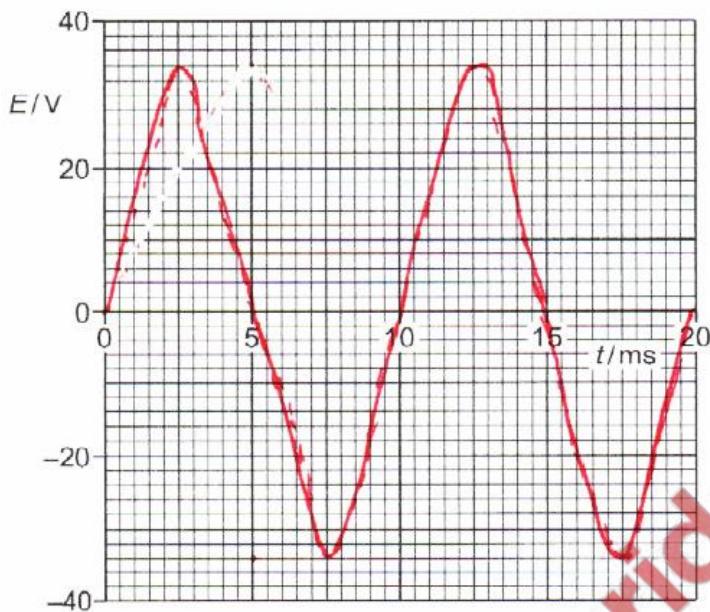


Fig. 9.1

$$V_{\text{r.m.s.}} = \frac{V_0}{\sqrt{2}}$$

$$V_0 = V_{\text{r.m.s.}} \times \sqrt{2}$$

$$= 24 \times \sqrt{2}$$

$$= 33.9 \text{ V}$$

$$\approx 34 \text{ V}$$

$$T = \frac{1}{50}$$

$$= 0.02 \text{ s}$$

$$= 20 \text{ ms}$$

Double speed  
will halve the  
period

$$\frac{20}{2} = 10 \text{ ms}$$

[3]

$$\therefore T = 10 \text{ ms}$$

- (c) State and explain the effect on the motion of the coil in (b) of connecting a load resistor across its terminals.

— Current flowing in the resistor  
dissipates the energy of rotation  
so the coil will stop to rotate.

[2]

[Total: 9]

2. Nov/2021/Paper\_42/No.10

Fig. 10.1 shows a simple laminated iron-cored transformer consisting of a primary coil of 25000 turns and a secondary coil of 625 turns.

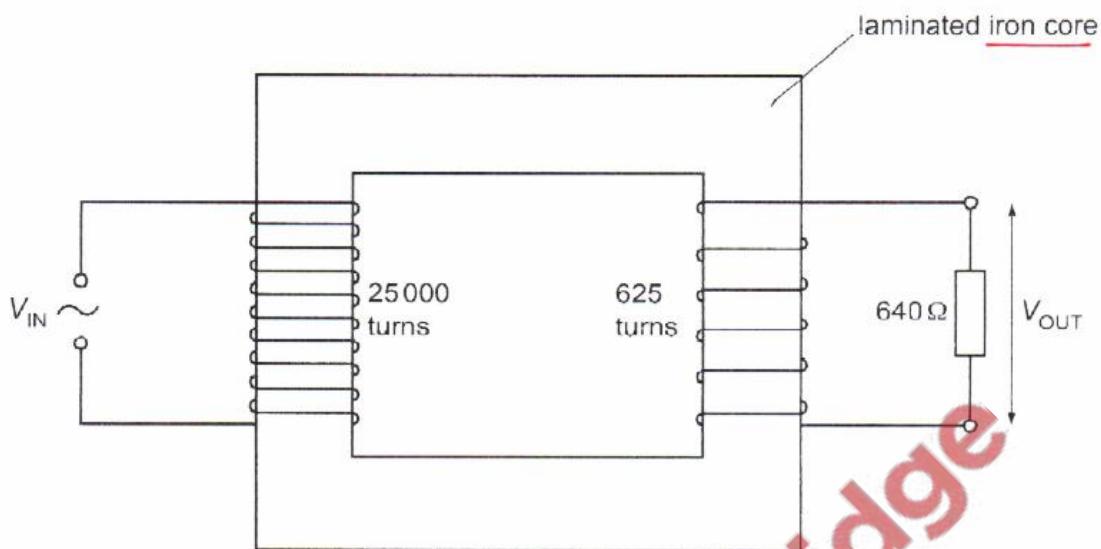


Fig. 10.1

The output potential difference (p.d.)  $V_{\text{OUT}}$  is applied to a load resistor of resistance  $640\Omega$ .

- (a) (i) State the function of the iron core.

to increase the magnetic flux linkage between the coils. [1]

- (ii) Explain why the iron core is laminated.

- To reduce eddy currents (induced currents) and hence minimise energy losses. [2]

- (b) The input p.d.  $V_{\text{IN}}$  is a sinusoidal alternating voltage of peak value  $12\text{kV}$  and period  $40\text{ ms}$ .

- (i) Calculate the maximum value of  $V_{\text{OUT}}$ .

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{N_s}{N_p} \quad | \quad V_{\text{out}} = \frac{12000 \times 625}{25000}$$

$$V_{\text{out}} = V_{\text{in}} \times \frac{N_s}{N_p} \quad | \quad \text{maximum } V_{\text{OUT}} = \dots \text{ V} \quad [1]$$


- (ii) Calculate the root-mean-square (r.m.s.) current in the load resistor.

$$I = \frac{V}{R} \quad ; \quad I_{\text{rms}} = \frac{300V}{640\Omega} \div \sqrt{2} \quad ; \quad I_{\text{r.m.s.}} = 0.33 \text{ A}$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}} \quad ; \quad = \frac{300}{640 \times \sqrt{2}} \quad ; \quad$$

r.m.s. current = ..... 0.33 A [1]

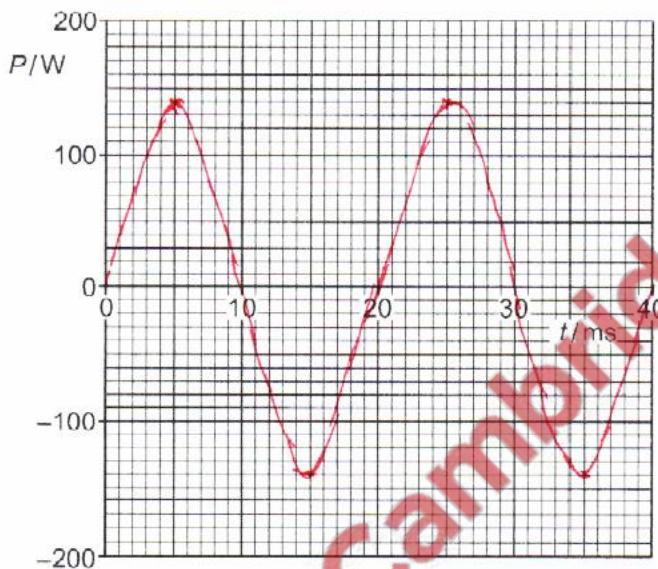- (iii) On Fig. 10.2, sketch the variation with time  $t$  of the power  $P$  dissipated in the load resistor for time  $t = 0$  to  $t = 40$  ms. Assume that  $P = 0$  when  $t = 0$ .



$$I_{\text{v.m.s.}} = \frac{I_0}{\sqrt{2}}$$

$$I_0 = I_{\text{v.m.s.}} \times \sqrt{2}$$

$$= 0.33 \times \sqrt{2}$$

$$= 0.466 \text{ A}$$

$$P = I \times V$$

$$= 0.466 \times 300$$

$$= 140 \text{ W}$$

Fig. 10.2

[3]

- (c) Explain, with reference to Fig. 10.2, why the mean power in the load resistor is 70W.

- The power curve is symmetrical about the mid-point on the power axis
- So the mean power is half the peak power.

[2]

[Total: 10]

3. June/2021/Paper\_42/No.10

- (a) By reference to heating effect, explain what is meant by the *root-mean-square (r.m.s.)* value of an alternating current.

- this is the value of direct current  
that produces the same heating effect  
as the alternating current [2]

- (b) The variations with time  $t$  of two currents  $I_1$  and  $I_2$  are shown in Fig. 10.1 and Fig. 10.2.

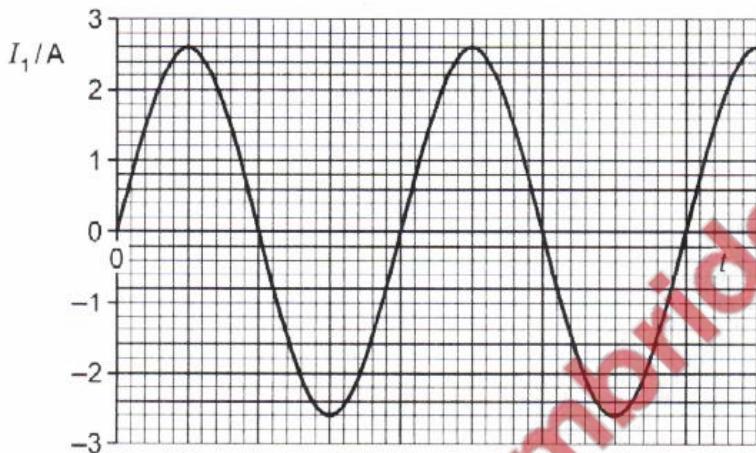


Fig. 10.1

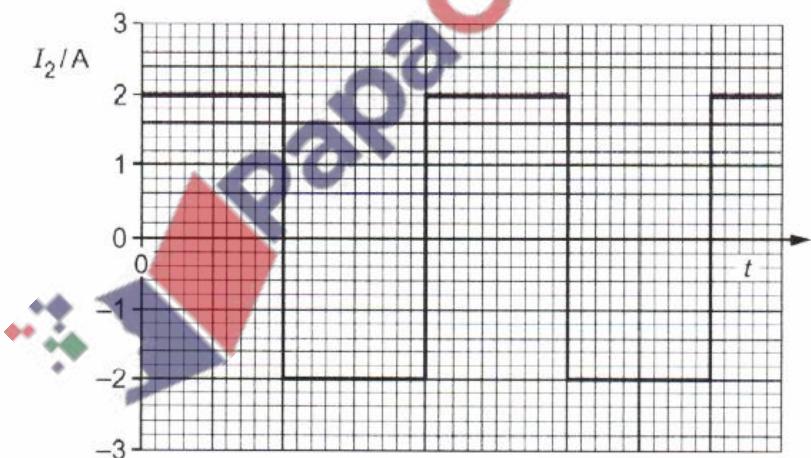


Fig. 10.2

- (i) Use Fig. 10.1 to determine the peak value and the r.m.s. value of the current  $I_1$ .

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

$$= \frac{2.6}{\sqrt{2}} = 1.838 \approx 1.8$$

peak value = ..... A 2.6  
r.m.s. value = ..... A 1.8 [1]

- (ii) Use Fig. 10.2 to determine the peak value and the r.m.s. value of the current  $I_2$ .

peak value = ..... A 2.0  
r.m.s. value = ..... A 2.0

The current  $I_2$  is not fluctuating only  
(changes direction at constant time).

- (c) The variation with time  $t$  of the supply voltage  $V$  to a house is given by the expression

$$V = 240 \sin kt$$

where  $V$  is in volts,  $t$  is in seconds and  $k$  is a constant with unit  $\text{rad s}^{-1}$ .

- (i) The frequency of the supply voltage is 50 Hz.

↑ Angular velocity

Determine  $k$  to two significant figures.

$$\omega = 2\pi f$$

$$\therefore k = 2\pi f$$

$$= 2\pi \times 50$$

$$= 310 \text{ rad s}^{-1}$$

  $k = ..... \text{ rad s}^{-1}$  [2] 310

- (ii) The supply voltage is applied to a heater. The mean power of the heater is 3.2 kW.

Calculate the resistance of the heater.

$$P = \frac{V_{\text{rms}}^2}{R}$$

$$R = \frac{V_{\text{rms}}^2}{P}$$

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$$

$$= \frac{240}{\sqrt{2}}$$

  $V_{\text{rms}} = 169.7 \text{ V}$   
 $\therefore R = \frac{169.7^2}{3.2 \times 10^3}$   
 $= 8.999 \Omega$   
 $\approx 9.0$

resistance = ..... 9.0  $\Omega$  [2]

[Total: 8]

4. March/2021/Paper\_42/No.10

The output potential difference (p.d.) of an alternating power supply is represented by

$$V = 320 \sin(100\pi t)$$

$$V = V_0 \sin \omega t$$

where  $V$  is the p.d. in volts and  $t$  is the time in seconds.

- (a) Determine the root-mean-square (r.m.s.) p.d. of the power supply.

$$V_{\text{r.m.s.}} = \frac{V_0}{\sqrt{2}}$$

$$= \frac{320}{\sqrt{2}} = 226$$

$$\text{r.m.s. p.d.} = \dots \text{V} [1]$$

$$230\text{V}$$

- (b) Determine the period  $T$  of the output.

$$\omega = 100\pi$$

$$T = \frac{2\pi}{\omega}$$

$$= \frac{2\pi}{100\pi} = \frac{2}{100} = 0.02$$

$$T = \dots \text{s} [2]$$

$$0.02$$

- (c) The power supply is connected to resistor  $R$  and a diode in the circuit shown in Fig. 10.1.


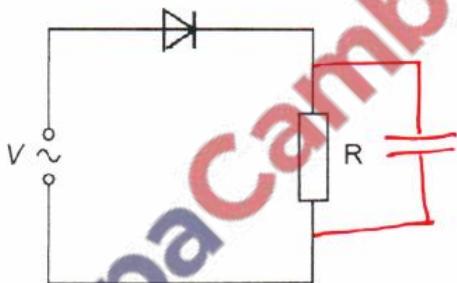


Fig. 10.1


- (i) State the name of the type of rectification produced by the diode in Fig. 10.1.

half-wave rectification

[1]

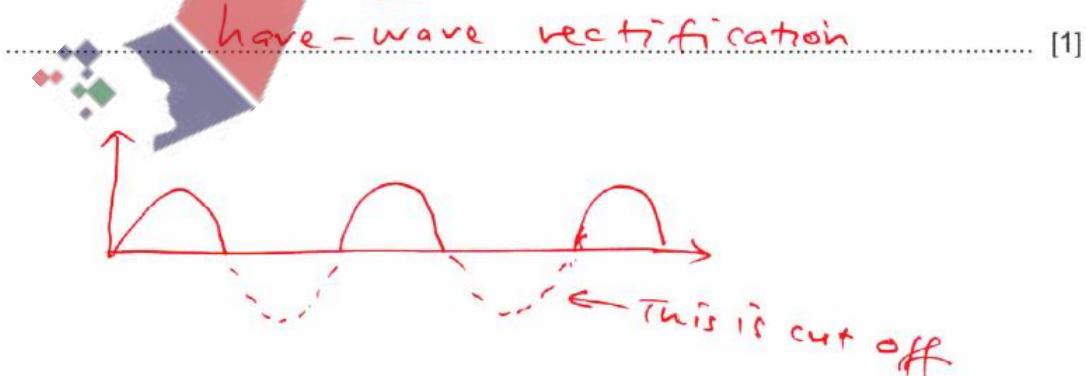

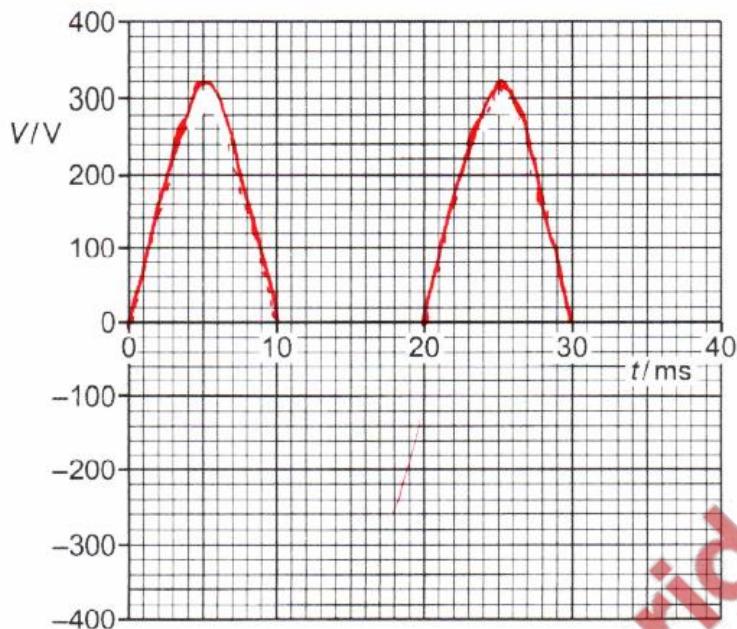- (ii) On Fig. 10.2 sketch the variation with time  $t$  of the p.d.  $V_R$  across R from time  $t = 0$  to time  $t = 40\text{ ms}$ .



$$\begin{aligned}V_0 &= 320\text{V} \\T &= 0.02 \\&= 20\text{ms.}\end{aligned}$$

Fig. 10.2

[3]

- (iii) On Fig. 10.1, draw the symbol for a component that may be connected to produce smoothing of  $V_R$ .

[1]

↑  
done by a capacitor.

[Total: 8]

