

1. Nov/2022/Paper_11/No.2

A voltmeter connected across a resistor in a circuit reads 3.6 V.

What could be the current in the resistor and the resistance of the resistor?

	current	resistance
A	150 mA	0.24 kΩ
B	15 mA	2.4 kΩ
C	1.5 mA	0.24 MΩ
D	15 μA	240 kΩ

$$V = IR$$

$$\leftarrow 150 \times 10^{-3} \times 0.24 \times 10^3 = 36V$$

$$\leftarrow 15 \times 10^{-3} \times 2.4 \times 10^3 = 36V$$

$$\leftarrow 1.5 \times 10^{-3} \times 0.24 \times 10^6 = 360V$$

$$\leftarrow 15 \times 10^{-6} \times 240 \times 10^3 = \underline{3.6V} \checkmark$$

2. Nov/2022/Paper_11/No.31

A length of wire RS has a circular cross-section.



At end R of the wire, the cross-sectional area is A.

At end S of the wire, the cross-sectional area is $\frac{A}{2}$.

Charge Q takes time t to pass through end R of the wire. There is a constant electric current in the wire.

How much charge will pass through end S in a time interval of $\frac{t}{4}$?

A $\frac{Q}{8}$

B $\frac{Q}{4}$

C $\frac{Q}{2}$

D Q

$$I = \frac{Q}{t}$$

If Q takes t time
Then at $\frac{t}{4} = \frac{Q}{4} \checkmark$

3. Nov/2022/Paper_11/No.32

A power supply is connected to a component by connecting wires of total resistance 4.9 Ω.

The power supply has an output power of 3.6 W and a terminal potential difference of 12 V.

How much thermal energy is dissipated in the connecting wires in a time of 1.0 hour?

A 0.44 J

B 29 J

C 1.6 kJ

D 11 kJ

$$P = IV \quad ; \quad I = \frac{3.6}{12} = 0.3A \quad ; \quad E = P \times t \quad ; \quad E = (0.3)^2 \times 4.9 \times 3600$$

$$I = \frac{P}{V} \quad ; \quad = 12A \times t \quad ; \quad = 1587.6 J \approx 1.6 kJ$$

4. Nov/2022/Paper_11/No.33

A copper wire is to be replaced by an aluminium alloy wire of the same length and resistance. Copper has half the resistivity of the alloy.

What is the ratio $\frac{\text{diameter of alloy wire}}{\text{diameter of copper wire}}$?

- (A) $\sqrt{2}$ B 2 C $2\sqrt{2}$ D 4


d_c - diameter of copper wire
 d_A - diameter of Al alloy
 $R = \frac{\rho l}{\pi \left(\frac{d}{2}\right)^2}$
 Copper:
 $R = \frac{\frac{1}{2} \rho \times l}{\pi \times \left(\frac{d_c}{2}\right)^2}$
 $= \frac{\frac{1}{2} \rho \times l}{\pi \times \frac{d_c^2}{4}}$

Alloy:
 $R = \frac{\rho \times l}{\pi \times \frac{d_A^2}{4}}$
 Equilibre:
 $\frac{\frac{1}{2} \rho \times l}{\pi \times \frac{d_A^2}{4}} = \frac{\frac{1}{2} \rho \times l}{\pi \times \frac{d_c^2}{4}}$
 $\frac{1}{d_A^2} = \frac{1}{d_c^2}$
 $\frac{d_A^2}{1} = \frac{d_c^2}{\frac{1}{2}} = 2d_c^2$
 $\frac{d_A}{d_c} = \sqrt{2}$

$\frac{d_A^2}{d_c^2} = 2$
 Take square root
 $\frac{d_A}{d_c} = \sqrt{2}$

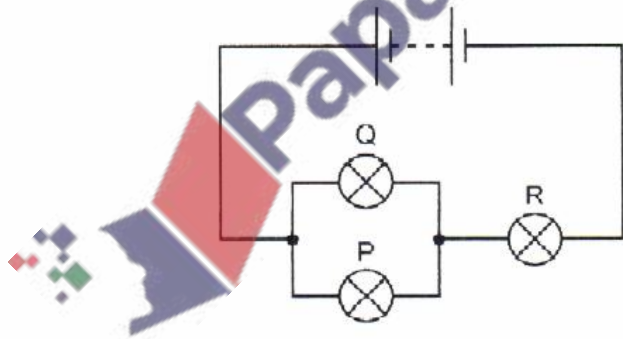5. Nov/2022/Paper_11/No.34

Three identical filament lamps, P, Q and R, are connected to a battery of negligible internal resistance, as shown.



- In parallel Q and P offer less resistance
- But when Q breaks resistance by P will increase to total circuit resistance

The filament wire in lamp Q breaks so that it no longer conducts.

What are the changes in the brightness of lamps P and R?

	lamp P	lamp R
A	brighter	brighter
(B)	brighter	dimmer
C	dimmer	brighter
D	dimmer	dimmer

- Circuit becomes a series circuit when Q breaks.
- Since P and R are identical, then they share the battery voltage equally.
- So p.d for P increases, - brighter.
- p.d for R decreases - less brighter.

6. Nov/2022/Paper_11/No.35

Which ratio has the same units as electromotive force (e.m.f.)?

- A charge per unit energy transferred
- B charge per unit time
- C energy transferred per unit charge
- D energy transferred per unit time

$$e.m.f = V$$

$$\text{Voltage} = \frac{\text{Energy}}{\text{Charge}}$$


$$V = \frac{J}{C}$$

7. Nov/2022/Paper_11/No.36

A circuit consists of a battery, a voltmeter and five fixed resistors, as shown.

When voltmeter is zero, then the arrangement is called wheatstone bridge.

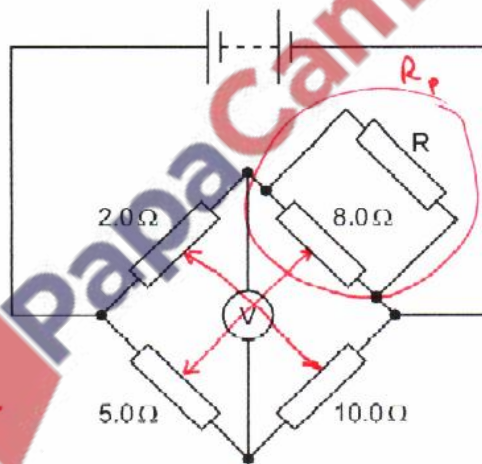- So multiply opposite resistor and equalize them



$$20 \times 10 = 5 \times R_p$$

$$20 = 5 R_p$$

$$R_p = \frac{20}{5} = 4 \Omega$$

but R_p is parallel.

$$4 = \frac{8 \times R}{8 + R}$$

$$8R = 32 + 4R$$

$$8R - 4R = 32$$

$$4R = 32$$

$$R = 8 \Omega$$

The voltmeter reading is zero.

What is the resistance of resistor R?


- A 1.1Ω
- B 2.1Ω
- C 4.0Ω
- D 8.0Ω

8. Nov/2022/Paper_11/No.37

A battery of electromotive force (e.m.f.) 6.0 V and negligible internal resistance is connected to a voltmeter and four other components, as shown.

The voltmeter is connected between points X and Y. The positive terminal of the voltmeter is connected to X and the negative terminal of the voltmeter is connected to Y.

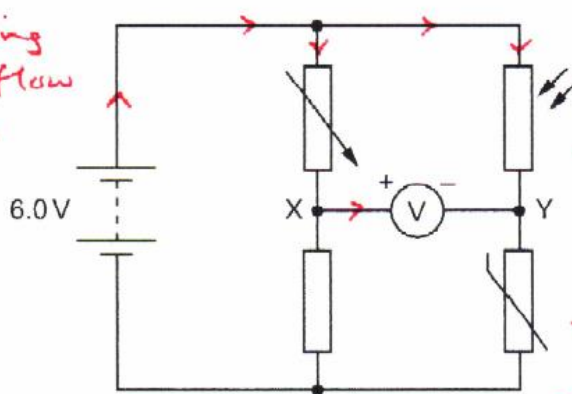For the reading current must flow from X to Y.



When LDR intensity decreases and its resistance increase.

- So more current will flow through variable resistor than the LDR
- So X will have more current than Y

- Hence current can flow from X to Y.

Initially, the resistance of each of the four components is 1.0 kΩ.

Which change, on its own, will cause the voltmeter to show a positive reading?

- A Decrease the temperature of the thermistor.
- B Increase the resistance of the variable resistor.
- C Reduce the intensity of light incident on the light-dependent resistor (LDR).
- D Replace the fixed resistor with a 500 Ω resistor.

↑
Current need to move from X to Y.

9. Nov/2022/Paper_12/No.31

A nichrome wire has a resistance of 15 Ω and a diameter of 3.0 mm. The number density of the free electrons in nichrome is $9.0 \times 10^{28} \text{ m}^{-3}$.

A potential difference (p.d.) of 6.0 V is applied between the ends of the wire.

What is the average drift speed of the free electrons in the wire?

- A $9.8 \times 10^{-7} \text{ ms}^{-1}$
- B $3.9 \times 10^{-6} \text{ ms}^{-1}$
- C $6.1 \times 10^{-6} \text{ ms}^{-1}$
- D $2.5 \times 10^{-5} \text{ ms}^{-1}$

$$V = \frac{I}{n A e}$$



$$I = \frac{V}{R} = \frac{6V}{15\Omega} = 0.4A$$

$$A = \pi r^2 = \pi \times (1.5 \times 10^{-3})^2$$

$$V = \frac{0.4}{9.0 \times 10^{28} \times \pi \times (1.5 \times 10^{-3})^2 \times 1.6 \times 10^{-19}} = 3.929 \times 10^{-6} \text{ ms}^{-1} = 3.9 \times 10^{-6} \text{ ms}^{-1}$$

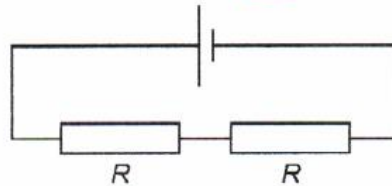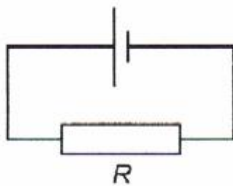10. Nov/2022/Paper_12/No.32

The diagrams show two different circuits.



The cells in each circuit have the same electromotive force (e.m.f.) and negligible internal resistance. The three resistors each have the same resistance R .

In the circuit on the left, the power dissipated in the resistor is P .

What is the total power dissipated in the circuit on the right?

- A $\frac{P}{4}$ B $\frac{P}{2}$ C P D $2P$

$P = \frac{V^2}{R}$
 Resistor in series
 $= R + R = 2R$
 $\text{Power} = \frac{V^2}{2R} = \frac{1}{2} \left(\frac{V^2}{R} \right) = \frac{1}{2} P = \frac{P}{2}$

11. Nov/2022/Paper_12/No.33

The potential difference (p.d.) across a filament lamp is increased.

Which statement is correct?

- A The resistance of the lamp decreases because the temperature decreases.
 B The resistance of the lamp decreases because the temperature increases.
 C The resistance of the lamp increases because the temperature decreases.
 D The resistance of the lamp increases because the temperature increases.

$= \frac{1}{2} P = \frac{P}{2}$

12. Nov/2022/Paper_12/No.34

A metal wire has resistance R .

The wire is stretched so that its diameter decreases to 94.0% of the original diameter.

The volume of the wire is unchanged.

What is the resistance of the stretched wire?

- A $1.06R$ B $1.13R$ C $1.20R$ D $1.28R$

new diameter = $0.94d$ / New length = $1.1377l$

$0.94^2 = 0.8836$ / $0.8836 \times l = 1$ / $l = \frac{1}{0.8836} = 1.137$

$R = \frac{\rho l}{\pi \frac{d^2}{4}}$ / $V = A \times l$ / $V_{\text{new}} = \pi (0.94d)^2 \times l$
 $= \frac{\rho \times 1.1377l}{0.8836 \frac{\pi d^2}{4}} = \frac{1.1377}{0.8836} \left(\frac{\rho l}{\pi \frac{d^2}{4}} \right) = 1.28R$

13. Nov/2022/Paper_12/No.35


The diagram shows a cell of electromotive force (e.m.f.) 3.0V and internal resistance 4.7Ω connected across a lamp. The lamp has a resistance of 9.3Ω.

$$E = I(R+r)$$

$$I = \frac{E}{R+r}$$

$$= \frac{3.0}{9.3 + 4.7}$$

$$= 0.214A$$

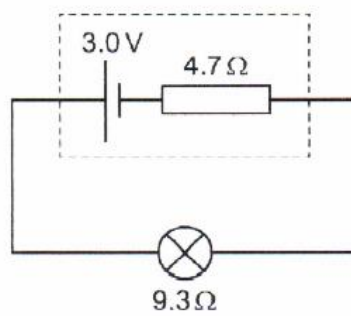

$$P = I^2 R$$

$$= 0.214^2 \times 4.7$$

$$= 0.2152$$


$$\approx 0.22W$$

What is the power dissipated by the internal resistance of the cell?

- A 0.22W B 0.43W C 0.64W D 1.0W

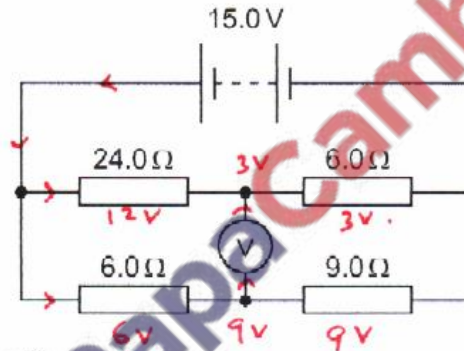14. Nov/2022/Paper_12/No.36

A circuit consists of a battery, a high-resistance voltmeter and four fixed resistors, as shown. The battery has an electromotive force (e.m.f.) of 15.0V and negligible internal resistance.



What is the reading on the voltmeter?

- A 3.0V B 6.0V C 9.0V D 12.0V

Find voltage on each resistor using potential divider method.

$$V = \frac{15 \times 24}{24 + 6} = 12V$$

$$15 - 12 = 3V$$

$$V = \frac{6 \times 15}{6 + 9} = 6V$$


$$15 - 6 = 9V$$

- The voltage at the junctions will be 3V and 9V respectively

- The difference will be the voltmeter reading
 $9 - 3 = 6V$

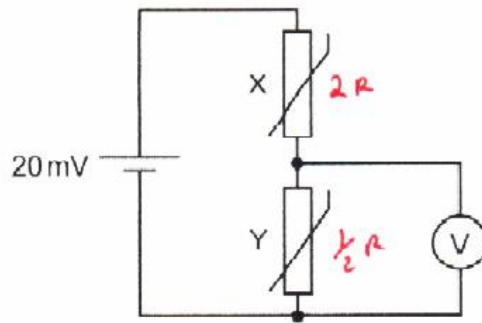15. Nov/2022/Paper_12/No.37

A potential divider circuit is designed to detect the difference in temperature between two different places.



$$V = \frac{20 \times \frac{1}{2} R}{2R + \frac{1}{2} R}$$

$$= \frac{10R}{\frac{5}{2} R}$$

$$= \frac{20}{5}$$

$$V = 4 \text{ mV}$$

The cell has electromotive force (e.m.f.) 20 mV and negligible internal resistance.

Initially, thermistors X and Y are at the same temperature and have the same resistance. The voltmeter reads 10 mV. X is then placed in a cold environment and its resistance doubles. Y is placed in a warm environment and its resistance halves.

What is the new reading on the voltmeter?

- A 4 mV B 5 mV C 15 mV D 16 mV

16. Nov/2022/Paper_13/No.30

There is an electric current in a copper wire.

Which statement describing the average drift speed of the charge carriers in the wire is correct?

- A It is nearly $3 \times 10^8 \text{ ms}^{-1}$.
 B It is proportional to the cross-sectional area of the wire.
 C It is proportional to the length of the wire.
 D It is proportional to the magnitude of the current.

$$I = nA v q$$

$$v = \frac{I}{nAq}$$


but $nAq = \text{constant}$

$$\Rightarrow v = kI$$

$$\therefore v \propto I$$

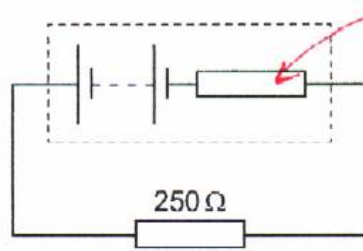17. Nov/2022/Paper_13/No.31

A battery with a constant internal resistance is connected to a resistor of resistance $250\ \Omega$, as shown.



$$E = VIt$$

$$6 = V \times 40 \times 10^{-3} \times 60$$

$$6 = V \times 2.4$$

$$V = \frac{6}{2.4}$$

$$= 2.5\text{ V}$$

The current in the resistor is 40 mA for a time of 60 s . During this time 6.0 J of energy is dissipated by the internal resistance.

What is the energy supplied to the external resistor during the 60 s and the electromotive force (e.m.f.) of the battery?

	energy/J	e.m.f./V
A	30	2.5
B	30	7.5
C	24	10.0
D	24	12.5

Voltage across $250\ \Omega$ resistor

$$V = IR$$

$$= 40 \times 10^{-3} \times 250$$

$$= 10\text{ V}$$

$$E = IR + Ir$$

$$= 10 + 2.5$$

$$= 12.5\text{ V}$$


$$E = VIt$$

$$= 10 \times 40 \times 10^{-3} \times 60$$

$$= 24\text{ J}$$

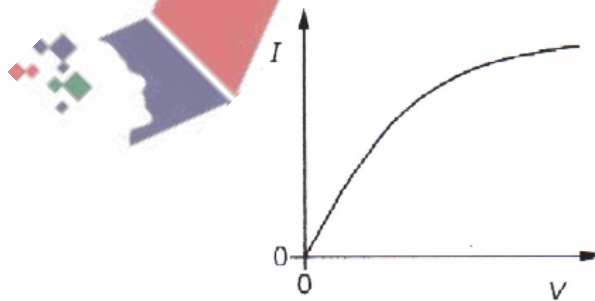18. Nov/2022/Paper_13/No.32

Which component has the I - V graph shown?



- A** filament lamp
- B metallic conductor at constant temperature
- C resistor of fixed resistance
- D semiconductor diode

19. Nov/2022/Paper_13/No.33

Two wires, P and Q, have the same resistance. Wire Q is made of material that has twice the resistivity of the material used to make wire P. The diameter of wire Q is twice the diameter of wire P.

What is the ratio $\frac{\text{length of wire P}}{\text{length of wire Q}}$?

A $\frac{1}{8}$

B $\frac{1}{4}$

C $\frac{1}{2}$

D $\frac{2}{1}$

$$R_p = R_q$$

$$R_p = \frac{\rho \times l_p}{\pi \times \left(\frac{d}{2}\right)^2} = \frac{\rho \times l_p}{\pi \times \frac{d^2}{4}}$$

$$R_q = \frac{2\rho \times l_q}{\pi \times \left(\frac{2d}{2}\right)^2} = \frac{2\rho \times l_q}{\pi \times d^2}$$

$$\frac{\rho \times l_p}{\pi \times \frac{d^2}{4}} = \frac{2\rho \times l_q}{\pi \times d^2}$$

$$\frac{l_p}{\frac{1}{4}} = 2l_q$$

$$\frac{l_p}{l_q} = 2 \times \frac{1}{4} = \frac{1}{2}$$

20. Nov/2022/Paper_13/No.35

Each of Kirchhoff's laws is linked to the conservation of a physical quantity.

Which conserved physical quantities are used in the derivation of Kirchhoff's first law and of Kirchhoff's second law?


	Kirchhoff's first law	Kirchhoff's second law
A	energy	charge
B	energy	momentum
<input checked="" type="radio"/> C	charge	energy
D	momentum	energy

1st law:
 Sum of currents into a junction is equal to sum of currents out of the junction.
 Conservation of charge
 charge not consumed.

2nd Law:
 Sum of emfs in a closed circuit is equal to sum of p.d.s in the circuit

6 Three batteries and three identical resistors are connected in a circuit PQR, as shown.

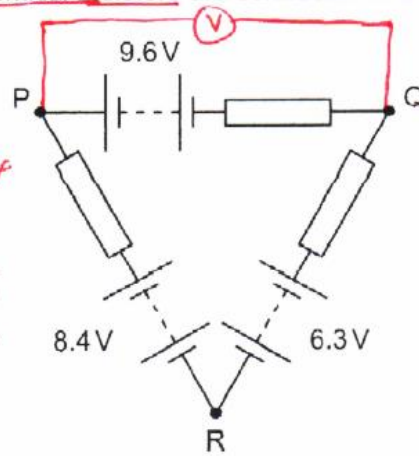Find the emf of battery
 $\text{e.m.f} = 9.6 + 6.3 - 8.4$
 $= 7.5 \text{ V}$
 Since resistors are identical, find p.d across each resistor
 $\frac{7.5}{3} = 2.5 \text{ V}$



If you cannot a voltmeter across PQ .
 - voltmeter reading will be
 $9.6 \text{ V} - 2.5 = 7.1 \text{ V}$


The batteries have negligible internal resistance.

What is the potential difference between points P and Q?

- A 1.5V B 2.1V **C 7.1V** D 12.1V

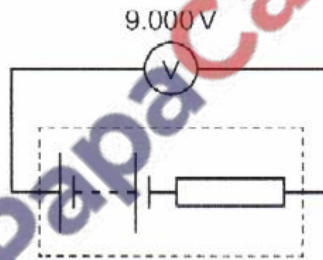
22. Nov/2022/Paper_13/No.34

A voltmeter reads 9.000 V when it is connected across the terminals of a battery.



When a resistor of resistance 11.0Ω is connected in parallel with the battery, the voltmeter reading changes to 8.800 V.

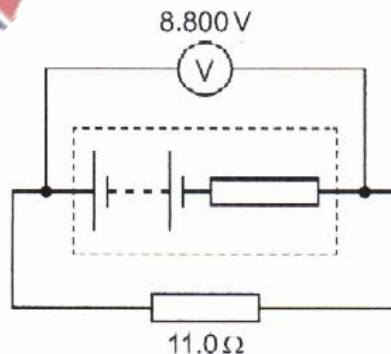$\text{E.m.f} = 9.0 \text{ V}$
 $E = IR + Ir$
 $IR = V$
 $E = V + Ir$
 $\therefore V = 8.8 \text{ V}$



Calculate I in circuit

$$I = \frac{V}{R}$$

$$= \frac{8.8}{11} = 0.8 \text{ A}$$

$$E = V + Ir$$

$$Ir = E - V$$

$$= 9 - 8.8$$

$$= 0.2 \text{ V}$$


$$r = \frac{V}{I} = \frac{0.2}{0.8}$$

$$= 0.25 \Omega$$

What is the internal resistance of the battery?

- A 0.244Ω **B 0.250Ω** C 10.8Ω D 11.3Ω

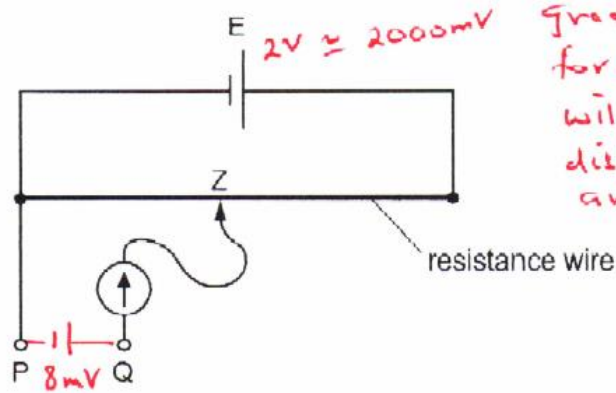A cell E, of electromotive force (e.m.f.) 2V and negligible internal resistance, is connected to a uniform resistance wire of resistance $10\ \Omega$ and length 1.0 m.



Since 2000mV is much greater than 8mV, for balance point will be a very small distance on the wire and difficult to measure precisely.

Z is a connection that may be made at any position along the resistance wire. A galvanometer is connected between Z and a point Q.

A new source of e.m.f. of approximately 8mV is connected between points P and Q. The e.m.f. of the new source is determined by changing the position of Z until the reading on the galvanometer is zero.

Which change to the circuit allows a much more precise value for the e.m.f. of the new source to be obtained?


- A Add a resistor of resistance $0.1\ \Omega$ in series with cell E.
- B Add a resistor of resistance $1000\ \Omega$ in series with cell E.
- C Add a resistor of resistance $10\ \Omega$ in series with the new source.
- D Add a resistor of resistance $800\ \Omega$ in series with the new source.

Adding a $1000\ \Omega$ in series with cell E will reduce the voltage 2000mV closer to 8mV, hence comparable. — So distance will be larger on the wire to measure precisely.

- (a) State Ohm's law. $R = \frac{V}{I}$ $V = IR$ $V \propto I$, $R = \text{constant}$.

Current through a conductor is directly proportional to potential difference across it provided temperature remains constant. [2]

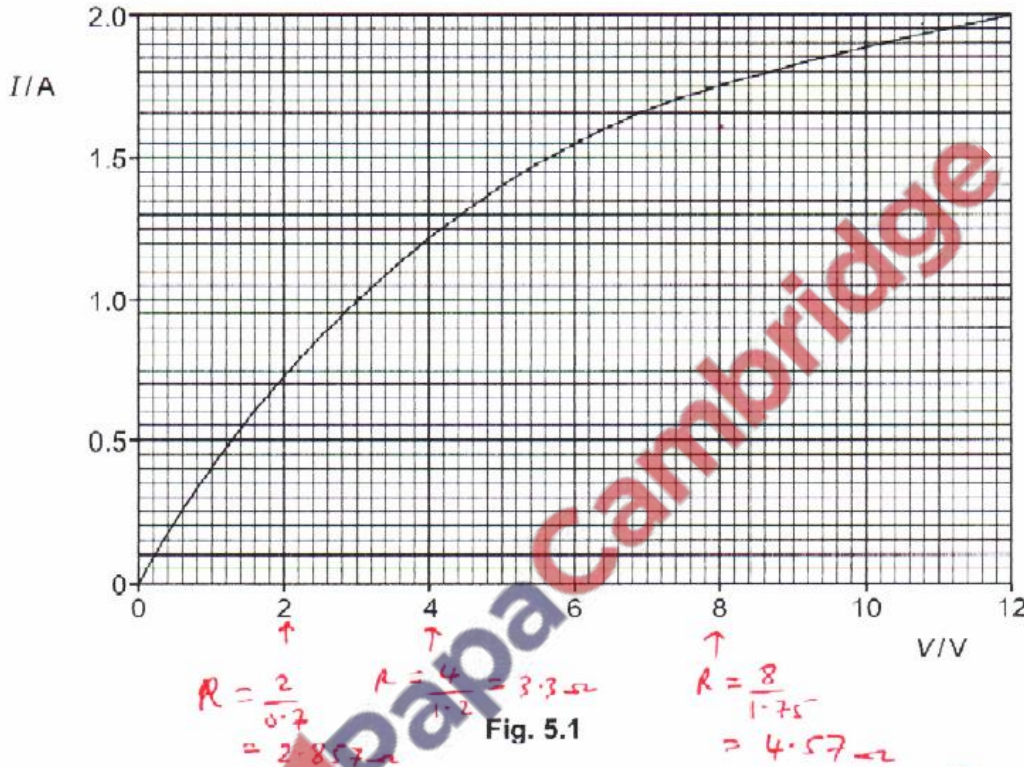- (b) The variation of current I with potential difference V for a filament lamp is shown in Fig. 5.1.



The resistance of the filament lamp increases with potential difference. $R = \frac{V}{I}$

- (i) State how Fig. 5.1 shows this.
 - The ratio of V/I increases as p.d increases.
 - $\frac{V}{I} = \text{Resistance}$ [1]

- (ii) Explain why the resistance varies in this way.
 - As p.d increase, current increases as well.
 - This causes temperature to increase [1]
 - Resistance will increase when temperature increases.

- (c) Fig. 5.2 shows a circuit with a battery of electromotive force (e.m.f.) 12.0V connected to a linear potentiometer AB and two identical filament lamps P and Q.

↑
divide p.d
btw the 2
lamps


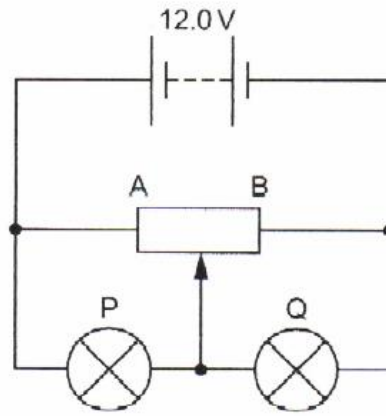


Fig. 5.2

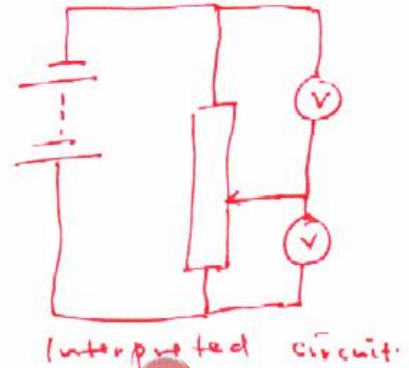

The battery has negligible internal resistance and the lamps each have the same I - V characteristic shown in Fig. 5.1.

When the slider of the potentiometer is at its midpoint, as shown in Fig. 5.2, the current I in the battery is 1.78A.

Determine:

- (i) the current in lamp P

At midpoint p.d across potentiometer = 6V.

At p.d = 6.0V, the current, $I = 1.55$ A

current = 1.55 A [1]

- (ii) the total power dissipated in lamps P and Q

$$P = V \times I$$

$$= (6 \times 1.55) \times 2 \text{ (two lamps P \& Q).}$$

$$= 19 \text{ W}$$

total power = 19 W [2]

- (iii) the resistance of the potentiometer between its ends A and B.

$$I = 1.78 - 1.55$$

$$= 0.23 \text{ A}$$

$$R = \frac{12 \text{ V}}{0.23 \text{ A}} = 52 \Omega$$

$$R = \frac{V}{I}$$

Voltage across the potentiometer = 12V from end A to B.

resistance = 52 Ω [2]

(d) The slider of the potentiometer in (c) is moved to end A.


State and explain the effect on the brightness of lamps P and Q.

lamp P: p.d across the lamp decreases to zero, so
..... the lamp will go off.

lamp Q: p.d across the lamp increases to 12V
..... so lamp get brighter.

[2]

[Total: 11]

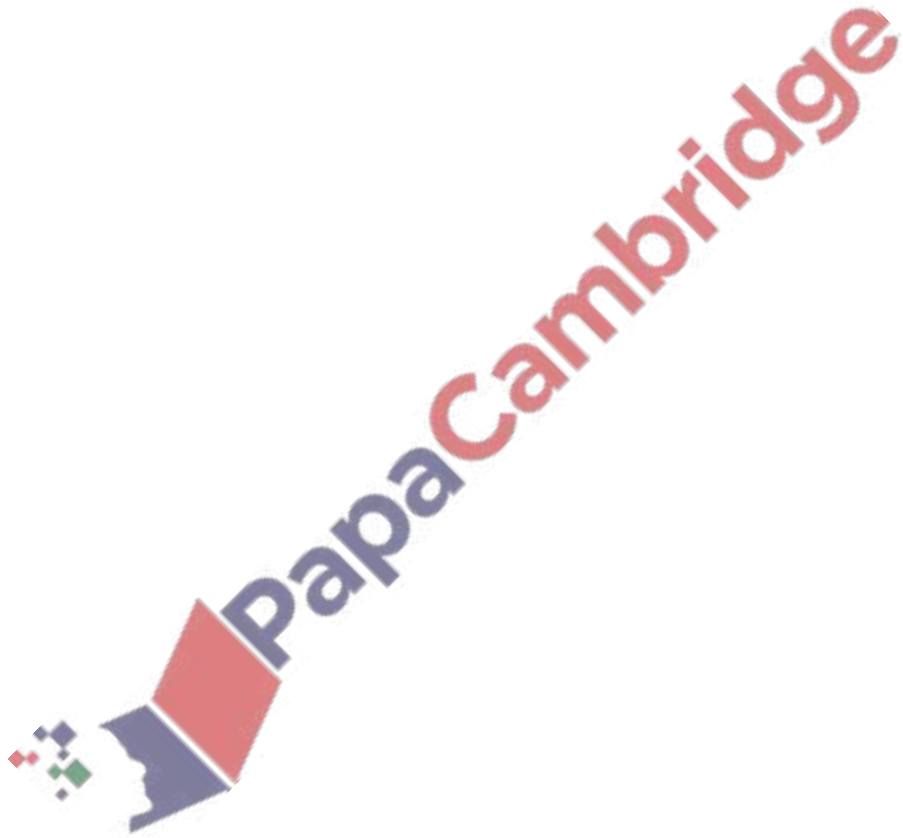

- (a) Define electric potential difference.

Is energy transferred per unit charge from electrical to other forms of energy. [1]

- (b) A battery is connected to two resistors X and Y, as shown in Fig. 6.1.

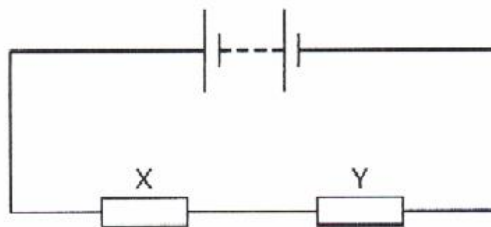


Fig. 6.1

The resistance of resistor X is greater than the resistance of resistor Y.

State and explain which resistor dissipates more power.

- $R_x > R_y$
- Both resistors are in series, so same current flow through both.
 - Power = $I^2 R$, and since R_x is greater than R_y , then more power will be dissipated on resistor X.
- [3]

- (c) A battery of electromotive force (e.m.f.) 9.0V and internal resistance
- r
- is connected to two resistors P and Q, as shown in Fig. 6.2.

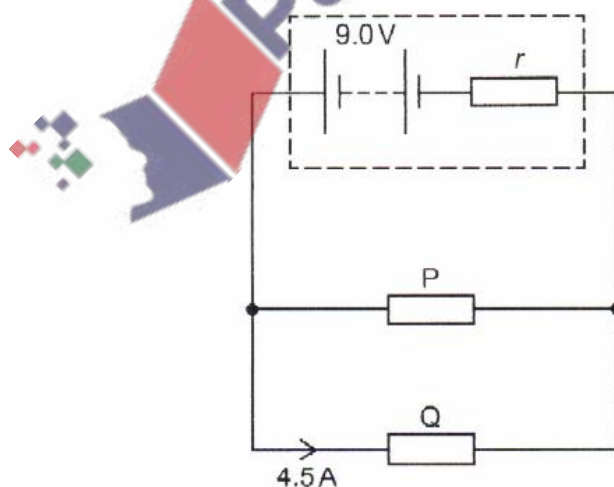


Fig. 6.2

A total charge of 650 C moves through resistor P in a time interval of 540 s. During this time resistor P dissipates 4800 J of energy. The current in resistor Q is 4.5 A. Assume that the e.m.f. of the battery remains constant.

Calculate:

- (i) the current in resistor P

$$I = \frac{Q}{t}$$

$$= \frac{650 \text{ C}}{540 \text{ s}}$$

$$= 1.2 \text{ A}$$

current = 1.2 A [2]

- (ii) the potential difference across resistor P

$$\text{Voltage} = \frac{\text{Energy}}{\text{charge}}$$

$$= \frac{4800 \text{ J}}{650 \text{ C}}$$

$$= 7.3846$$

$$\approx \underline{7.4 \text{ V}}$$

potential difference = 7.4 V [2]

- (iii) the internal resistance r of the battery.

Find current, I through the cell

$$\text{External} = 4.5 \text{ A} + 1.2$$

$$= 5.7 \text{ A}$$

$$E = I(R + r)$$

$$E = IR + Ir$$

$r =$ 0.28 Ω [2]

[Total: 10]

but $IR = V = 7.4$

$$9.0 = 7.4 + (5.7 \times r)$$

$$5.7r = 9.0 - 7.4$$

$$= 1.6$$

$$r = \frac{1.6}{5.7} = 0.2807$$

$$\approx \underline{\underline{0.28 \Omega}}$$

(a) State Kirchhoff's second law.

In a closed loop the sum of emf's is equal to the sum of p.d's.
(or algebraic sum of emf's and p.d's is zero). [2]

(b) Three identical cells, each of electromotive force (e.m.f.) 1.5 V and internal resistance 590 mΩ, are connected in parallel across a conductor, as shown in Fig. 5.1.

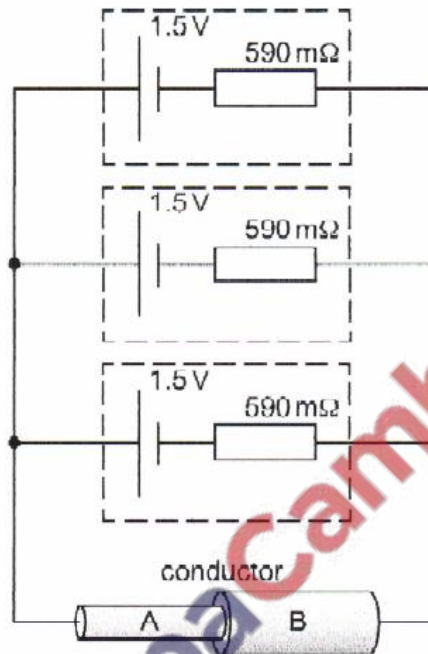


Fig. 5.1

The conductor is composed of two cylindrical sections A and B.
The total resistance of the circuit is 2.2 Ω.

(i) Show that the resistance of the conductor is 2.0 Ω.

$$\frac{1}{r_T} = \frac{1}{590} + \frac{1}{590} + \frac{1}{590}$$

$$= \frac{1}{0.59} + \frac{1}{0.59} + \frac{1}{0.59}$$

$$\frac{1}{r_T} = 5.0847$$

$$r_T = \frac{1}{5.0847}$$

$$= 0.1966$$

$$\approx 0.197 \Omega$$

$$590 \text{ m}\Omega = 590 \times 10^{-3} \Omega$$

$$= 0.59 \Omega$$

$$R_c = 2.2 - 0.197$$

$$= 2.0033$$

$$\approx \underline{\underline{2.0 \Omega}} \checkmark$$

[2]

(ii) Calculate the current in the conductor.

$$I = \frac{V}{R}$$

Cells in parallel give p.d equal to that of one cell.

$$= \frac{1.5}{2.2} = 0.68 \text{ A}$$

current = 0.68 A [2]

(c) The two cylindrical sections A and B of the conductor in Fig. 5.1 are made from the same material and have the same length.

The diameter of section A is 4.3 mm and the diameter of section B is 7.6 mm.

The resistance of section A is R_A and the resistance of section B is R_B .

(i) Calculate the ratio $\frac{R_A}{R_B}$.

$R = \frac{\rho L}{A}$
Same length and resistivity

$$\rho L = R A$$

$$R_A A_A = R_B A_B$$

$$\frac{R_A}{R_B} = \frac{A_B}{A_A}$$

$$A = \pi \left(\frac{d}{2}\right)^2$$

$$\therefore \frac{R_A}{R_B} = \frac{\pi \times \left(\frac{7.6}{2}\right)^2}{\pi \times \left(\frac{4.3}{2}\right)^2}$$

$$= 3.123$$

$$\approx 3.1$$

$\frac{R_A}{R_B} = \dots\dots\dots 3.1 \dots\dots\dots$ [3]

(ii) Calculate the ratio

$$\frac{\text{average drift speed of free electrons in section A}}{\text{average drift speed of free electrons in section B}}$$

Explain your reasoning.

$I = n A v q$
 $v = \frac{I}{n A q}$
but I, n, q are same in both sections
 $\Rightarrow v = \frac{K}{A}$

$$v_B A_B = K$$

$$\Rightarrow v_A A_A = v_B A_B$$

$$\frac{v_A}{v_B} = \frac{A_B}{A_A} = \frac{\pi \times \left(\frac{7.6}{2}\right)^2}{\pi \times \left(\frac{4.3}{2}\right)^2} = 3.1$$

$$v_A = \frac{K}{A_A}$$

$$v_A A_A = K$$

ratio = 3.1 [2]


(d) The circuit of Fig. 5.1 is altered by removing one of the cells.

State and explain the effect, if any, of this change on the potential difference across the conductor.

- The combined resistance of the two cell will be greater than previous 3 cells.
- There will be more lost volts (Ir) in the cells so the p-d across the resistor conductor will be less.

[3]

[Total: 14]

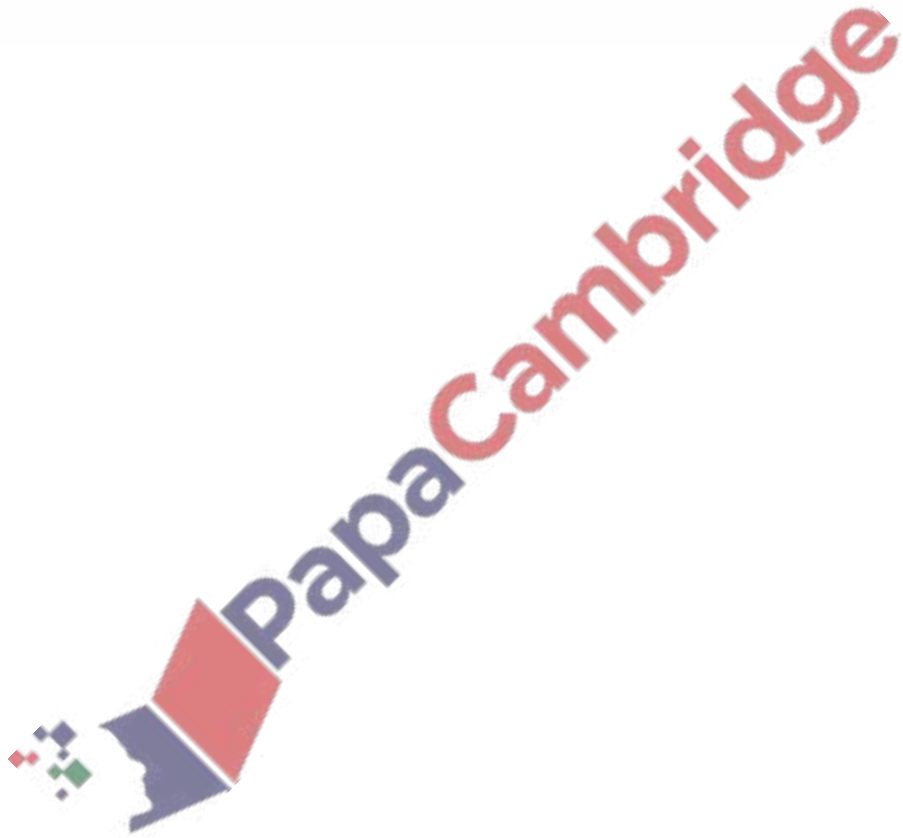

[2]