

1. Nov/2021/Paper_21/No.5

(a) State Kirchhoff's first law.

.....
.....
..... [2]

(b) The circuit shown in Fig. 5.1 contains a battery of electromotive force (e.m.f.) E and negligible internal resistance connected to four resistors R_1 , R_2 , R_3 and R_4 , each of resistance R .

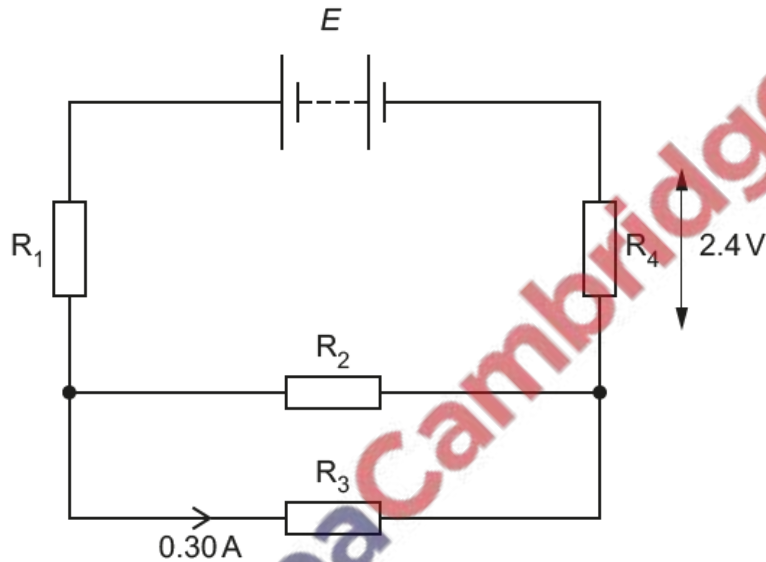


Fig. 5.1

The current in R_3 is 0.30 A and the potential difference (p.d.) across R_4 is 2.4 V .

(i) Show that R is equal to $4.0\ \Omega$.



[2]

(ii) Determine the e.m.f. E of the battery.

$E = \dots\dots\dots\text{ V}$ [2]

- (c) The battery in (b) is replaced with another battery of the same e.m.f. E but with an internal resistance that is not negligible.

State and explain the change, if any, in the total power produced by the battery.


.....
.....
..... [2]

- (d) The resistors in the circuit of Fig. 5.1 are made from nichrome wire of uniform radius $240\ \mu\text{m}$. The length of this wire needed to make each resistor is $0.67\ \text{m}$.

Calculate the resistivity of nichrome.

resistivity = $\Omega\ \text{m}$ [3]

[Total: 11]

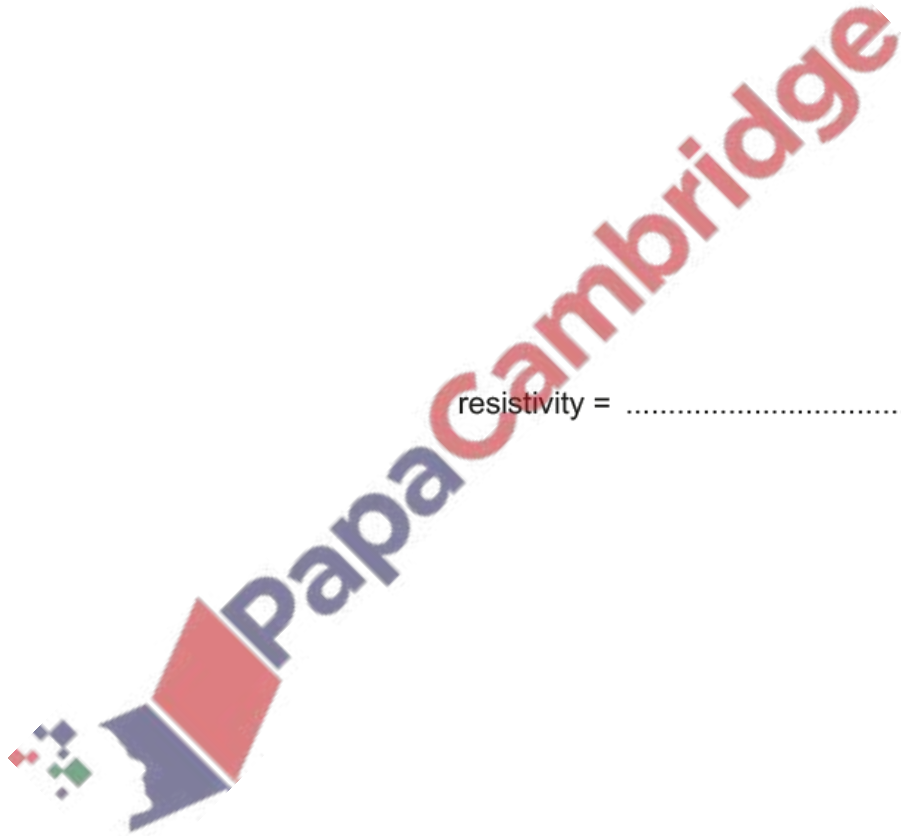

A cell of electromotive force (e.m.f.) 0.48V is connected to a metal wire X, as shown in Fig. 6.1.

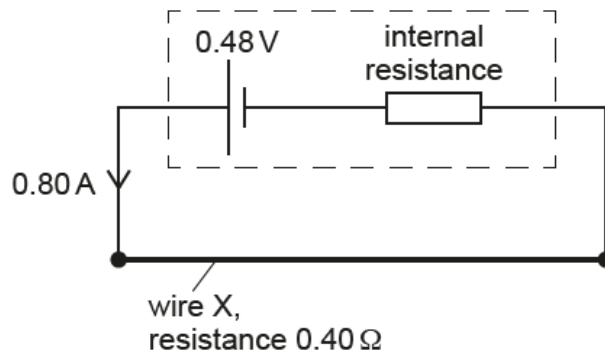


Fig. 6.1

The cell has internal resistance. The current in the cell is 0.80A.

Wire X has length 3.0m, cross-sectional area $1.3 \times 10^{-7} \text{ m}^2$ and resistance 0.40Ω .

(a) Calculate the charge passing through the cell in a time of 7.5 minutes.

charge = C [2]

(b) Calculate the percentage efficiency with which the cell supplies power to wire X.

efficiency = % [3]

(c) There are 3.2×10^{22} free (conduction) electrons contained in the volume of wire X.

For wire X, calculate:

(i) the number density n of the free electrons

$n = \dots\dots\dots \text{m}^{-3}$ [1]

(ii) the average drift speed of the free electrons.

average drift speed = $\dots\dots\dots \text{ms}^{-1}$ [2]

(d) A wire Y has the same cross-sectional area as wire X and is made of the same metal. Wire Y is longer than wire X.

Wire X in the circuit is now replaced by wire Y. Assume that wire Y has the same temperature as wire X.

State and explain whether the average drift speed of the free electrons in wire Y is greater than, the same as, or less than that in wire X.

.....
.....
.....
.....
.....
.....
.....
..... [3]

[Total: 11]

3. Nov/2021/Paper_23/No.6

- (a) A resistance wire of uniform cross-sectional area $3.3 \times 10^{-7} \text{ m}^2$ and length 2.0 m is made of metal of resistivity $5.0 \times 10^{-7} \Omega \text{ m}$.

Show that the resistance of the wire is 3.0Ω .

[2]

- (b) The ends of the resistance wire in (a) are connected to the terminals X and Y in the circuit shown in Fig. 6.1.

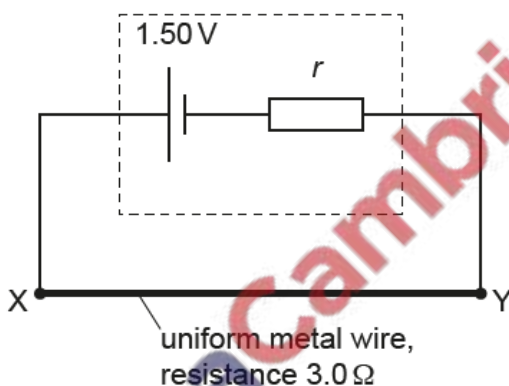


Fig. 6.1

The cell has an electromotive force (e.m.f.) of 1.50 V and internal resistance r . The potential difference between X and Y is 1.20 V.

Calculate:

- (i) the current in the circuit

current = A [1]

- (ii) the internal resistance r .

$r = \dots \dots \dots \Omega$ [2]

- (c) A galvanometer and a cell of e.m.f. E with negligible internal resistance are connected to the circuit in (b), as shown in Fig. 6.2.

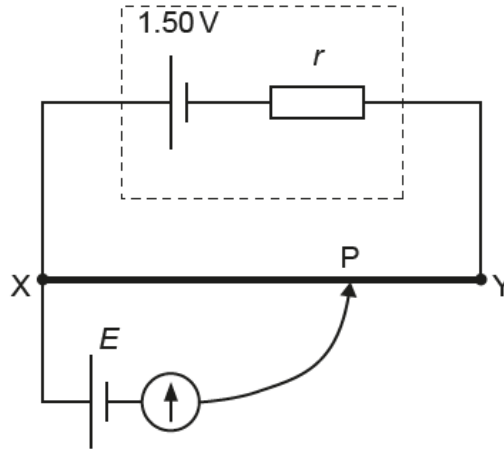


Fig. 6.2

The resistance wire between X and Y has a length of 2.0 m. The galvanometer has a reading of zero when the connection P is adjusted so that the length XP is 1.4 m.

Determine the e.m.f. E of the cell.

$E = \dots\dots\dots$ V [2]

- (d) The circuit in Fig. 6.2 is modified by replacing the original resistance wire with a second resistance wire. The second wire has the same length as the original wire and is made of the same metal.

The second wire has a smaller cross-sectional area than the original wire.

Connection P is adjusted on the second wire so that the galvanometer has a reading of zero.

State and explain whether length XP for the second wire is shorter than, longer than or the same as length XP for the original wire when the galvanometer reading is zero.

.....

.....

.....

.....

..... [3]

[Total:10]

(a) State Kirchhoff's second law.

.....

.....

..... [2]

(b) A battery has electromotive force (e.m.f.) 4.0V and internal resistance 0.35Ω. The battery is connected to a uniform resistance wire XY and a fixed resistor of resistance R, as shown in Fig. 5.1.

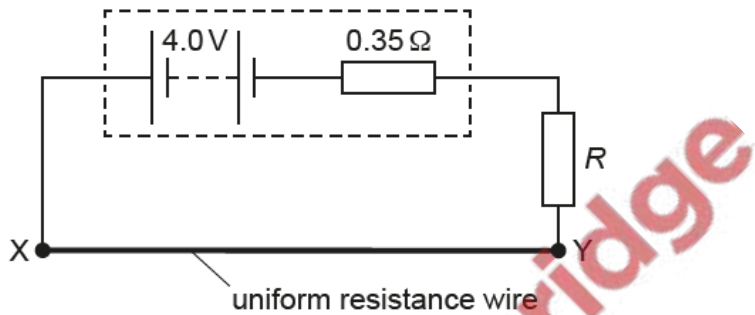


Fig. 5.1

Wire XY has resistance 0.90Ω. The potential difference across wire XY is 1.8V.

Calculate:

(i) the current in wire XY

current = A [1]

(ii) the number of free electrons that pass a point in the battery in a time of 45 s

number = [2]

(iii) resistance R.

R = Ω [2]

(c) A cell of e.m.f. 1.2V is connected to the circuit in (b), as shown in Fig. 5.2.

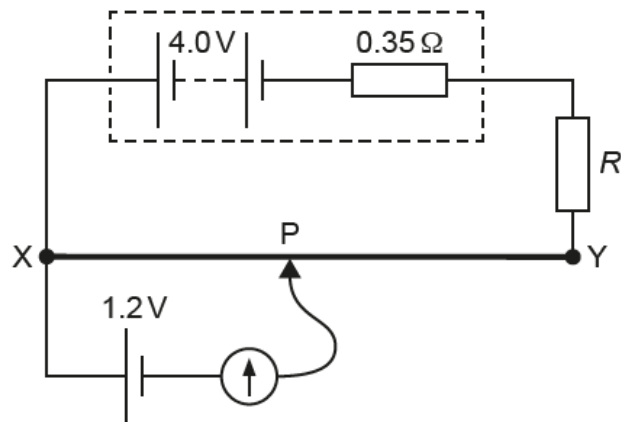


Fig. 5.2

The connection P is moved along the wire XY. The galvanometer reading is zero when distance XP is 0.30 m.

(i) Calculate the total length L of wire XY.

$L = \dots\dots\dots$ m [2]

(ii) The fixed resistor is replaced by a different fixed resistor of resistance greater than R .

State and explain the change, if any, that must be made to the position of P on wire XY so that the galvanometer reading is zero.

.....

.....

.....

..... [2]

[Total: 11]

(a) Define the *ohm*.

.....
 [1]

(b) A wire is made of metal of resistivity ρ . The length L of the wire is gradually increased. Assume that the volume V of the wire remains constant as its length is increased.

Show that the resistance R of the extending wire is proportional to L^2 .

[2]

(c) A battery of electromotive force (e.m.f.) E and internal resistance r is connected to a variable resistor of resistance R , as shown in Fig. 5.1.

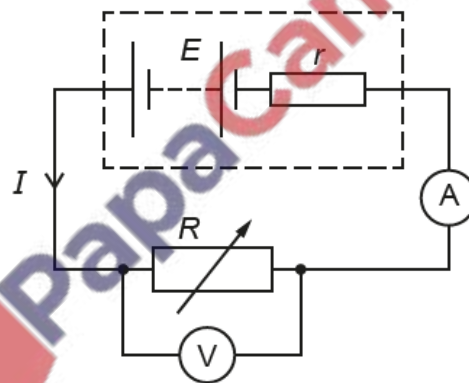


Fig. 5.1

An ammeter measures the current I in the circuit. A voltmeter measures the potential difference V across the variable resistor.

The resistance R is now varied to change the values of I and V .

The variation with I of V is shown in Fig. 5.2.

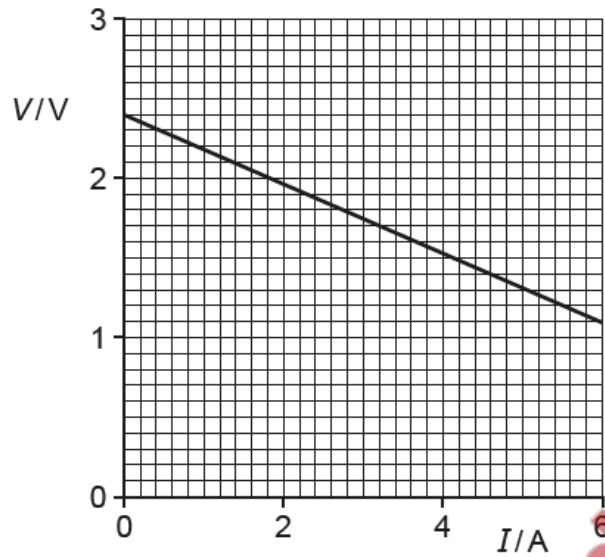


Fig. 5.2

(i) Use Fig. 5.2 to state the e.m.f. E of the battery.

$E = \dots\dots\dots$ V [1]

(ii) Use Fig. 5.2 to determine the power dissipated in the variable resistor when there is a current of 5.0A.

power = $\dots\dots\dots$ W [3]

(iii) State what is represented by the value of the gradient of the graph.

$\dots\dots\dots$ [1]

[Total: 8]

(a) Define the *electromotive force (e.m.f.)* of a source.

.....

.....

..... [2]

(b) The circuit shown in Fig. 5.1 contains a battery of e.m.f. E that has internal resistance r , a variable resistor, a voltmeter and an ammeter.

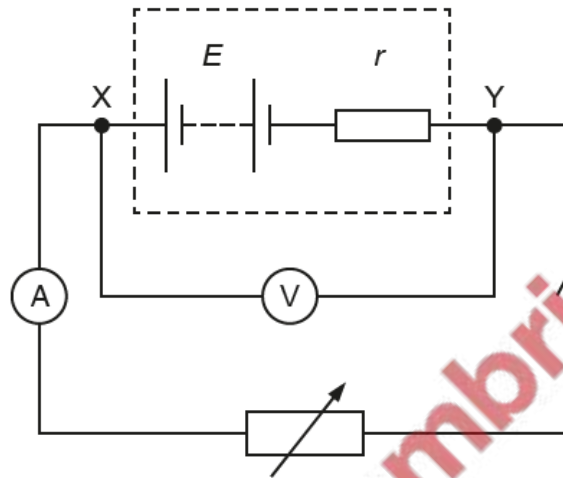


Fig. 5.1

Readings from the two meters are taken for different settings of the variable resistor. The variation with current I of the potential difference (p.d.) V across the terminals XY of the battery is shown in Fig. 5.2.

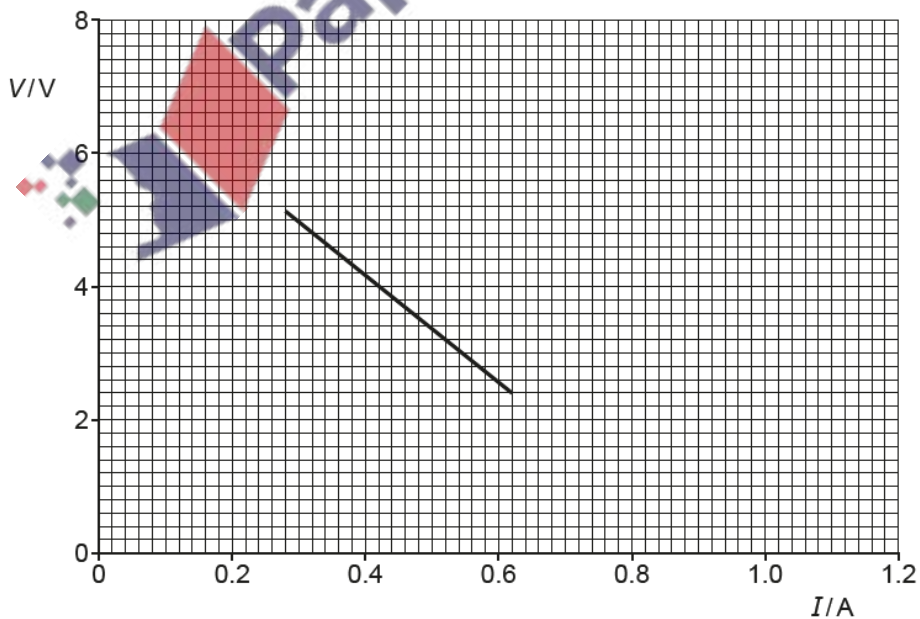


Fig. 5.2

Explain why V is not constant.

.....
.....
.....
..... [3]

(c) For the battery in (b), use Fig. 5.2 to determine:

(i) the e.m.f. E

$E =$ V [1]

(ii) the maximum current that the battery can supply

maximum current = A [1]

(iii) the internal resistance r .

$r =$ Ω [2]

(d) On Fig. 5.2, sketch a line to show a possible variation with I of V for a battery with a lower e.m.f. and a lower internal resistance than the battery in (b). Your line should extend over at least the same range of currents as the original line. [2]

[Total: 11]

(a) State Kirchoff's first law.

.....
 [1]

(b) A battery of electromotive force (e.m.f.) 12.0V and internal resistance r is connected to a filament lamp and a resistor, as shown in Fig. 6.1.

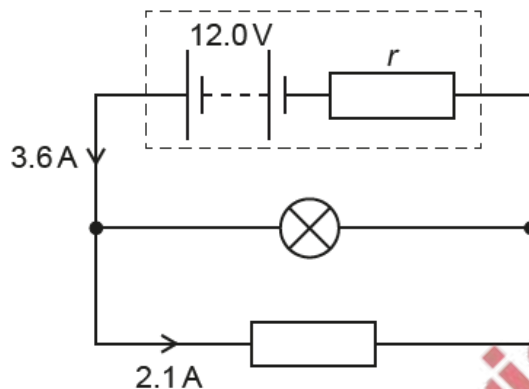


Fig. 6.1

The current in the battery is 3.6A and the current in the resistor is 2.1A. The I - V characteristic for the lamp is shown in Fig. 6.2.

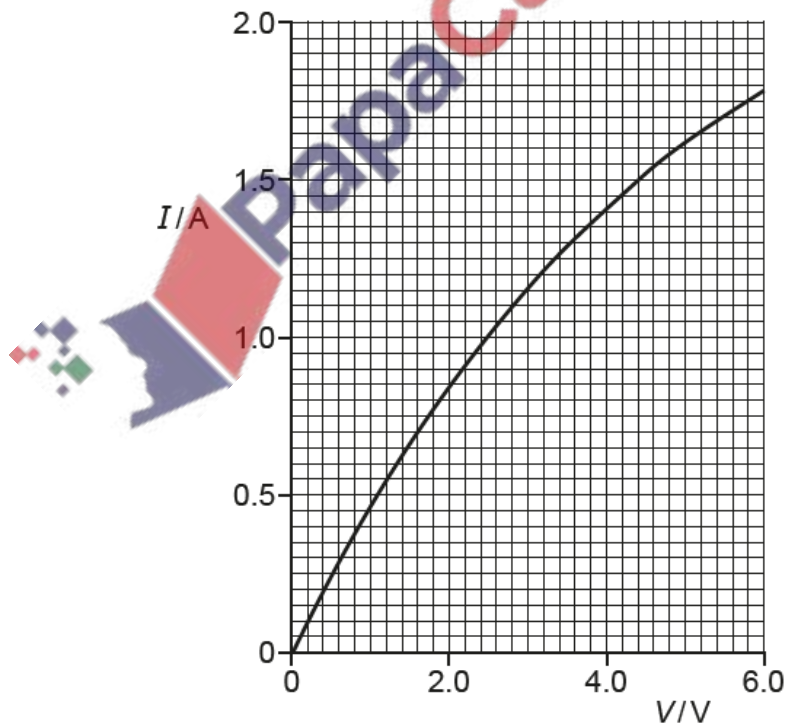


Fig. 6.2

(i) Determine the resistance of the lamp in Fig. 6.1.

resistance = Ω [3]


(ii) Determine the internal resistance r of the battery.

$r =$ Ω [2]

(iii) The initial energy stored in the battery is 470 kJ. Assume that the e.m.f. and the current in the battery do not change with time.

Calculate the time taken for the energy stored in the battery to become 240 kJ.

time = s [2]

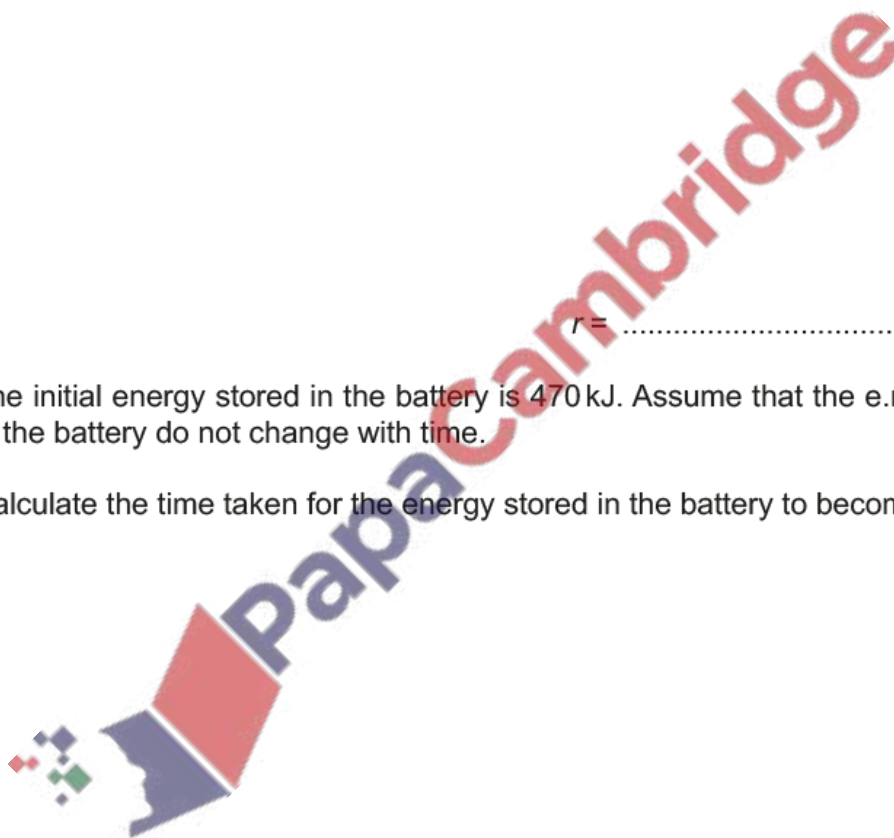

- (iv) The filament wire of the lamp is connected in series with the adjacent copper connecting wire of the circuit, as illustrated in Fig. 6.3.

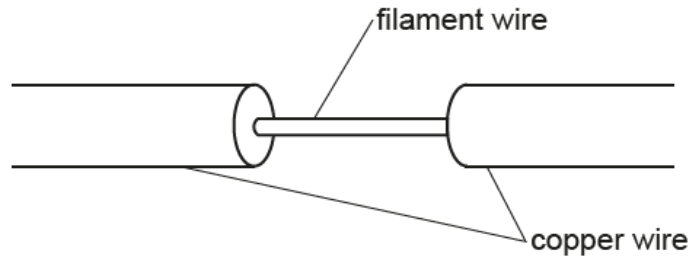


Fig. 6.3 (not to scale)


Some data for the filament wire and the adjacent copper connecting wire are given in Table 6.1.

Table 6.1

	filament wire	copper wire
cross-sectional area	A	$360A$
number density of free electrons	n	$2.5n$

Calculate the ratio
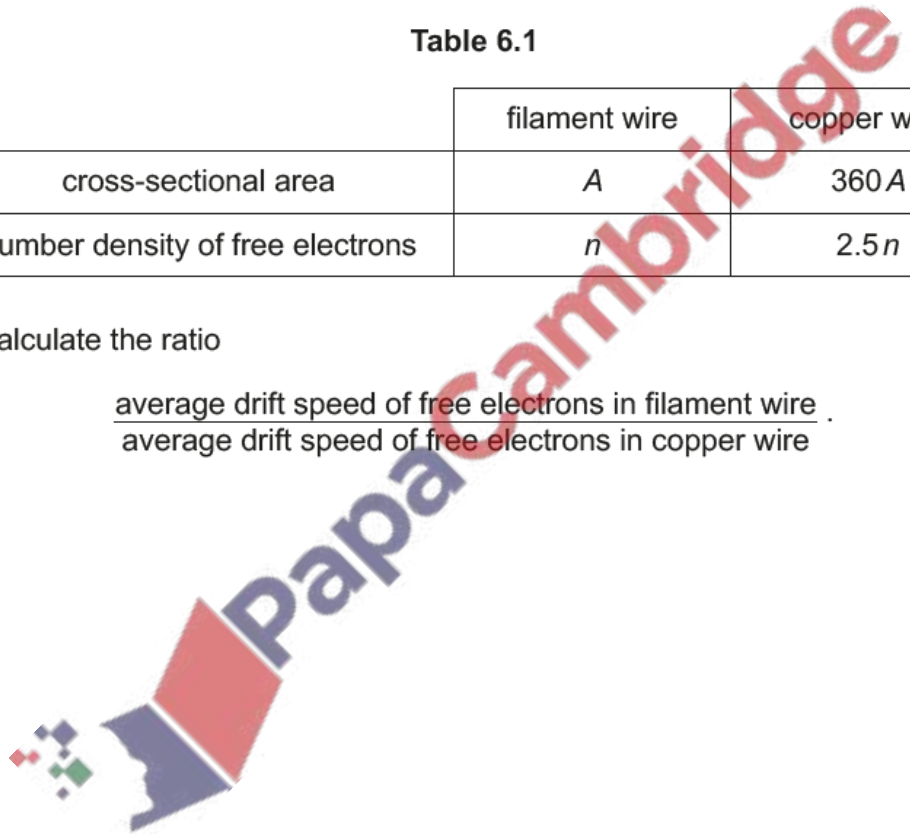
$$\frac{\text{average drift speed of free electrons in filament wire}}{\text{average drift speed of free electrons in copper wire}}$$



ratio = [2]

[Total: 10]