

Capacitance – 2020 A2

1. Nov/2020/Paper_41/No.6

- (a) (i) Define the *capacitance* of a parallel plate capacitor.

.....
.....
..... [2]

- (ii) State **three** functions of capacitors in electrical circuits.

1.
2.
3. [3]

- (b) A student has available four capacitors, each of capacitance $24 \mu\text{F}$.

The capacitors are connected as shown in Fig. 6.1.

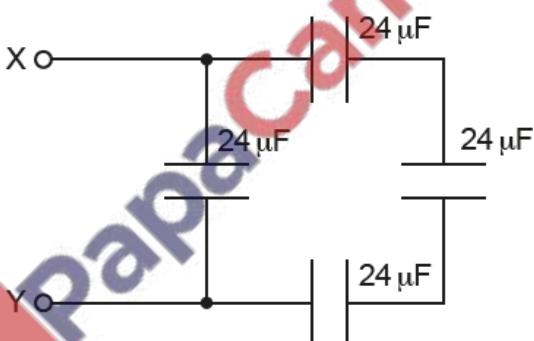


Fig. 6.1

Calculate the combined capacitance between the terminals X and Y.

capacitance = μF [2]

[Total: 7]

2. Nov/2020/Paper_42/No.6

- (a) (i) Define the *capacitance* of a parallel plate capacitor.

.....
.....
..... [2]

- (ii) State **three** functions of capacitors in electrical circuits.

1.
2.
3. [3]

- (b) A student has available **three** capacitors, each of capacitance $12\mu\text{F}$.

Draw diagrams, one in each case, to show how the student connects the capacitors to give a combined capacitance between the terminals of:

- (i) $18\mu\text{F}$



[1]

- (ii) $8\mu\text{F}$



[1]

[Total: 7]