


1. **Nov/2021/Paper\_41/No.7**

(a) State **two** properties of an ideal operational amplifier (op-amp).

1. ....
- .....
2. ....
- .....

[2]

(b) Fig. 7.1 shows a circuit that includes an ideal op-amp and two identical resistors R.

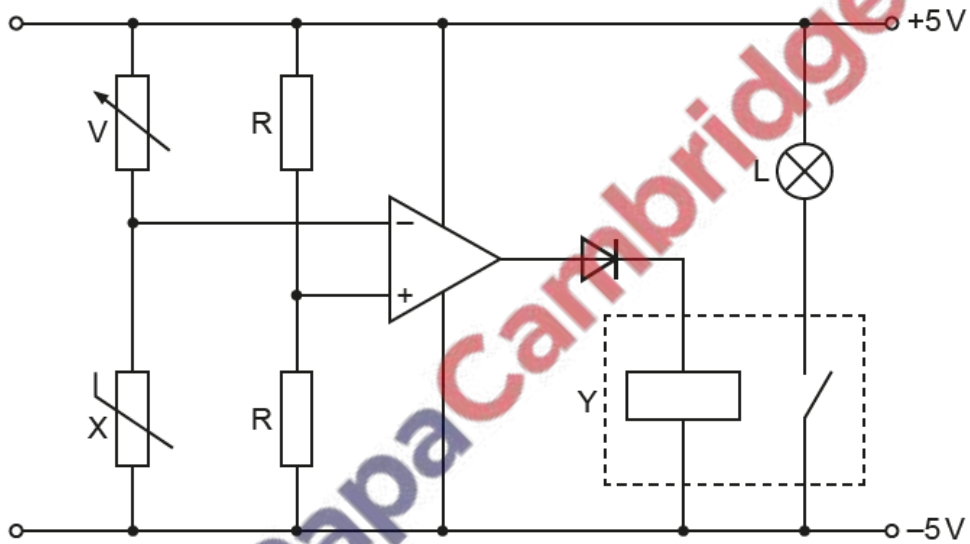

**Fig. 7.1**

State the names of components X and Y.

X: ..... Y: ..... [1]

(c) (i) Explain why the op-amp in Fig. 7.1 has only two possible output states.

- .....
- .....
- .....
- ..... [2]

(ii) State the name of the type of op-amp circuit in which the op-amp behaves as in (c)(i).

..... [1]


(iii) Describe the environmental condition under which the lamp L in Fig. 7.1 will light.

.....  
.....  
..... [2]

(iv) Suggest the purpose of the variable resistor V in the circuit.

.....  
..... [1]

[Total: 9]

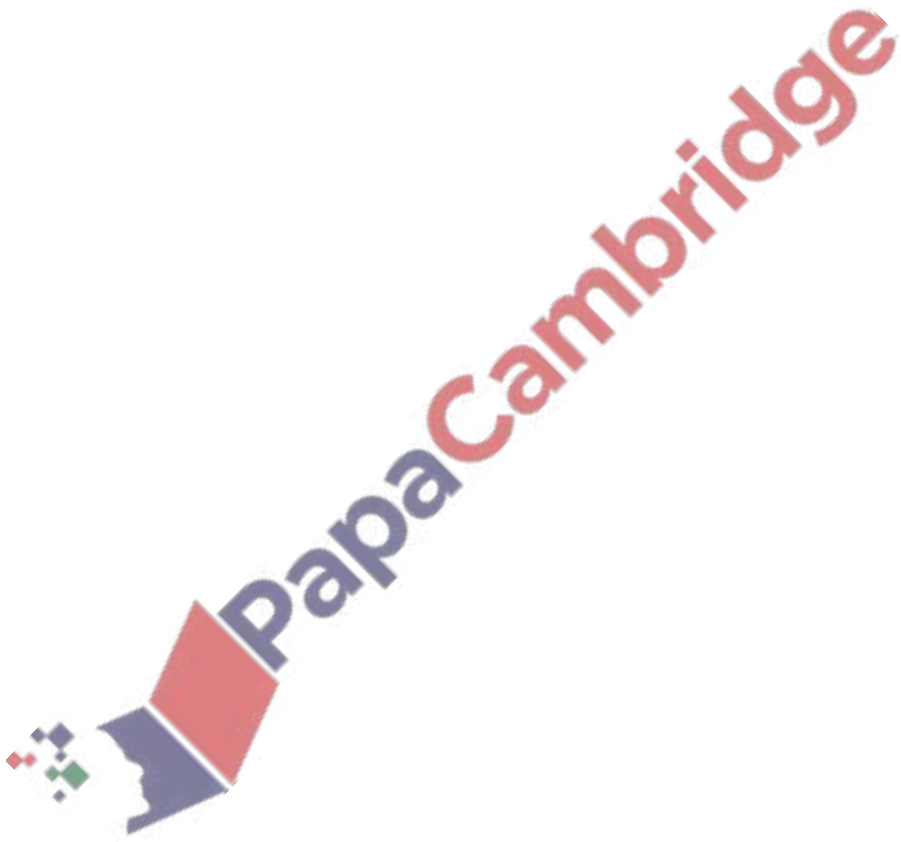

(a) An operational amplifier (op-amp) has two input terminals and one output terminal.

State what is meant by the *gain* of an op-amp.

.....  
 .....  
 ..... [2]

(b) State **two** effects of negative feedback on the gain of an amplifier circuit that uses an op-amp.

1. ....  
 .....  
 2. ....  
 ..... [2]

(c) Fig. 7.1 shows an op-amp circuit that uses negative feedback.

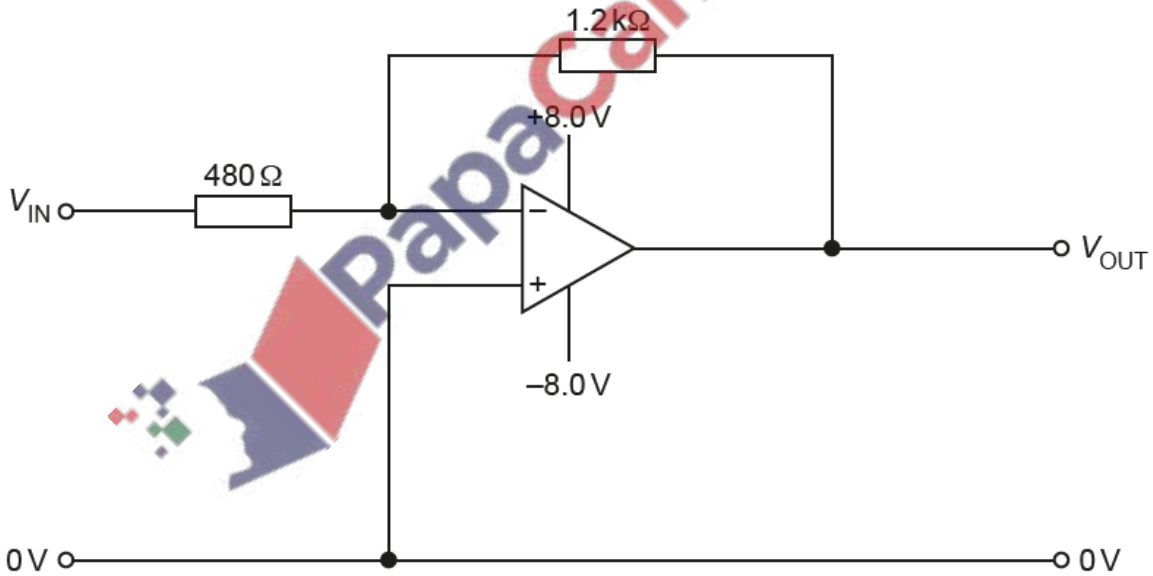


Fig. 7.1

(i) State the name of the type of circuit shown in Fig. 7.1.

..... [1]

(ii) On Fig. 7.1, label with the letter X a point in the circuit that is considered to be a virtual earth. [1]

(iii) Calculate the gain of the circuit in Fig. 7.1.

gain = ..... [2]


(iv) Determine the value of  $V_{IN}$  when  $V_{OUT}$  is +6.5V.

$V_{IN}$  = .....V [1]

(v) Determine the value of  $V_{OUT}$  when  $V_{IN}$  is -5.4V.

$V_{OUT}$  = .....V [1]

[Total: 10]

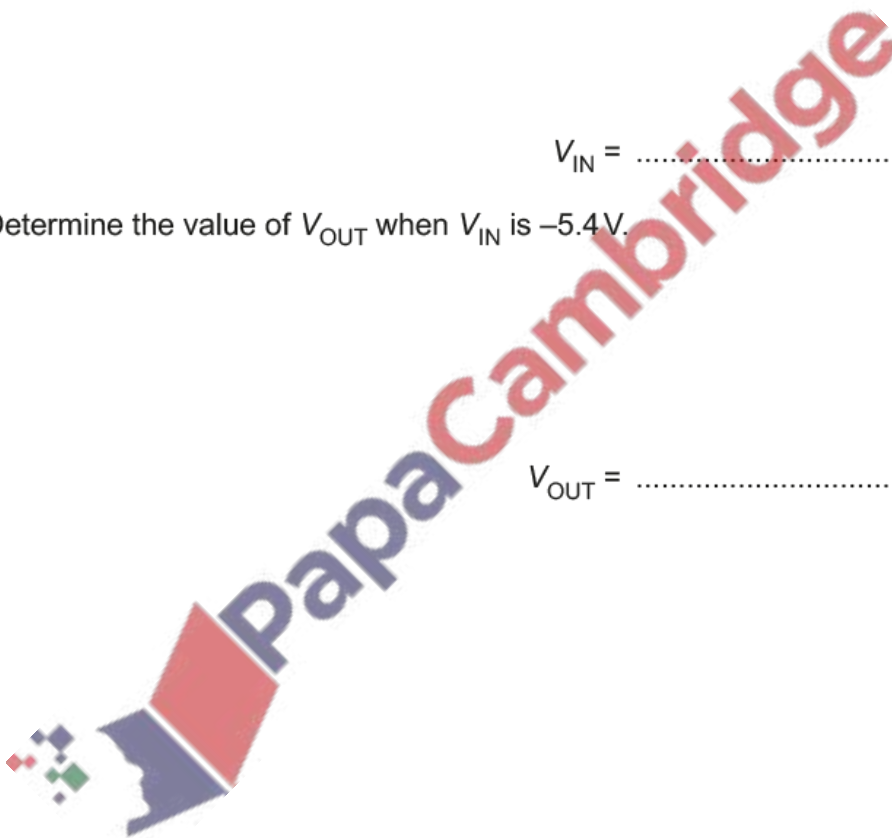

The variation with temperature of the resistance of a thermistor is shown in Fig. 8.1.

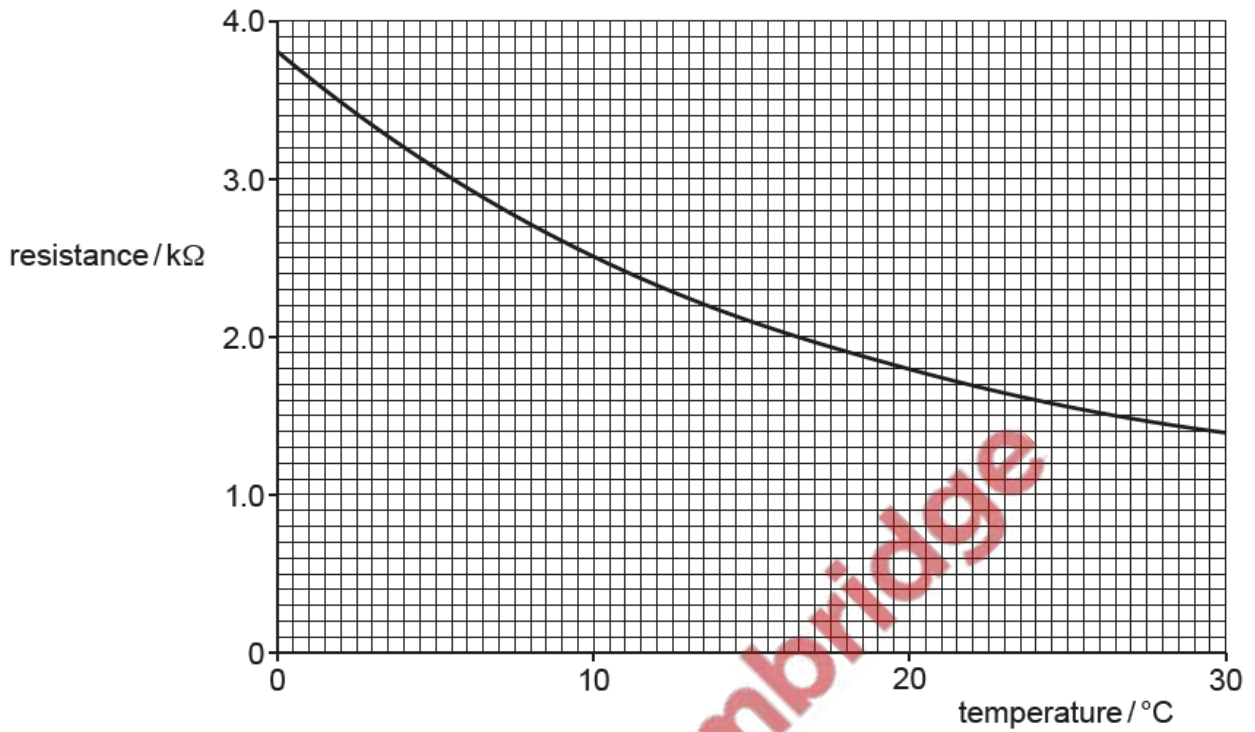


Fig. 8.1

A student includes the thermistor and an ideal operational amplifier (op-amp) in the circuit of Fig. 8.2.

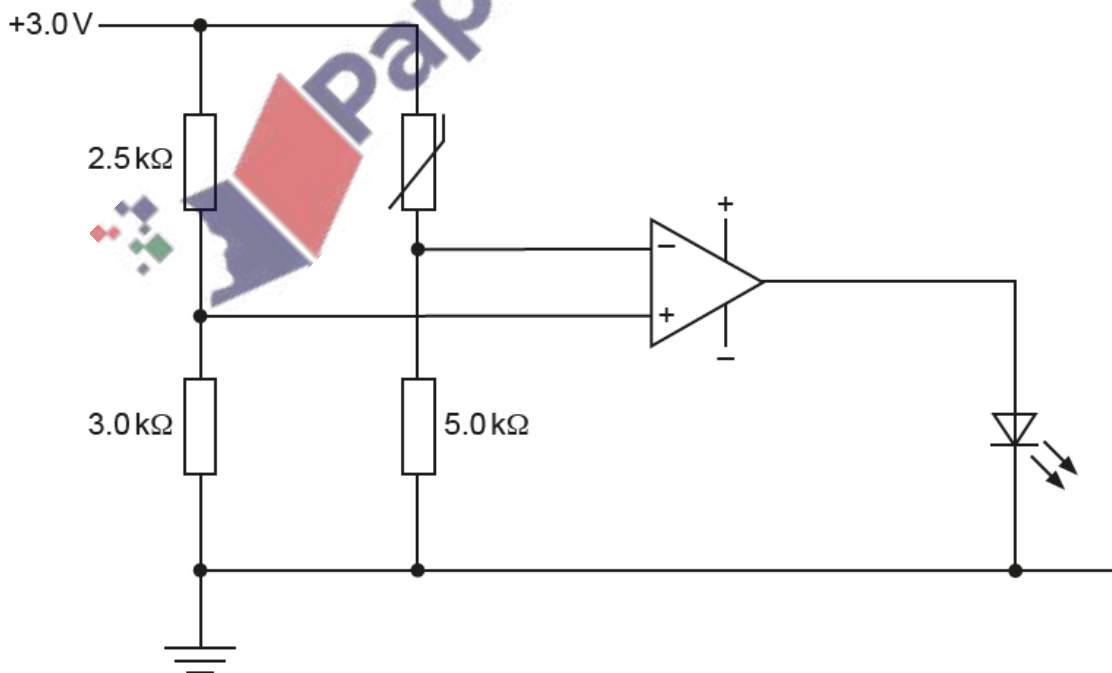


Fig. 8.2

(a) Calculate the potential  $V^+$  at the non-inverting input of the op-amp.

$V^+ = \dots\dots\dots$  V [2]

(b) At  $10^\circ\text{C}$ , the resistance of the thermistor is  $2.5\text{k}\Omega$ .

State and explain whether the light-emitting diode (LED) is emitting light.

.....  
.....  
..... [2]

(c) Explain why the student's circuit will not indicate any change in temperature above  $0^\circ\text{C}$ .

.....  
.....  
..... [2]

(d) The resistor of resistance  $5.0\text{k}\Omega$  is changed to a resistor of resistance  $R$  so that the LED switches on or off at a temperature of  $20^\circ\text{C}$ .

Determine  $R$  in  $\text{k}\Omega$ .

$R = \dots\dots\dots$   $\text{k}\Omega$  [3]

[Total: 9]

- (a) Two properties of an ideal operational amplifier (op-amp) are infinite input impedance and infinite bandwidth.

State what is meant by:

- (i) *infinite input impedance*

.....  
 ..... [1]

- (ii) *infinite bandwidth.*

.....  
 ..... [1]

- (b) A student uses a negative temperature coefficient thermistor in the circuit of Fig. 7.1 to indicate changes in temperature.

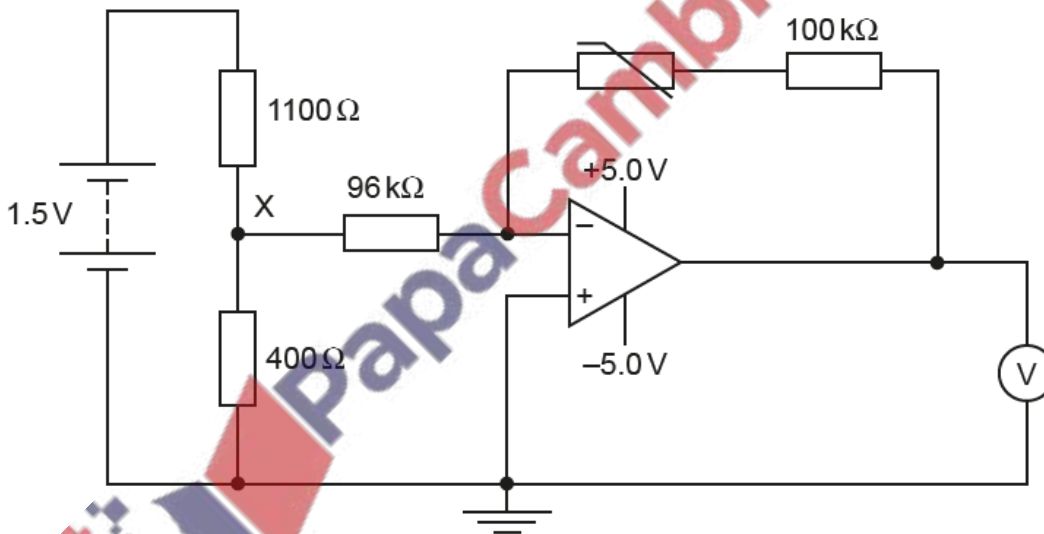


Fig. 7.1

- (i) Show that the potential at point X is 0.40V.

[1]

(ii) The thermistor has a resistance of  $360\text{ k}\Omega$  at a particular temperature.

For this temperature of the thermistor, calculate the magnitude of the reading on the voltmeter.

voltmeter reading = ..... V [3]

(iii) The temperature of the thermistor increases.

State and explain the effect of this change on the magnitude of the reading on the voltmeter.

.....  
.....  
..... [2]

(iv) Explain why the amplifier circuit will no longer indicate temperature changes when the magnitude of the gain of the circuit is greater than 12.5.

.....  
..... [1]

[Total: 9]





(a) Fig. 7.1 shows the circuit diagram containing an operational amplifier (op-amp).


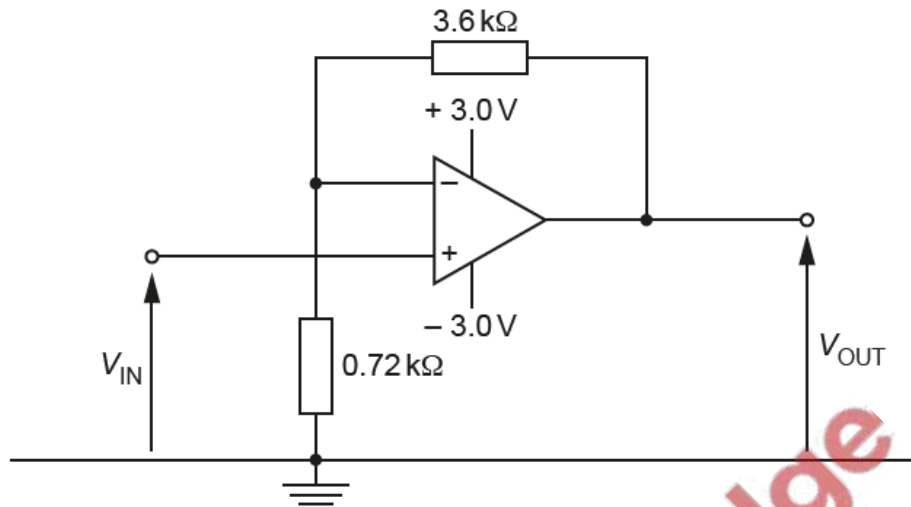


Fig. 7.1

(i) State the name of this type of amplifier.

..... [1]

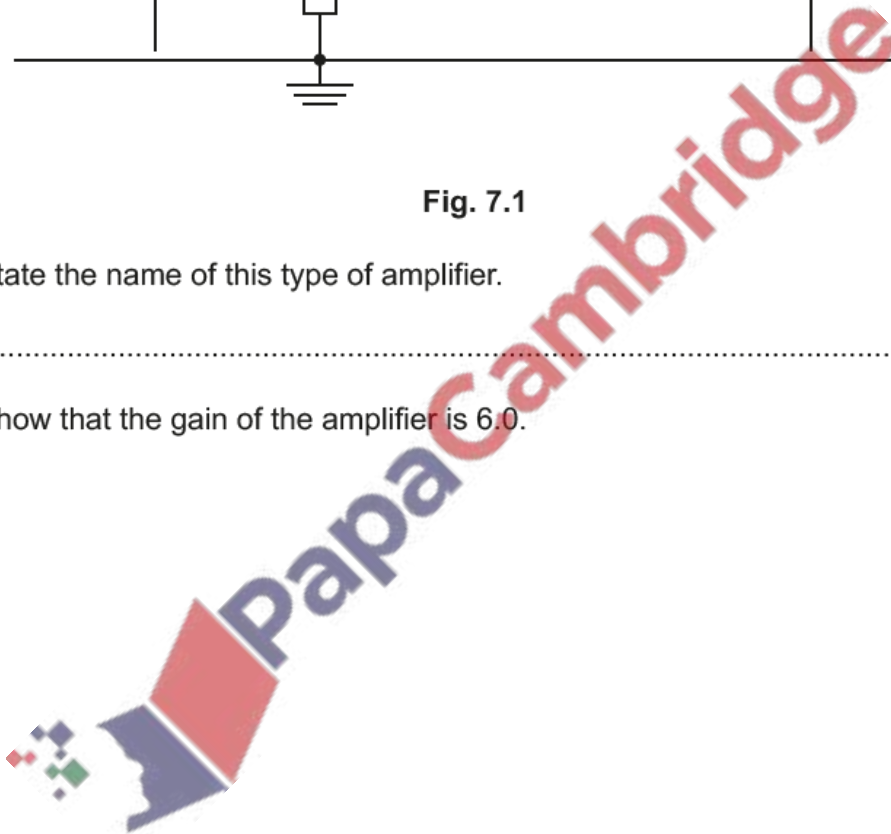(ii) Show that the gain of the amplifier is 6.0.



[1]

- (iii) At time  $t = 0$  the input potential  $V_{IN}$  is zero.  $V_{IN}$  then gradually increases with time  $t$  as shown in Fig. 7.2.

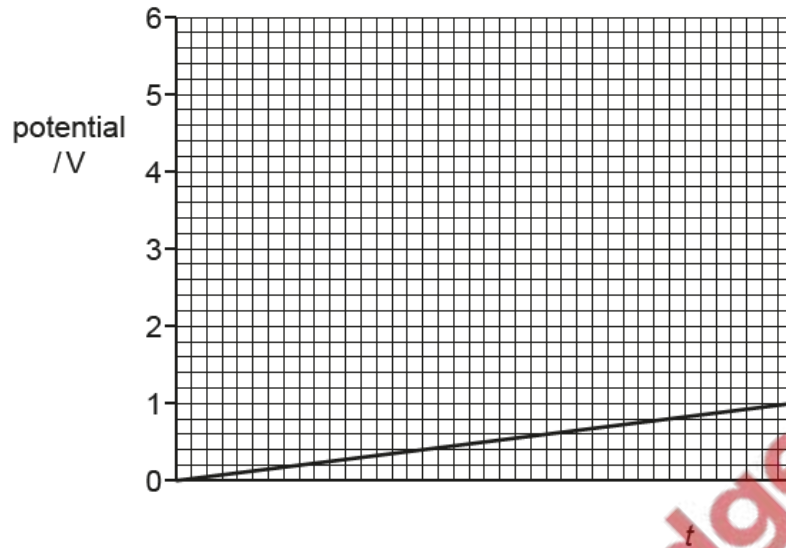


Fig. 7.2

On Fig. 7.2 sketch a line to show the variation with time  $t$  of the output potential  $V_{OUT}$  from time  $t = 0$  to time  $t = T$ . [2]

- (iv) State how the circuit of Fig. 7.1 may be changed so that the gain of the amplifier is dependent on light intensity.

..... [1]

(b) An op-amp is to be used to switch on a high-voltage heater.

- (i) State the name of the component used as the output device of the op-amp.

..... [1]

- (ii) Complete Fig. 7.3 using the device named in (i) and a diode so that the heater may be switched on when the output of the op-amp is positive.

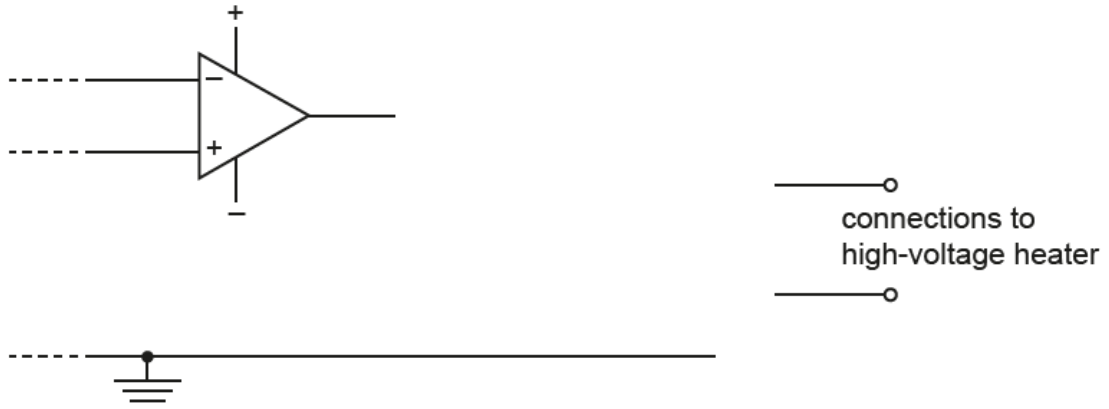


Fig. 7.3

[3]

[Total: 9]

