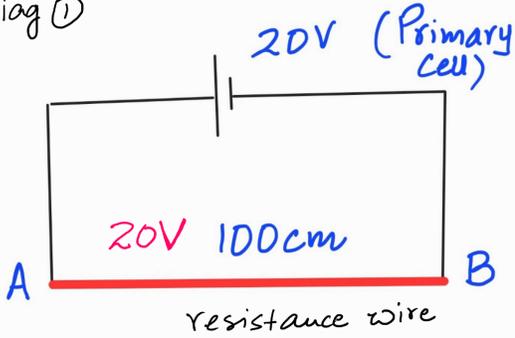



Diag 1



\* Diag 1 shows a resistance wire AB which is connected to a 20V battery (Primary cell). Length of wire AB = 100cm. Connecting wires have Zero Resistance

Q: How much Voltage will be available for this resistance wire AB

Ans = 20V (the entire voltage)

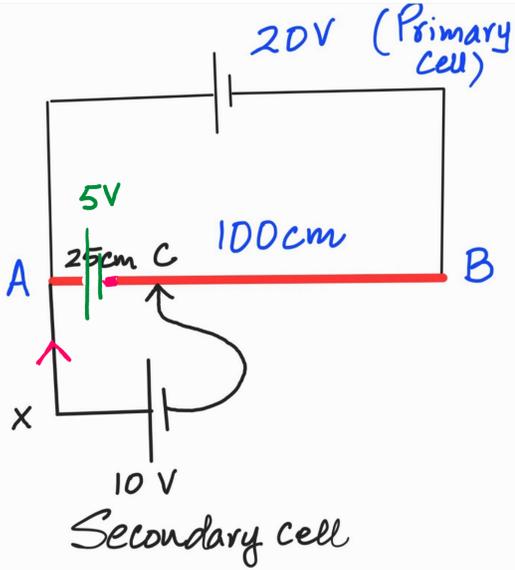


Q: How much Voltage is available for wire AC?

AC  $\frac{1}{4}$ th of AB so Voltage across AC = 5V

Q: for the shaded portion of the diagram Suggest with a reason, should the Current flow from A to X or X to A

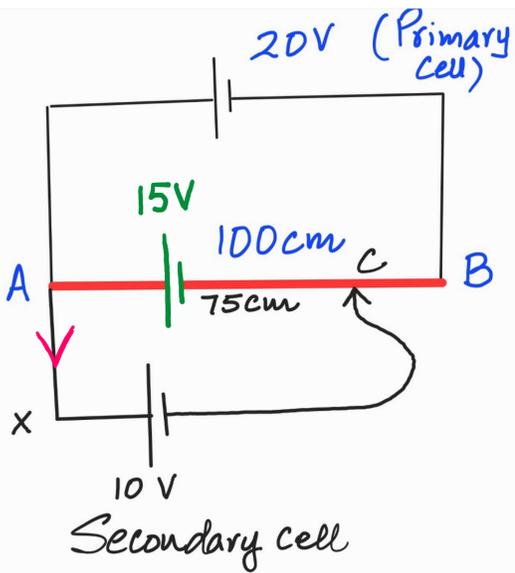
Ans: Current flows from a higher potential to a lower potential  $\therefore$  it flows from X to A



Q: How much voltage is available across wire of length AC where AC = 75cm  
AC =  $\frac{3}{4}$  AB  $\therefore$  Voltage across AC = 15V

Hence determine the direction of Current in the branch AX?

direction of Current A to X

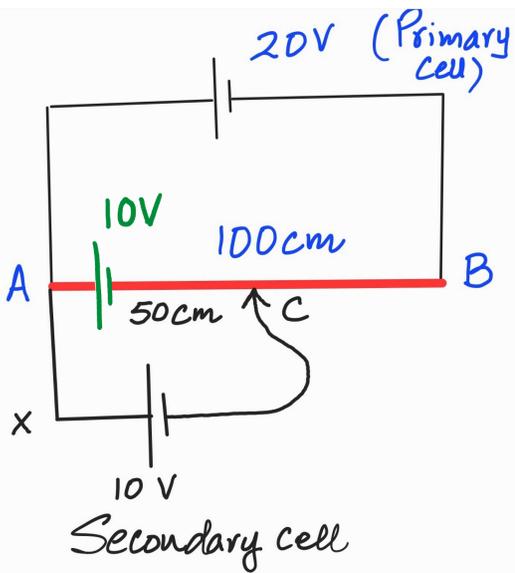


Q: What voltage is available for length AC of the wire  
AC =  $\frac{1}{2}$  AB hence Voltage across AC = 10V

Hence determine the direction of Current in the branch AX

Ans: Null deflection / Zero deflection / Zero Current / Current won't flow.

Why: Voltage across AC is equal to the voltage of the Secondary cell.

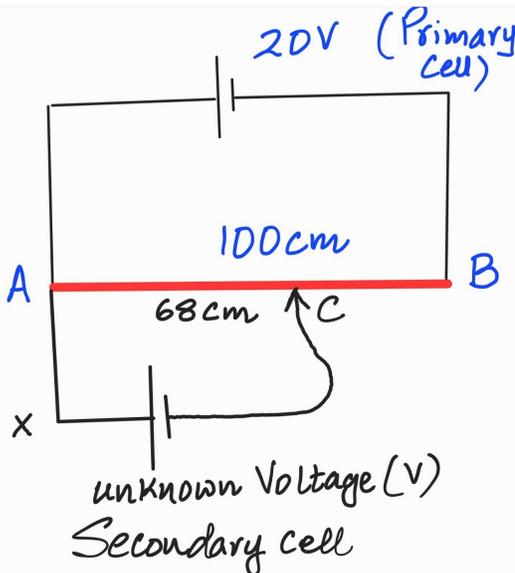Conclusion: For Zero current / Null deflection to be observed, the voltage across length AC of the wire = Voltage of the Secondary cell.



Q: Given that a null deflection / Zero Current / Balance pt is achieved for length AC = 68cm. Use this info. to calculate the unknown Voltage (V) of the Secondary cell.

$$V = \frac{68}{100} \times 20 = 13.6V$$

General formula

$$V = \frac{l_{AC}}{l_{AB}} \times V_{P.C}$$

P.C = Primary Cell

$$V = \frac{R_{AC}}{R_{AB}} \times V_{P.C}$$

$$R = \rho \frac{L}{A} \therefore R \propto L$$