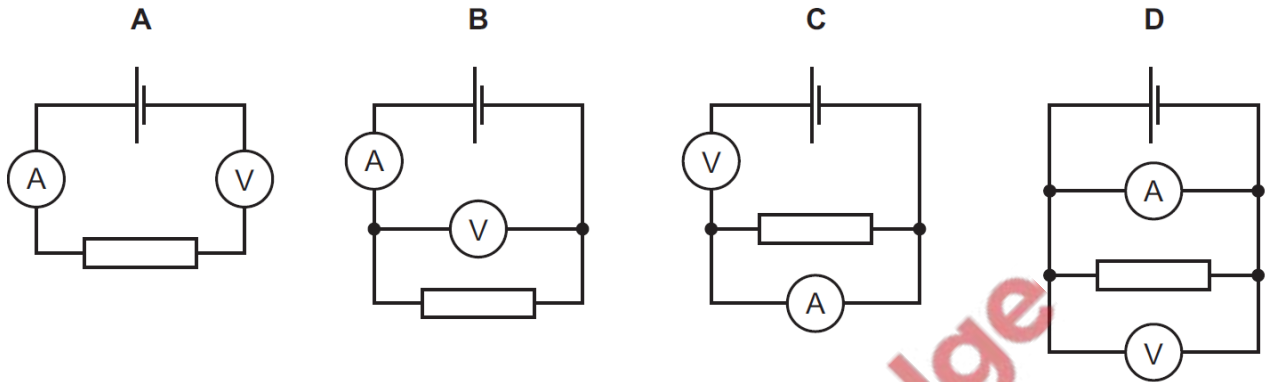


## Electricity – 2019 June

1. 0625/11/M/J/19/No.31

A voltmeter and an ammeter are used to measure the resistance of a resistor.


Which diagram shows the voltmeter and the ammeter correctly connected?



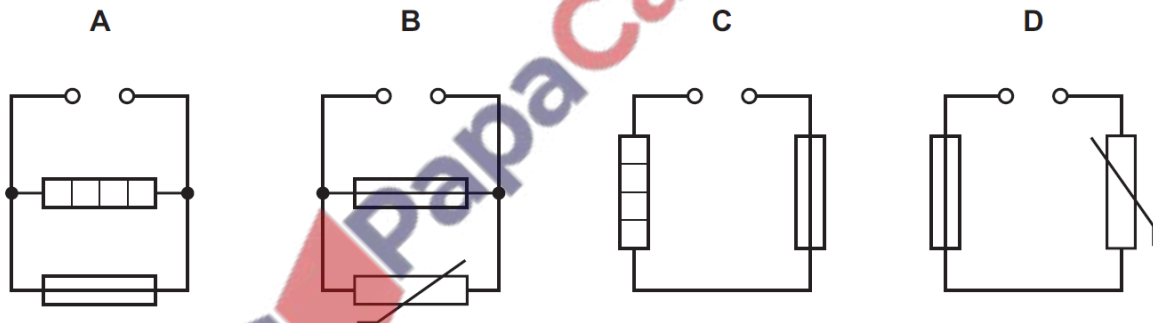2. 0625/11/M/J/19/No.32

A student sets up four circuits.

In which circuit is there a heater in series with a fuse?



3. 0625/11/M/J/19/No.35

An electric heater is plugged into the mains supply using a fused plug.

The current in the heater is 10 A.

The cable attached to the heater is rated at 15 A.

The fuses available are rated at 1 A, 3 A, 5 A and 13 A.

Which fuse should be used?

A 1 A

B 3 A


C 5 A

D 13 A

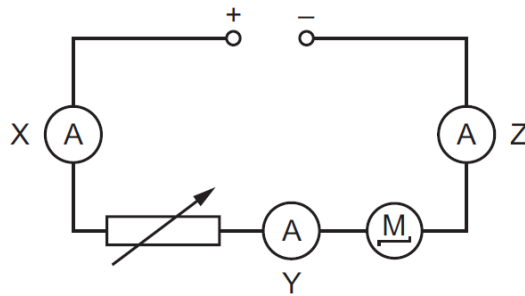4. 0625/11/M/J/19/No.33

The diagram shows a circuit containing a d.c. power supply, a motor and a variable resistor.

Three ammeters X, Y and Z show the current in different parts of the circuit.



The reading on X is 4.0 A.





Which statement is correct?

- A The readings on Y and Z are both less than 4.0 A.
- B The readings on Y and Z are both equal to 4.0 A.
- C The readings on Y and Z are both greater than 4.0 A.
- D The reading on Z is zero.

5. 0625/11/M/J/19/No.34

A lamp is to be connected in a circuit so that the potential difference (p.d.) across it can be varied from 0 to 6 V.


Which circuit would be most suitable?

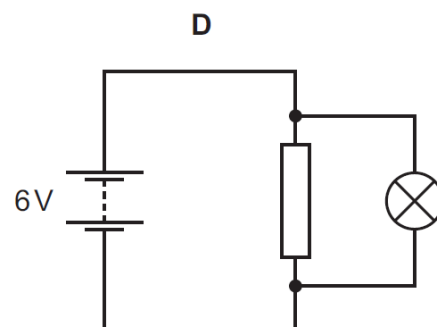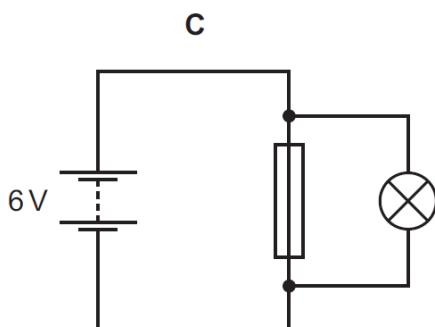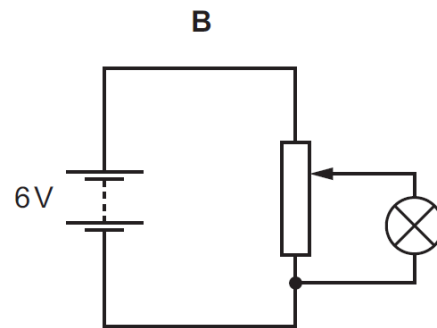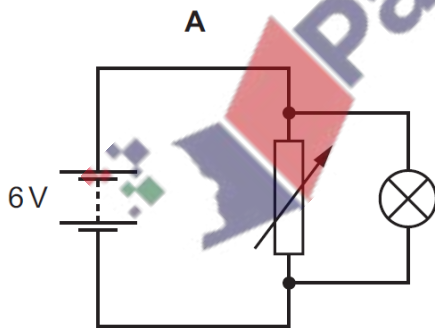

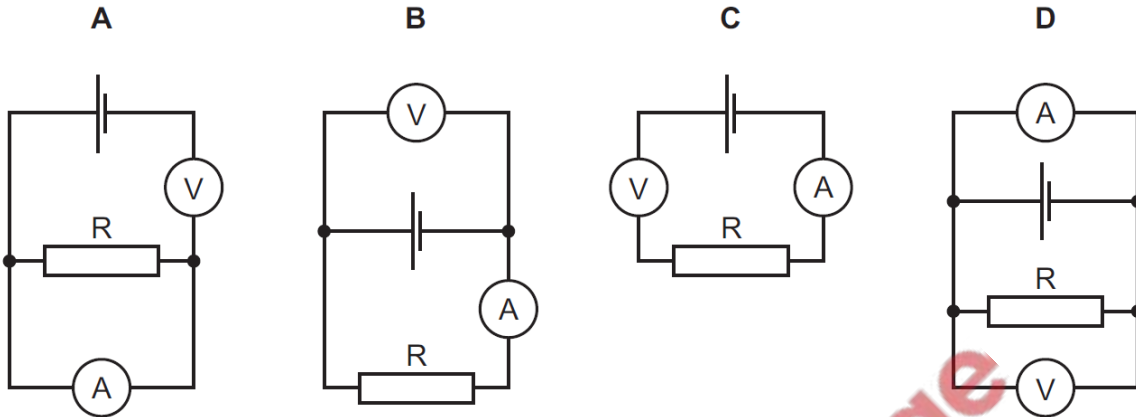6. 0625/12/M/J/19/No.31


An ammeter and a voltmeter are used to determine the resistance of a resistor.

Which circuit diagram shows the ammeter and the voltmeter correctly connected?



7. 0625/12/M/J/19/No.32

The diagram shows a circuit.

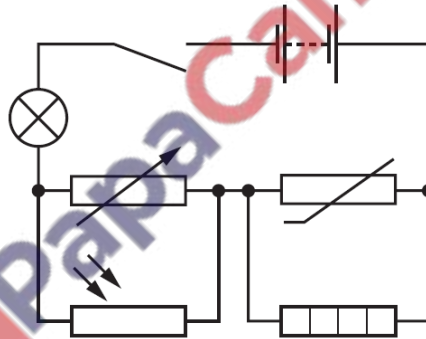


What is connected in parallel with the thermistor?

- A heater
- B lamp
- C light-dependent resistor
- D variable resistor

8. 0625/12/M/J/19/No.33


The circuit shows a relay being used to operate a mains lamp.

Two ammeters are labelled P and Q.

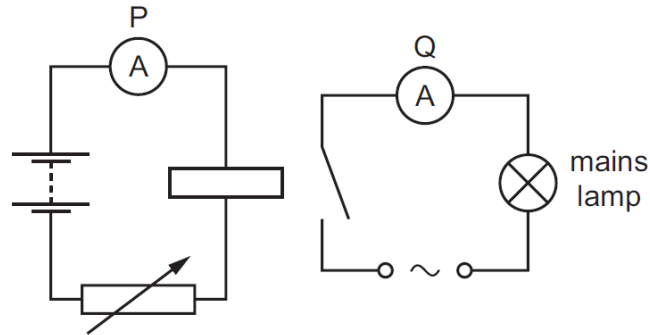

The variable resistor is used to vary the current in the relay coil. The mains lamp switches on when there is a large enough current in the relay coil.

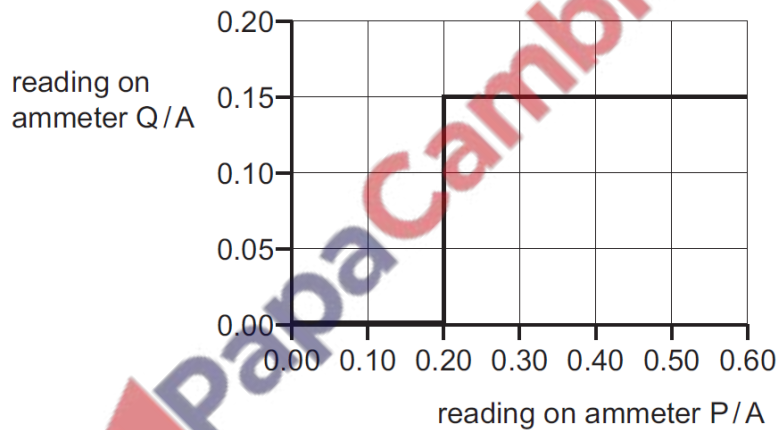The graph shows how the reading on ammeter Q changes as the reading on ammeter P increases.




What is the minimum current needed in the relay coil to switch on the mains lamp?

- A 0.15 A      B 0.20 A      C 0.35 A      D 0.60 A

9. 0625/12/M/J/19/No.34

A lamp is to be connected in a circuit so that the potential difference (p.d.) across it can be varied from 0 to 6 V.

Which circuit would be most suitable?

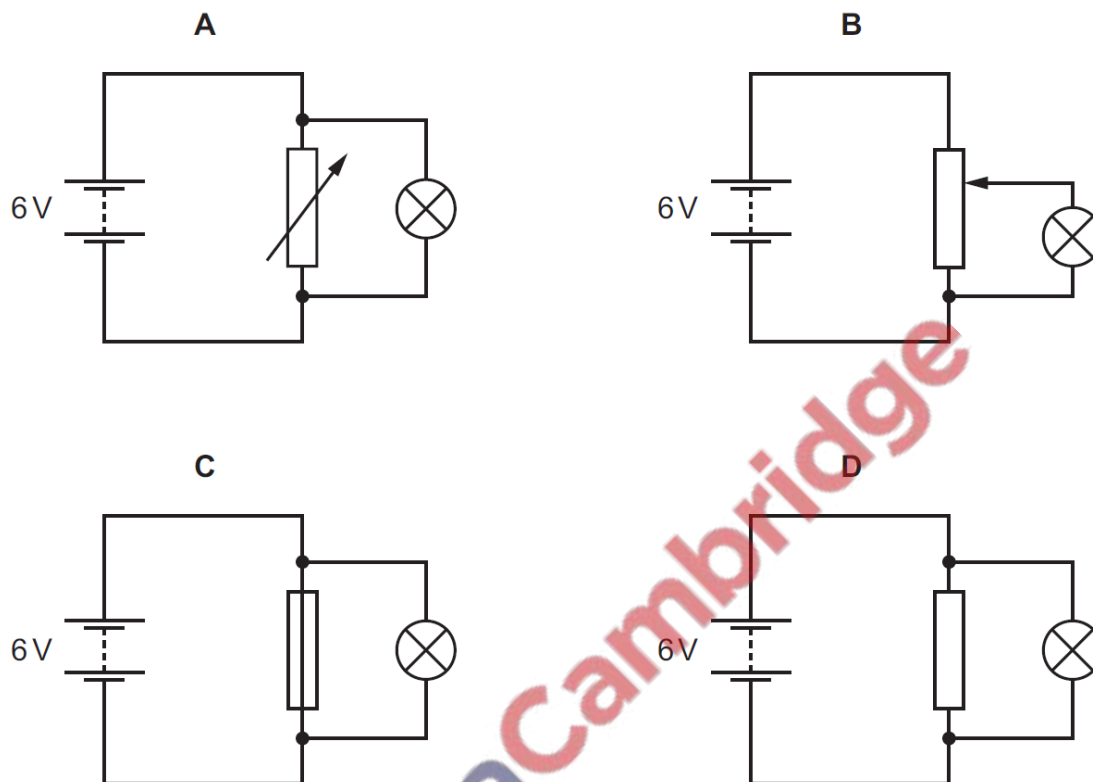

10. 0625/12/M/J/19/No.35

Which components are designed to improve the safe working of a mains electrical supply?

|          | circuit breaker | earth wire | fuse |
|----------|-----------------|------------|------|
| <b>A</b> | ✓               | ✓          | x    |
| <b>B</b> | ✓               | x          | ✓    |
| <b>C</b> | x               | ✓          | ✓    |
| <b>D</b> | ✓               | ✓          | ✓    |

11. 0625/13/M/J/19/No.31

A battery stores chemical potential energy. The battery is connected to a resistor.


As the battery runs down, what happens to its chemical energy?

|          | The energy is transferred by | and ends up as                   |
|----------|------------------------------|----------------------------------|
| <b>A</b> | electrical working           | internal energy in the resistor  |
| <b>B</b> | electrical working           | potential energy in the resistor |
| <b>C</b> | mechanical working           | internal energy in the resistor  |
| <b>D</b> | mechanical working           | potential energy in the resistor |

12. 0625/13/M/J/19/No.32

The diagram shows a circuit including a lamp, an electric bell and three switches  $S_1$ ,  $S_2$  and  $S_3$ .

The lamp and bell are not faulty.

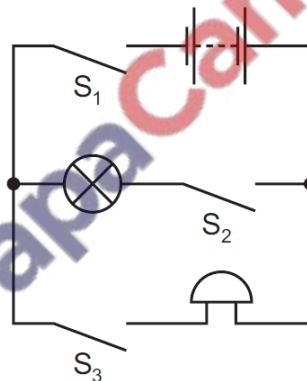

The bell is ringing but the lamp is not lit.

Which switches are closed?


- A**  $S_1$  only
- B**  $S_1$  and  $S_2$  only
- C**  $S_1$  and  $S_3$  only
- D**  $S_1$ ,  $S_2$  and  $S_3$

13. 0625/13/M/J/19/No.33

A student is designing a lighting circuit for a dolls' house. He sets up two different circuits.

Each circuit contains a 12V power supply and three identical lamps.

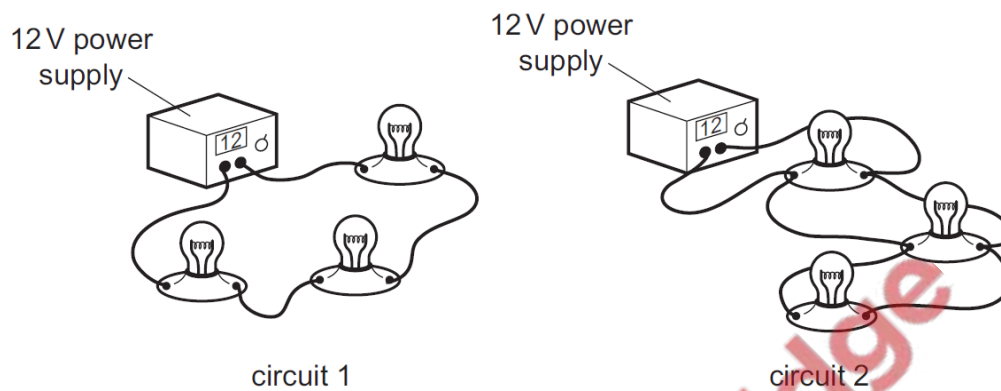Each lamp is designed to operate at normal brightness when connected individually to a 12V supply.



Which statement is correct?



- A In circuit 1, each of the lamps is at normal brightness.
- B In circuit 1, if one lamp fails, the other lamps remain lit.
- C In circuit 2, if one lamp fails, the other lamps remain lit.
- D In circuit 2, the current from the power supply is less than in circuit 1.



14. 0625/13/M/J/19/No.34

A lamp is to be connected in a circuit so that the potential difference (p.d.) across it can be varied from 0 to 6 V.


Which circuit would be most suitable?

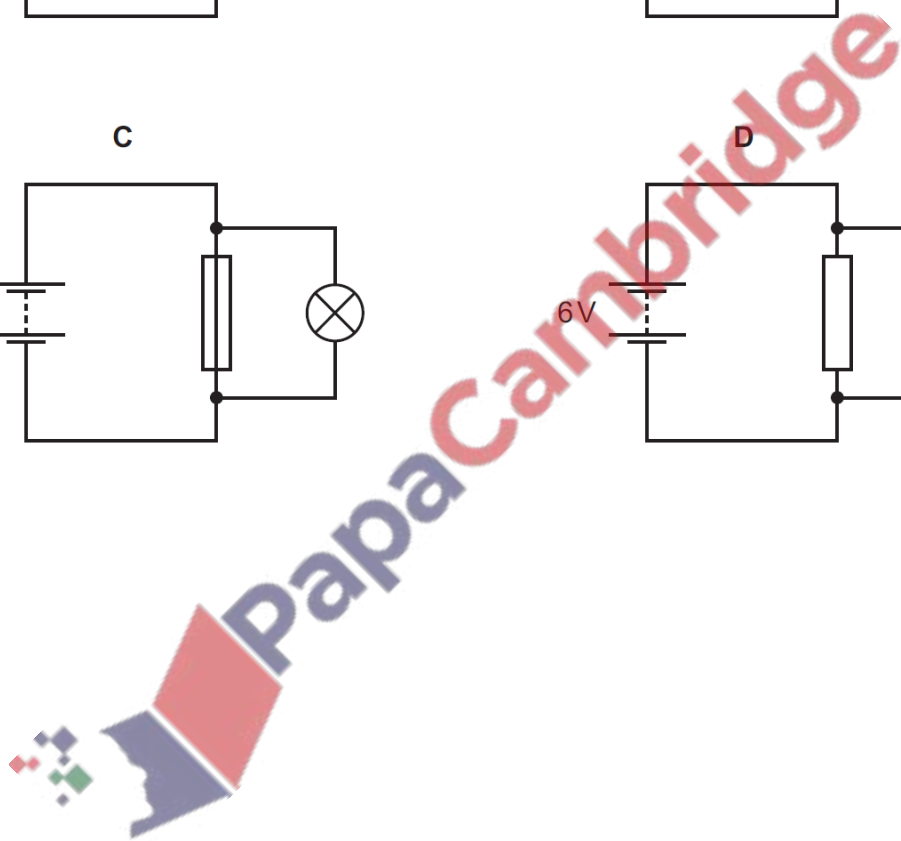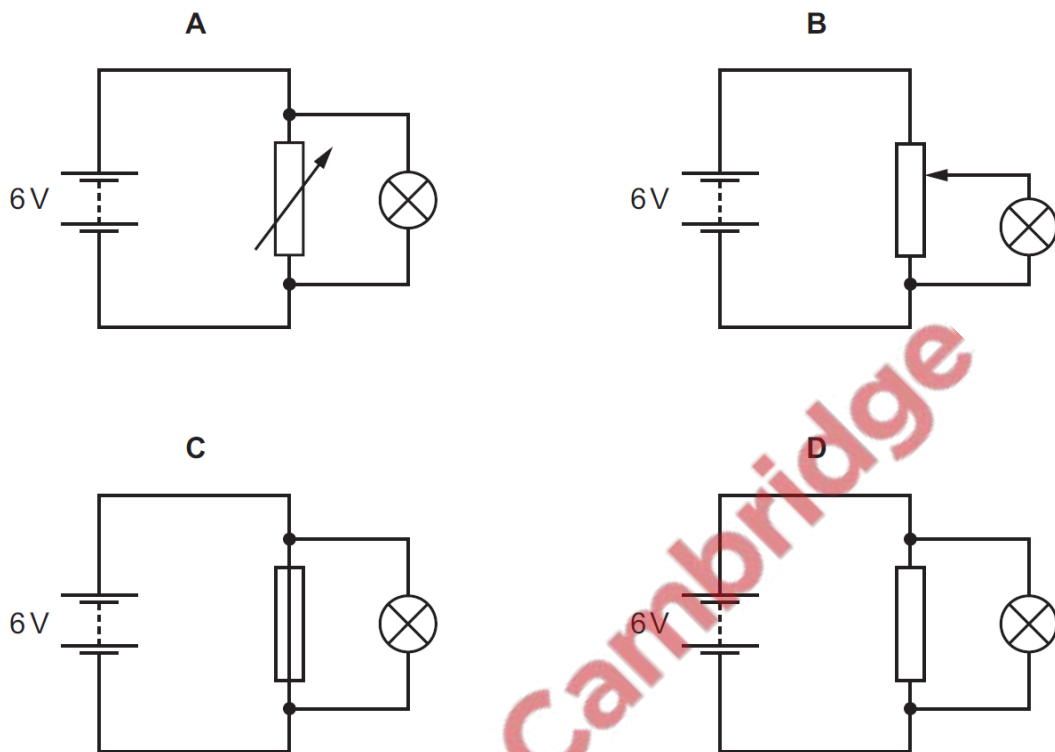



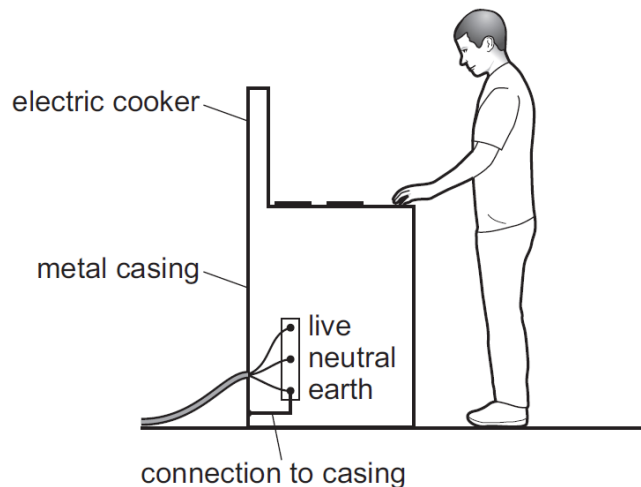15. 0625/13,23/M/J/19/No.35

A simple wiring diagram for an electric cooker is shown.



Why is there a wire connecting the metal case of the cooker to earth?

- A It improves the efficiency of the cooker.
- B It prevents the metal case from becoming too hot when the cooker is left on.
- C It reduces the risk of an electric shock if the live wire touches the metal case.
- D The electric cooker will not switch on without it.

16. 0625/21,22,23/M/J/19/No.28

A cell has an electromotive force (e.m.f.) of 1.5 V.

What does this statement mean?

- A The cell converts 1.0 J of energy when driving 1.5 C of charge round a complete circuit.
- B The cell converts 1.5 J of energy when driving 1.0 C of charge round a complete circuit.
- C The cell converts 1.5 J of energy per second when driving 1.0 C of charge round a complete circuit.
- D The cell converts 1.5 W of power when driving 1.0 C of charge round a complete circuit.

17. 0625/21/M/J/19/No.29


Which two changes to a metal wire both increase resistance?

- A decreasing its length and increasing its temperature
- B increasing its length and decreasing its temperature
- C decreasing its thickness and increasing its temperature
- D increasing its thickness and decreasing its temperature

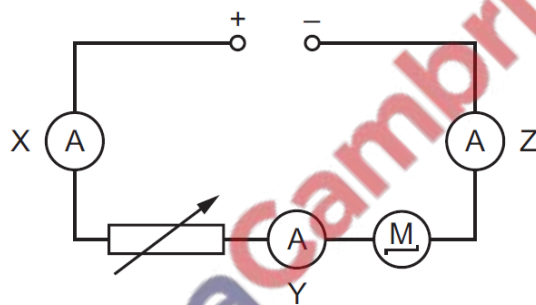18. 0625/21/M/J/19/No.30

The diagram shows a circuit containing a d.c. power supply, a motor and a variable resistor.

Three ammeters X, Y and Z show the current in different parts of the circuit.



The reading on X is 4.0 A.


Which statement is correct?

- A The readings on Y and Z are both less than 4.0 A.
- B The readings on Y and Z are both equal to 4.0 A.
- C The readings on Y and Z are both greater than 4.0 A.
- D The reading on Z is zero.

19. 0625/21/M/J/19/No.31


A lamp is to be connected in a circuit so that the potential difference (p.d.) across it can be varied from 0 to 6 V.

Which circuit would be most suitable?




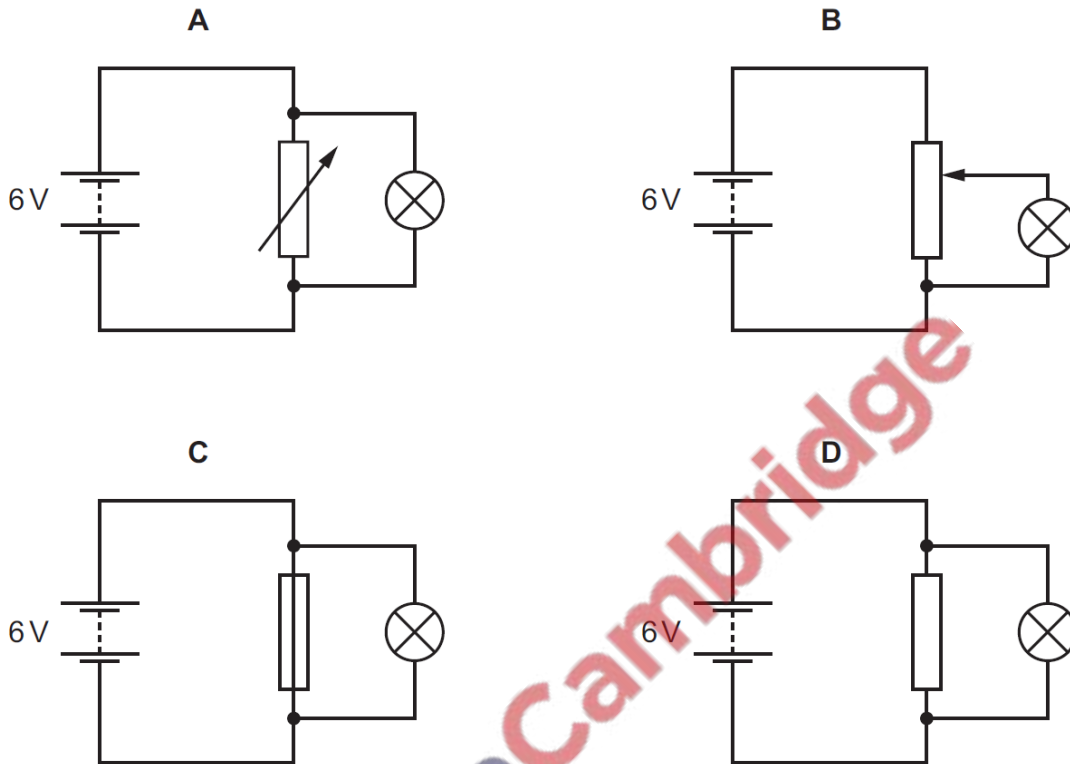


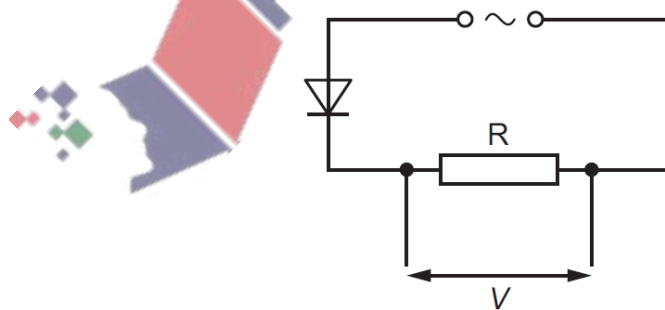20. 0625/21/M/J/19/No.34

An alternating current (a.c.) power supply is connected in series with a resistor  $R$  and a diode.



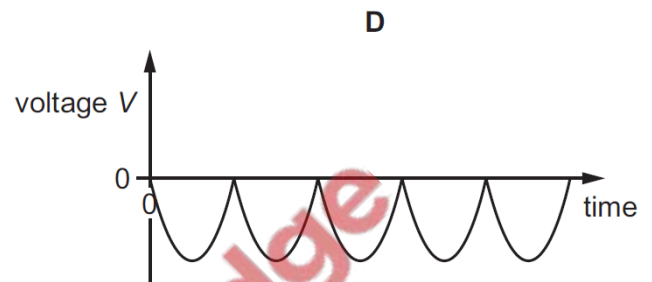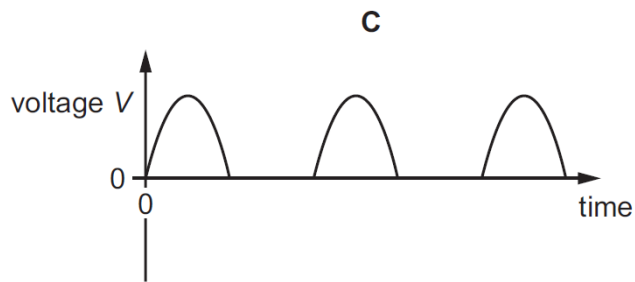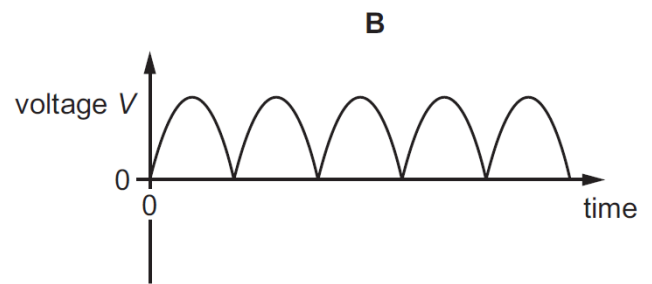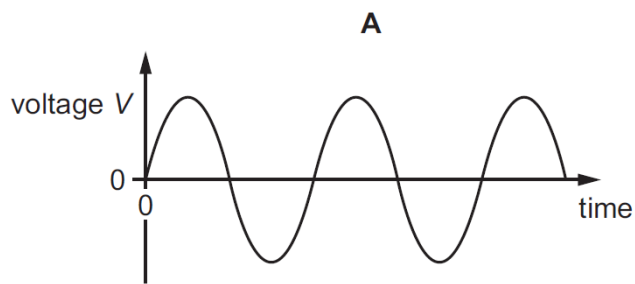Which graph shows how the voltage  $V$  across the resistor  $R$  varies with time?



**21.** 0625/21/M/J/19/No.35

An electric heater is plugged into the mains supply using a fused plug.

The current in the heater is 10 A.

The cable attached to the heater is rated at 15 A.

The fuses available are rated at 1 A, 3 A, 5 A and 13 A.

Which fuse should be used?

**A** 1 A

**B** 3 A

**C** 5 A

**D** 13 A

**22.** 0625/22/M/J/19/No.29

A metal wire of length 100 cm and cross-sectional area  $0.20 \text{ mm}^2$  has a resistance of  $8.0 \Omega$ .

What is the resistance of a wire of the same metal of length 50 cm and cross-sectional area of  $0.40 \text{ mm}^2$ ?

**A**  $2.0 \Omega$


**B**  $8.0 \Omega$

**C**  $16 \Omega$

**D**  $32 \Omega$

23. 0625/22/M/J/19/No.30

The diagram shows a circuit.

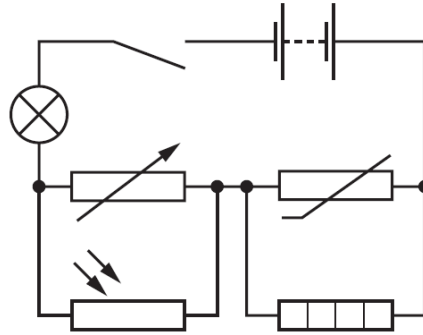


What is connected in parallel with the thermistor?

- A heater
- B lamp
- C light-dependent resistor
- D variable resistor

24. 0625/22/M/J/19/No.31


A lamp is to be connected in a circuit so that the potential difference (p.d.) across it can be varied from 0 to 6 V.

Which circuit would be most suitable?

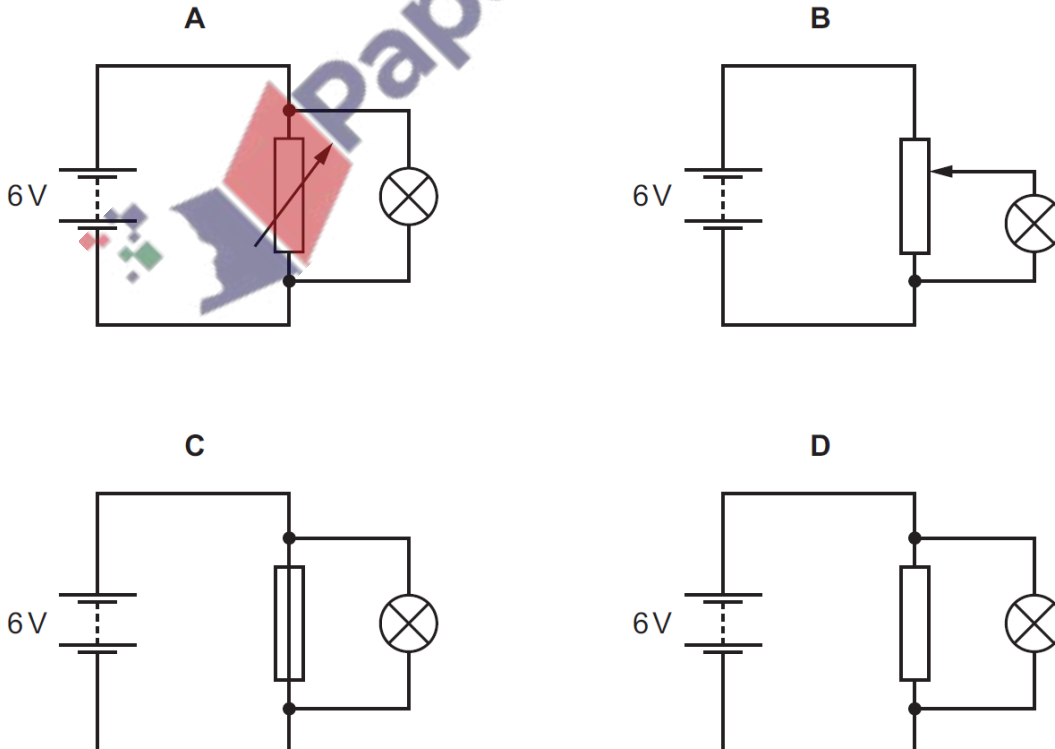

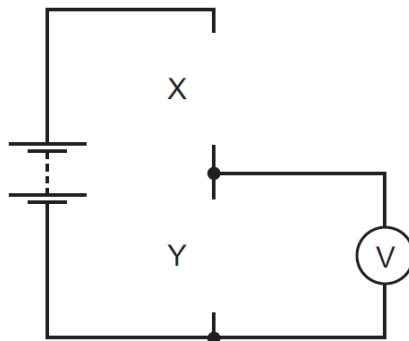25. 0625/22/M/J/19/No.32

Components X and Y can be inserted to complete the circuit below. The completed circuit is a potential divider in which the potential difference across component Y increases when the temperature increases.



Which row shows the components X and Y?

|          | X                        | Y                        |
|----------|--------------------------|--------------------------|
| <b>A</b> | light-dependent resistor | resistor                 |
| <b>B</b> | resistor                 | light-dependent resistor |
| <b>C</b> | resistor                 | thermistor               |
| <b>D</b> | thermistor               | resistor                 |

26. 0625/22/M/J/19/No.35

Which components are designed to improve the safe working of a mains electrical supply?

|          | circuit breaker | earth wire | fuse |
|----------|-----------------|------------|------|
| <b>A</b> | ✓               | ✓          | x    |
| <b>B</b> | ✓               | x          | ✓    |
| <b>C</b> | x               | ✓          | ✓    |
| <b>D</b> | ✓               | ✓          | ✓    |

27. 0625/23/M/J/19/No.29

Two wires X and Y are made from the same metal and have the same resistance.


Which row identifies a possible pair of values for X and for Y?

|          | length of X<br>/cm | diameter of X<br>/mm | length of Y<br>/cm | diameter of Y<br>/mm |
|----------|--------------------|----------------------|--------------------|----------------------|
| <b>A</b> | 50                 | 0.40                 | 200                | 0.10                 |
| <b>B</b> | 50                 | 0.40                 | 200                | 0.20                 |
| <b>C</b> | 50                 | 0.40                 | 200                | 0.80                 |
| <b>D</b> | 50                 | 0.40                 | 200                | 1.60                 |

28. 0625/23/M/J/19/No.30

The diagram shows a circuit including a lamp, an electric bell and three switches  $S_1$ ,  $S_2$  and  $S_3$ .

The lamp and bell are not faulty.

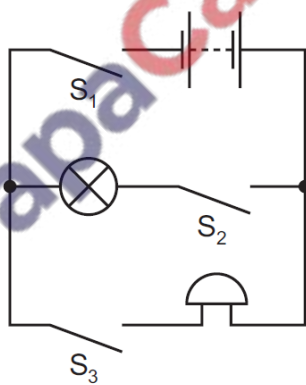

The bell is ringing but the lamp is not lit.


Which switches are closed?

- A**  $S_1$  only
- B**  $S_1$  and  $S_2$  only
- C**  $S_1$  and  $S_3$  only
- D**  $S_1$ ,  $S_2$  and  $S_3$

29. 0625/23/M/J/19/No.31


A lamp is to be connected in a circuit so that the potential difference (p.d.) across it can be varied from 0 to 6 V.

Which circuit would be most suitable?

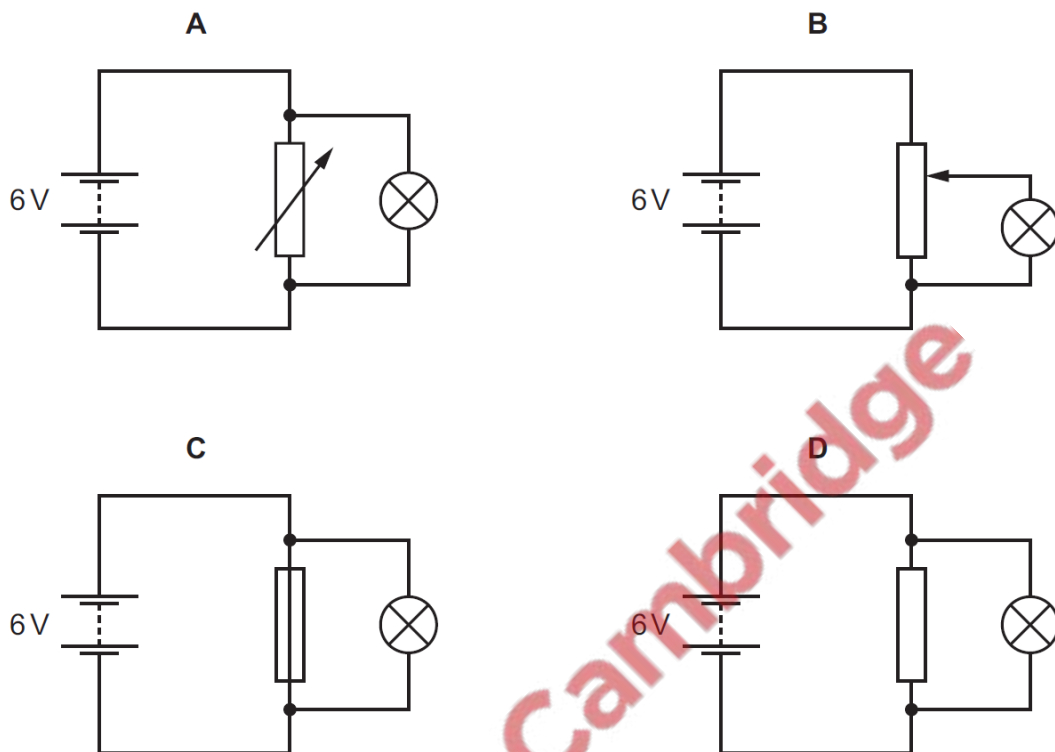

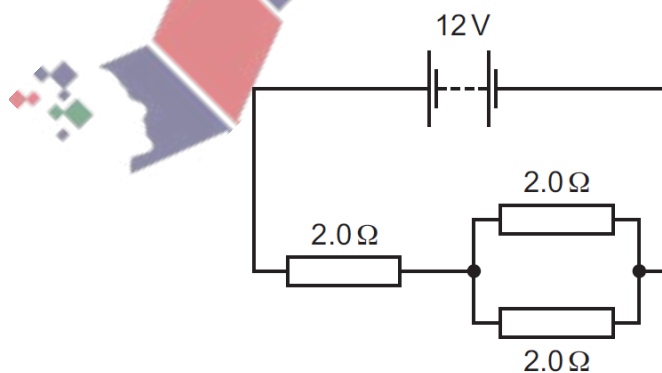30. 0625/23/M/J/19/No.32

A 12V battery is connected to a combination of  $2.0\Omega$  resistors as shown.



What is the current in the battery?

- A 1.5A      B 2.0A      C 4.0A      D 6.0A




31. 0625/23/M/J/19/No.33

A student is designing a lighting circuit for a dolls' house. He sets up two different circuits.

Each circuit contains a 12V power supply and three identical lamps.

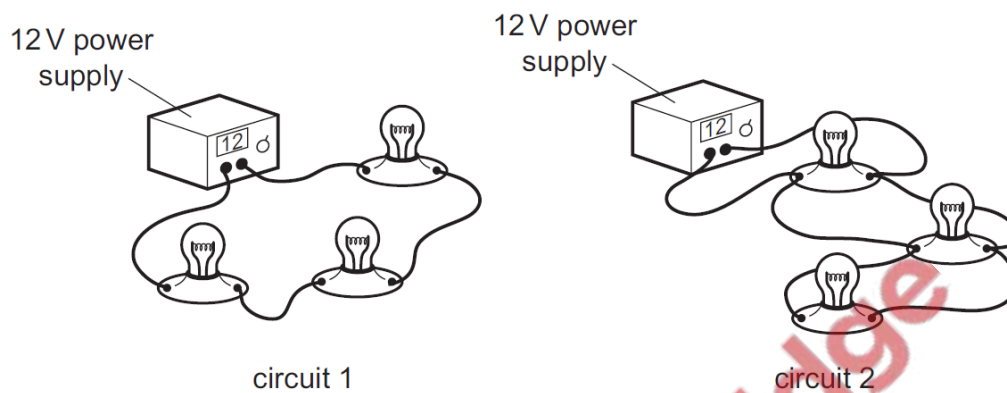Each lamp is designed to operate at normal brightness when connected individually to a 12V supply.



Which statement is correct?

- A In circuit 1, each of the lamps is at normal brightness.
- B In circuit 1, if one lamp fails, the other lamps remain lit.
- C In circuit 2, if one lamp fails, the other lamps remain lit.
- D In circuit 2, the current from the power supply is less than in circuit 1.

32. 0625/12/F/M/19/No.28

Which statement about a voltmeter is correct?

- A A voltmeter measures the current in a component and is connected in series with the component.
- B A voltmeter measures the current in a component and is connected in parallel with the component.
- C A voltmeter measures the potential difference (p.d.) across a component and is connected in series with the component.
- D A voltmeter measures the potential difference (p.d.) across a component and is connected in parallel with the component.

33. 0625/12/F/M/19/No.29


Four wires are made from the same metal.

Which wire has the lowest resistance?





|          | length of wire / cm | diameter of wire / mm |
|----------|---------------------|-----------------------|
| <b>A</b> | 20                  | 0.20                  |
| <b>B</b> | 20                  | 0.40                  |
| <b>C</b> | 40                  | 0.20                  |
| <b>D</b> | 40                  | 0.40                  |

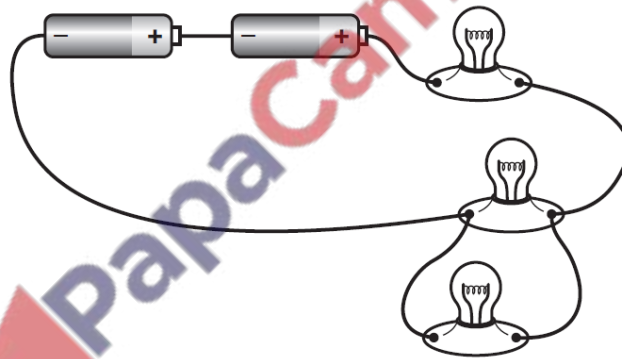34. 0625/12, 22/F/M/19/No.30, 31

A student sets up a circuit containing a battery of two cells and three lamps, as shown.



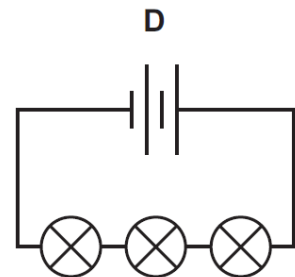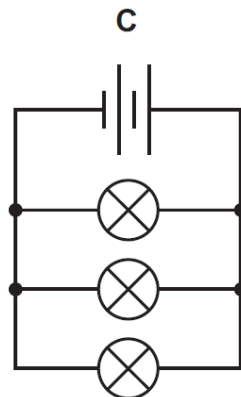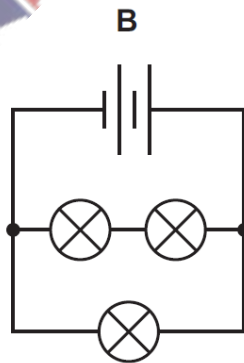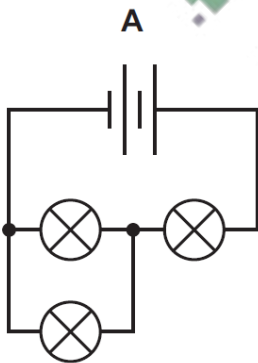
What is the circuit diagram for this arrangement?



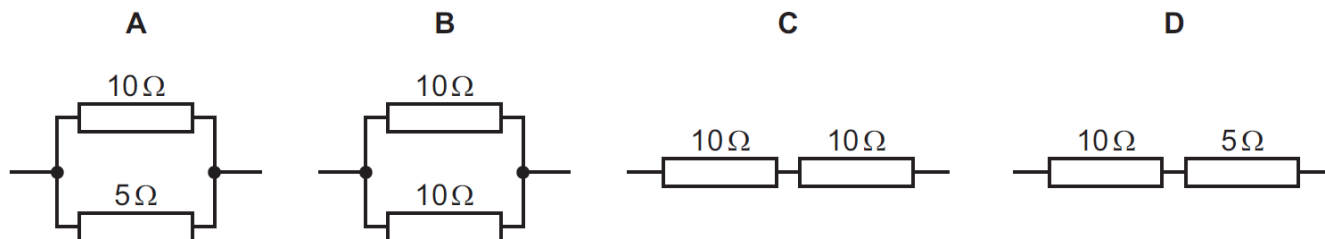35. 0625/12/F/M/19/No.31


The diagrams show different resistor arrangements.

Which arrangement has the smallest combined resistance?



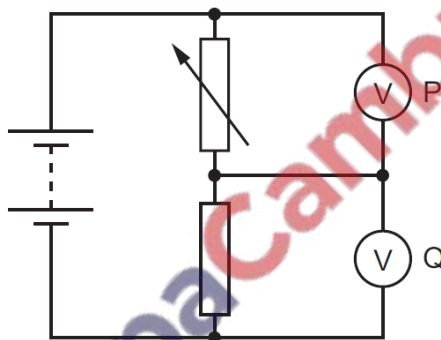36. 0625/12/F/M/19/No.32

The diagram shows a potential divider circuit.



The resistance of the variable resistor is increased.

Which row shows what happens to the reading on voltmeter P and on voltmeter Q?

|   | reading on voltmeter P | reading on voltmeter Q |
|---|------------------------|------------------------|
| A | decreases              | decreases              |
| B | decreases              | increases              |
| C | increases              | decreases              |
| D | increases              | increases              |

37. 0625/12/F/M/19/No.33

The current in a kettle is 10 A and the kettle is protected by a 13 A fuse.

The owner of the kettle replaces the 13 A fuse with a 3 A fuse.

What happens when the kettle is switched on?

- A The fuse melts and the kettle might be damaged.
- B The fuse melts and the kettle is undamaged.
- C The fuse does not melt and the kettle works correctly.
- D The fuse does not melt but the kettle fails to work.


38. 0625/22/F/M/19/No.30

Which electrical quantity is defined in terms of the energy supplied in driving charge round a complete circuit?

- A current
- B electromotive force
- C potential difference
- D power

39. 0625/22/F/M/19/No.32


In which circuit does the lamp light?

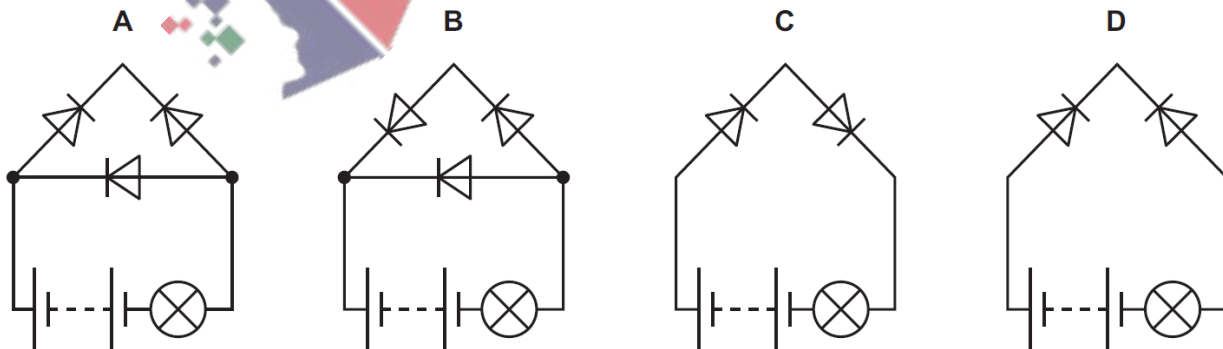

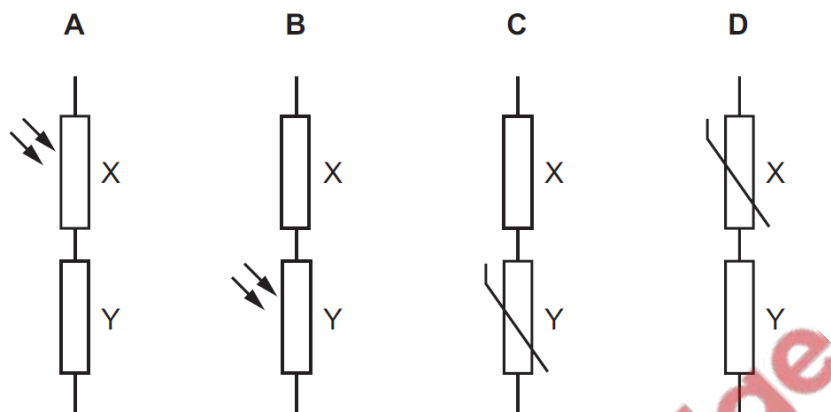40. 0625/22/F/M/19/No.33

Each potential divider is placed in a circuit with a power supply.

Which potential divider makes the potential difference across component Y increase when the light intensity increases?



41. 0625/22/F/M/19/No.35

The current in a kettle is 10 A and the kettle is protected by a 13 A fuse.

The owner of the kettle replaces the 13 A fuse with a 3 A fuse.

What happens when the kettle is switched on?

- A The fuse melts and the kettle might be damaged.
- B The fuse melts and the kettle is undamaged.
- C The fuse does not melt and the kettle works correctly.
- D The fuse does not melt but the kettle fails to work.

42. 0625/22/F/M/19/No.36

Which statement about the direction of a magnetic field at a point is correct?

- A It is the direction of the force on a north pole placed at that point.
- B It is the direction of the force on a south pole placed at that point.
- C It is the direction of the force on a positive charge placed at that point.
- D It is the direction of the force on a negative charge placed at that point.