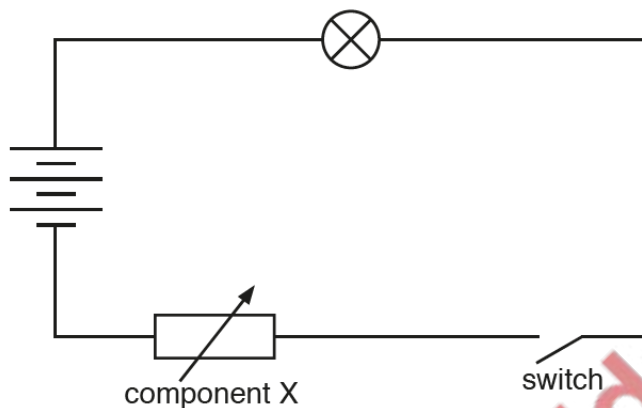


1. 0625/31/O/N/19/No.10

A teacher is investigating the resistance of a lamp.

Fig. 10.1 shows part of the circuit she uses. The circuit is incomplete.



**Fig. 10.1**

(a) (i) To determine the resistance of the lamp, the teacher adds two meters to her circuit.

On Fig. 10.1, draw circuit symbols to show each meter correctly connected in the circuit. [3]

(ii) When the current in the lamp is 0.25A, the potential difference (p.d.) across the lamp is 4.5V. Calculate the resistance of the lamp.

resistance = .....  $\Omega$  [3]

(b) (i) State the name of component X.

..... [1]

(ii) Describe and explain how the teacher uses component X to investigate the resistance of the lamp.

.....  
.....  
.....  
..... [2]

[Total: 9]

A circuit is made from two lamps, a cell and a switch, as shown in Fig. 10.1.

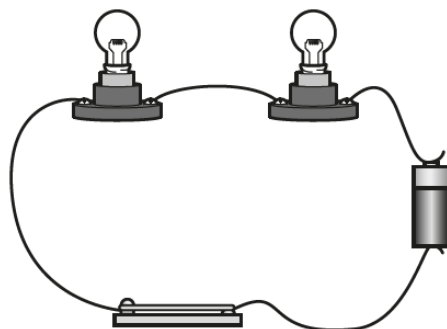


Fig. 10.1

(a) (i) Draw the circuit symbol for a cell.

[1]


(ii) State the term used for the arrangement of lamps in the circuit in Fig. 10.1.

..... [1]

(iii) The switch is closed and the lamps light.

State the name of the charged particles that are flowing through the wires

..... [1]

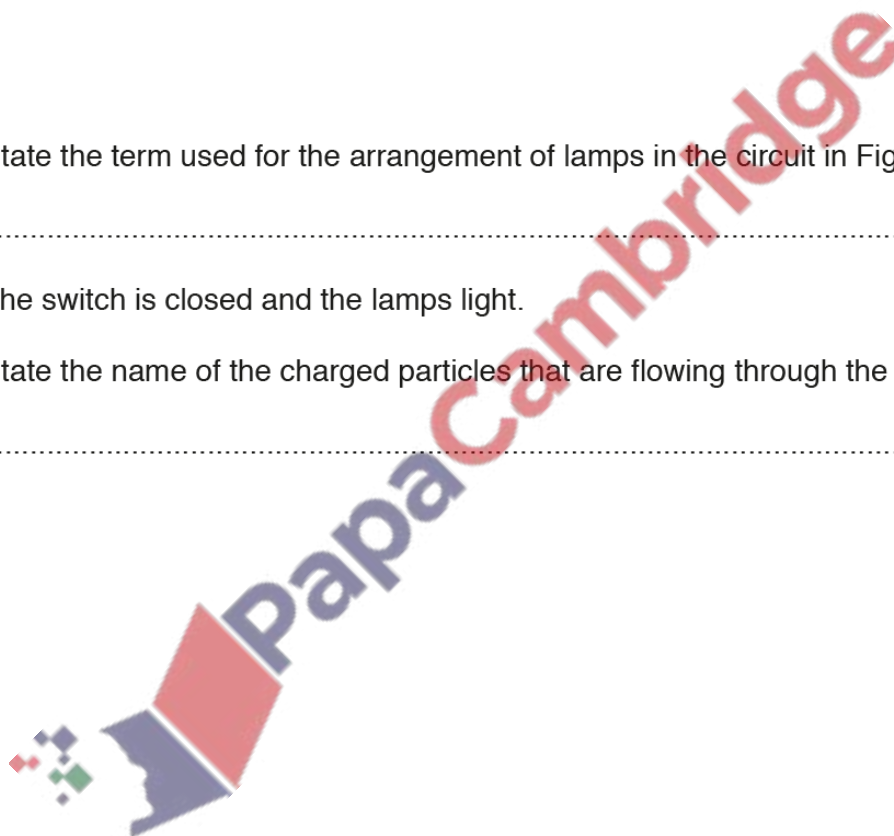

(b) Fig. 10.2 represents a different type of circuit.

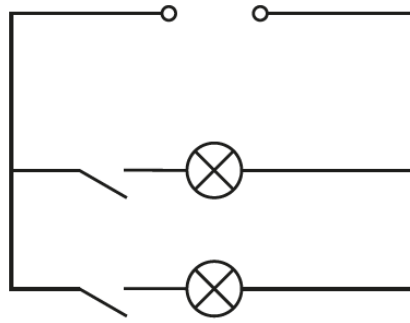


Fig. 10.2

(i) Compare Fig. 10.1 and Fig. 10.2. State **two** advantages of the type of circuit shown in Fig. 10.2 with the type of circuit shown in Fig. 10.1.

1. ....

2. ....

[2]

(ii) The potential difference across the power source in Fig. 10.2 is 3.0V. The combined resistance of the two lamps is  $12\Omega$ . Calculate the size of the current in the circuit.

current = ..... A [3]

[Total: 8]

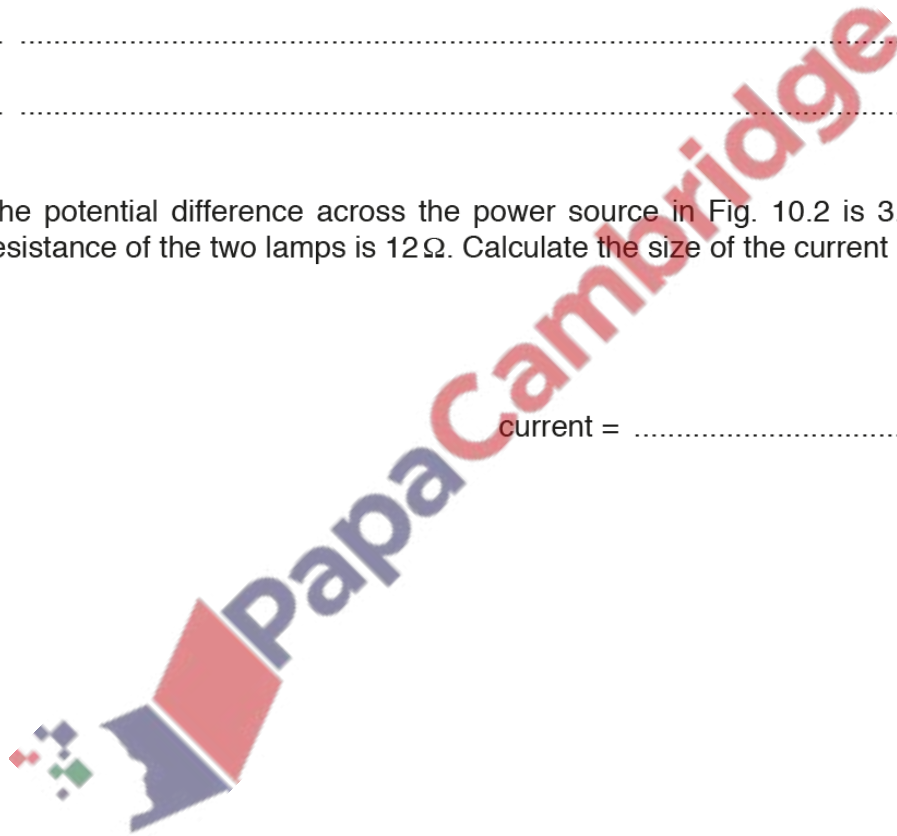


Fig. 10.1 shows the symbol for an electrical component.

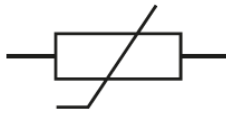


Fig. 10.1

(a) State the name of the component shown in Fig. 10.1.

..... [1]

(b) The resistance of the component shown in Fig. 10.1 varies with temperature. Fig. 10.2 shows a graph of resistance against temperature for the component.

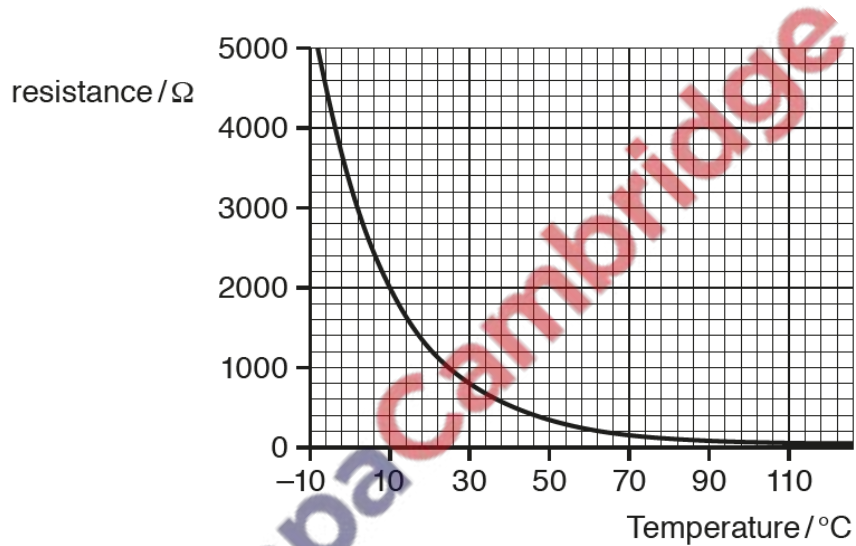


Fig. 10.2

(i) Use Fig. 10.2 to determine the resistance of the component at a temperature of 10 °C.

..... Ω [1]

(ii) At another temperature, the resistance of the component is 800 Ω. Calculate the current in the component when it is connected to a 12.0 V supply.

current = ..... A [3]

[Total: 5]

4. 0625/41/O/N/19/No.7

The resistance of a 1.0 m length of resistance wire is  $7.6 \Omega$ . A length of this wire is taped to a metre rule. A crocodile clip is connected to one end of the resistance wire exactly at the 0 m mark of the rule. Fig. 7.1 shows the crocodile clip connected to terminal P.

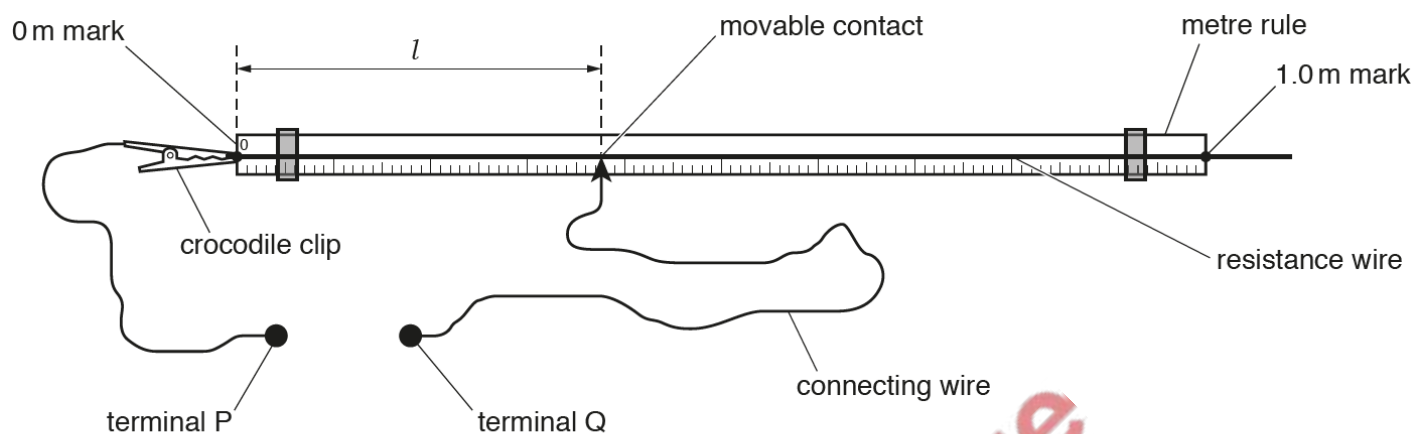


Fig. 7.1

A second terminal Q is connected to a movable contact using a long length of connecting wire. The movable contact is in contact with the resistance wire at a length  $l$  from the 0 m mark on the rule.

The movable contact is placed at different points on the resistance wire. The resistance  $R$  of the length  $l$  of the wire depends on  $l$ .

- (a) On Fig. 7.2, sketch a graph to show how  $R$  varies with  $l$  for values of  $l$  between  $l = 0$  and  $l = 1.0$  m. Mark appropriate values on the axes of the graph.

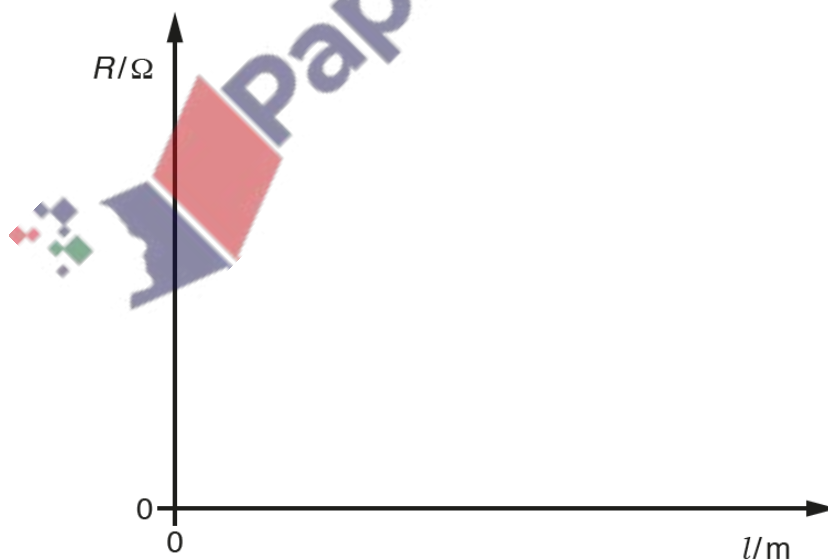


Fig. 7.2

[2]

(b) Fig. 7.3 shows a battery of electromotive (e.m.f.) 12 V connected across the 1.0 m length of the resistance wire.

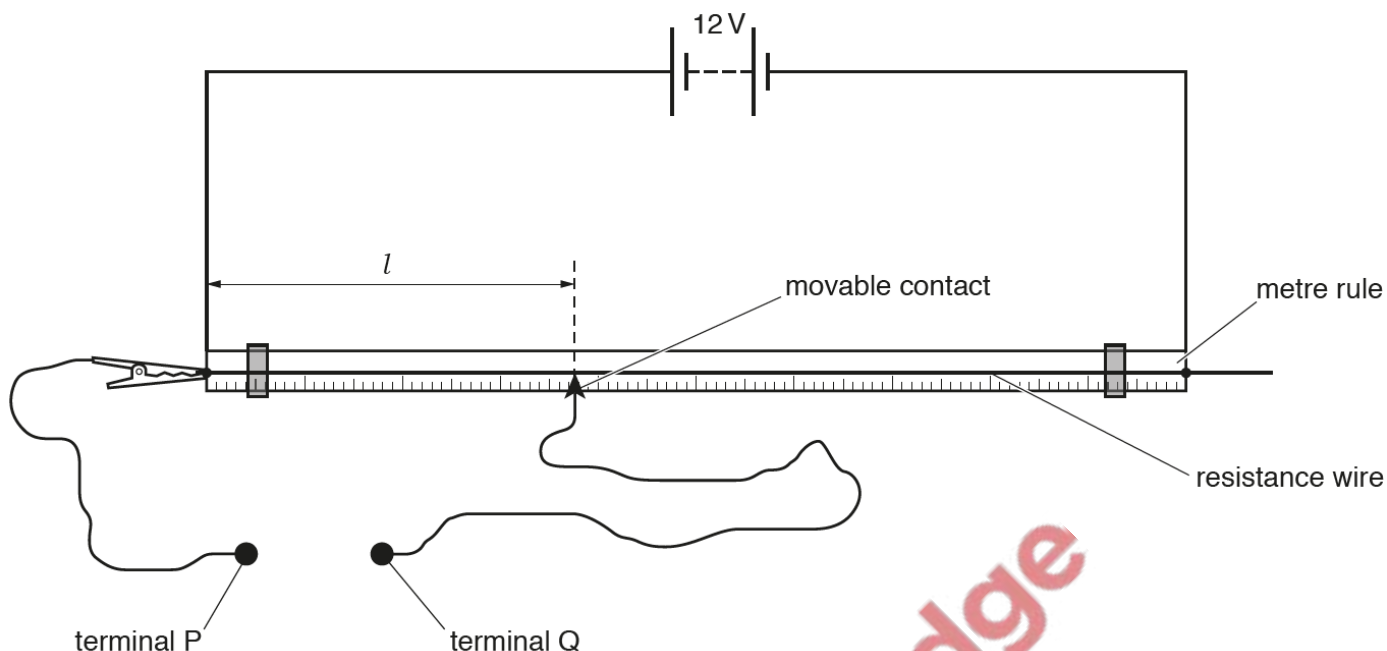


Fig. 7.3

(i) State what is meant by *electromotive force (e.m.f.)*.

.....  
 .....  
 ..... [2]

(ii) Calculate:

1. the current in the resistance wire

current = ..... [2]

2. the potential difference (p.d.) between terminal P and terminal Q when  $l = 0.35\text{ m}$

p.d. = ..... [1]

3. the charge that passes through the resistance wire in 5.5 minutes.

charge = ..... [2]

[Total: 9]

Fig. 9.1 shows a circuit containing an LED and two resistors in parallel, each of resistance  $R$ .

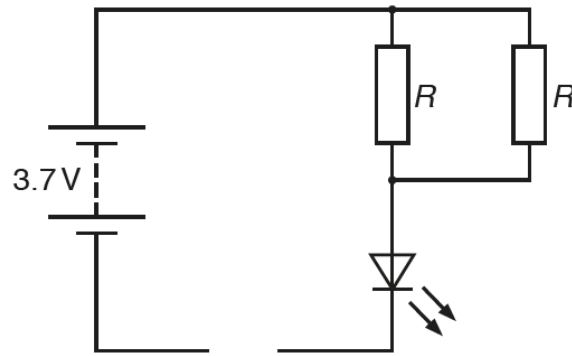


Fig. 9.1

The normal operating voltage of the LED is 2.1 V and the normal current is 0.19 A.

- (a) (i) The potential difference (p.d.) across the LED is measured with a voltmeter.

On Fig. 9.1, draw the symbol for this voltmeter connected to the circuit. [1]

- (ii) The current in the LED is measured with an ammeter.

On Fig. 9.1, draw the symbol for this ammeter connected to the circuit. [1]

- (b) Calculate the value of  $R$  when the LED is operating normally.

$R = \dots\dots\dots$  [5]

[Total: 7]