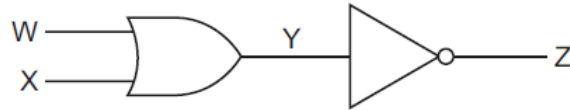


**1. June/2022/Paper\_21/No.34**

A digital circuit is made of two logic gates.




Which row is correct for this digital circuit?

	W	X	Y	Z
<b>A</b>	0	0	1	0
<b>B</b>	0	1	0	1
<b>C</b>	1	0	1	0
<b>D</b>	1	1	0	1

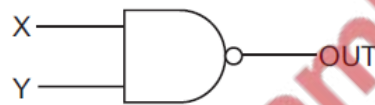**2. June/2022/Paper\_22/No.34**

What is the truth table for the logic gate shown by the symbol?



<b>A</b>			<b>B</b>			<b>C</b>			<b>D</b>		
X	Y	OUT	X	Y	OUT	X	Y	OUT	X	Y	OUT
0	0	0	0	0	0	0	0	1	0	0	1
0	1	0	0	1	1	0	1	0	0	1	1
1	0	0	1	0	1	1	0	0	1	0	1
1	1	1	1	1	1	1	1	0	1	1	0

**3. June/2022/Paper\_23/No.34**

The truth table for a logic gate is shown.

inputs		output
0	0	1
0	1	1
1	0	1
1	1	0

Which type of logic gate is it?

- A** AND      **B** NAND      **C** OR      **D** NOR

4. June/2022/Paper\_41/No.9

Combinations of logic gates are used when digital signals are processed.

- (a) Describe the difference between a digital signal and an analogue signal. You may include a diagram if it helps your answer.

.....

.....

..... [2]

- (b) Fig. 9.1 is the truth table for a logic gate X.

input A	input B	output
0	0	1
0	1	0
1	0	0
1	1	0

Fig. 9.1

State the name of logic gate X and draw the symbol that represents it.

name .....

symbol .....

[1]

(c) Logic gate Y is identical to logic gate X.

Draw a combination of logic gates X and Y that behaves like an OR gate. Label the inputs A and B and label the output Q.

[2]

[Total: 5]

5. June/2022/Paper\_42/No.10

Fig. 10.1 is a simplified diagram of a digital circuit. The output of logic gate Y controls a buzzer.

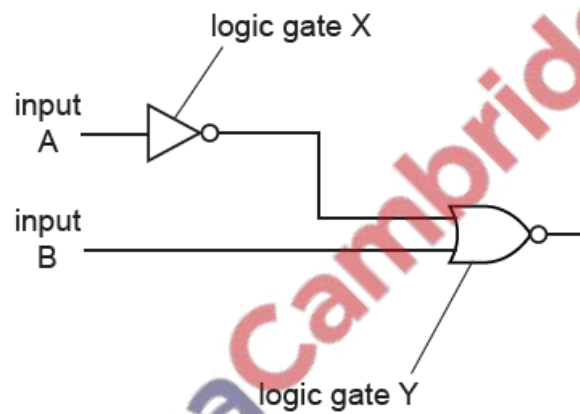


Fig. 10.1

(a) Complete Table 10.1, the truth table for the circuit.

Table 10.1

input A	input B	output of X	output of Y
0	0		
0	1		
1	0		
1	1		

[3]

(b) Input A is the output of a humidity sensor which gives logic 1 when the humidity is high and logic 0 when the humidity is low.

Input B is the output of a light sensor which gives logic 1 in bright light and logic 0 in darkness. The buzzer sounds when the output of Y is logic 1.

State the conditions of humidity and light when the buzzer is on.

..... [1]

(c) The output of the digital circuit alone is **not** able to operate the buzzer.

Ring the component from the list that must be connected between the output of the digital circuit and the buzzer.

- fuse      heater      relay      resistor      thermistor

Explain your answer.

.....  
.....

[3]

[Total: 7]

