

Electrical Quantities

Question Paper 3

Level	IGCSE
Subject	Physics (0625/0972)
Exam Board	Cambridge International Examinations (CIE)
Topic	General Physics
Sub-Topic	Electrical Quantities
Booklet	Question Paper 3

Time allowed: 19 minutes

Score: /15


Percentage: /100

Grade Boundaries:

9	8	7	6	5	4	3	2	1
>85%	75%	68%	60%	55%	50%	43%	35%	<30%

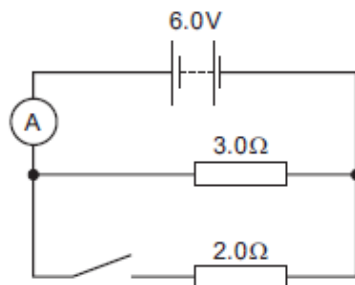Question 1

The diagram shows a circuit with a $3.0\ \Omega$ resistor and a $2.0\ \Omega$ resistor connected in parallel.



The switch is open, and the ammeter reads 2.0 A .

The switch is now closed and the ammeter reads the total current in both resistors.

What is the ammeter reading with the switch closed?

- A 1.2 A B 3.0 A C 4.0 A D 5.0 A

Question 2

Which row gives the unit for energy and the unit for electromotive force (e.m.f.)?

	energy	e.m.f.
A	J	N
B	J	V
C	W	N
D	W	V

Question 3

Four wires are made from the same material.

Which wire has the least resistance?

	diameter of wire/mm	length of wire/cm
A	0.2	100
B	0.2	200
C	0.4	100
D	0.4	200

Question 4

Which equation can be used to calculate the resistance R of a resistor?

- A $V = I \div R$ B $I = V \times R$ C $R = V \times I$ D $V = I \times R$

Question 5

A student wishes to measure first the electromotive force (e.m.f.) of a battery, and then the potential difference (p.d.) across a resistor.

She has the resistor, the battery and some connecting wires.


What else does she need?

- A. a force meter (newton meter) and a voltmeter
- B. an ammeter and a voltmeter
- C. an ammeter only
- D. a voltmeter only

Question 6


Two similar balloons hang side by side, on insulating threads, a short distance apart. They are both rubbed with the same dry cloth and become charged.

Which diagram shows how the balloons hang after charging?

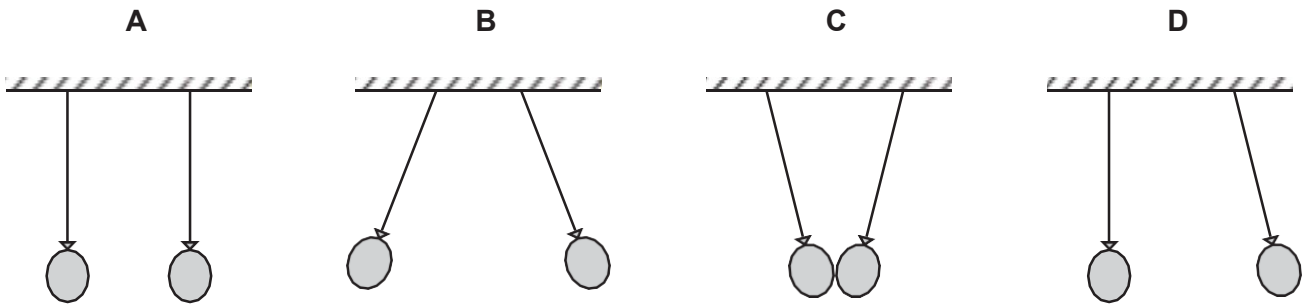

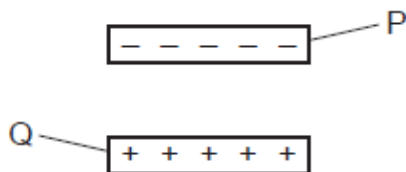Question 7

A negatively charged plastic rod P is placed above a positively charged plastic rod Q.




What are the directions of the electrostatic forces on rod P and on rod Q?

	electrostatic force on rod P	electrostatic force on rod Q
A	downwards	downwards
B	downwards	upwards
C	upwards	downwards
D	upwards	upwards

Question 8

The diagram shows a circuit.

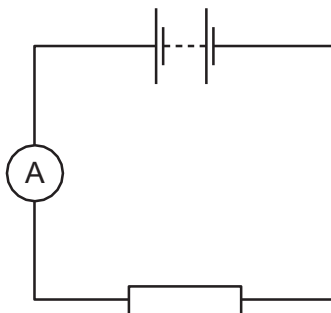

What should be increased to increase the current in the circuit?

- A. the e.m.f. of the battery
- B. the length of the connecting wires
- C. the resistance of the resistor
- D. the temperature of the resistor

Question 9

In which unit is potential difference measured?



- A. ampere
- B. ohm
- C. volt
- D. watt

Question 10

The circuit shown in the diagram contains an unknown component X, hidden in a box.

The voltage-current graph for X is as shown.

variable voltage supply

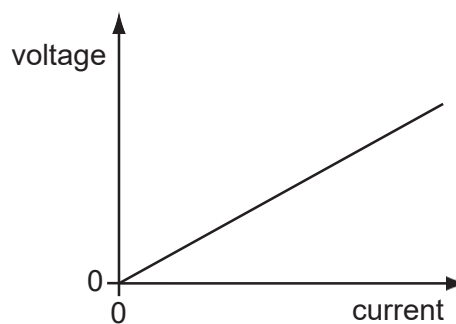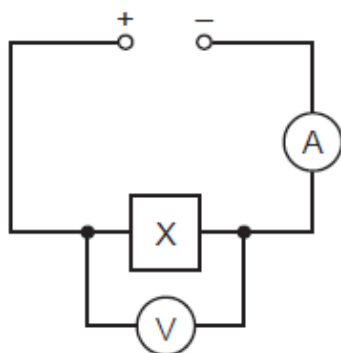


What is the component X?

- A. a capacitor
- B. a closed switch
- C. an open switch
- D. a resistor of constant resistance

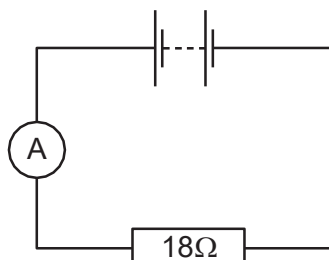Question 11

An ammeter and an $18\ \Omega$ resistor are connected in series with a battery. The reading on the ammeter is $0.50\ \text{A}$. The resistance of the battery and the ammeter can be ignored.



What is the electromotive force (e.m.f.) of the battery?

- A $9.0\ \text{N}$ B $9.0\ \text{V}$ C $36\ \text{N}$ D $36\ \text{V}$

Question 12

Which test could be used to find which end of a magnet is the north pole?

- A. putting it near a compass needle
- B. putting it near a ferrous metal
- C. putting it near a non-ferrous metal
- D. putting it near a steel spoon

Question 13

A polythene rod repels an inflated balloon hanging from a nylon thread.

What charges must the rod and the balloon carry?

- A The rod and the balloon carry opposite charges.
- B The rod and the balloon carry like charges.
- C The rod is charged but the balloon is not.
- D The balloon is charged but the rod is not.


Question 14

Which symbols are used for the units of current and of resistance?

	unit of current	unit of resistance
A	A	W
B	A	Ω
C	C	W
D	C	Ω

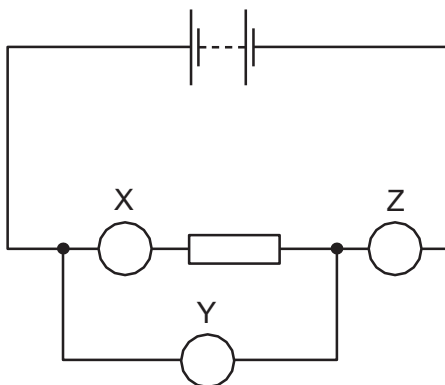Question 15

The diagram shows an electric circuit containing three meters, X, Y and Z, all connected correctly.



What are meters X, Y and Z?

	X	Y	Z
A	ammeter	ammeter	ammeter
B	ammeter	voltmeter	ammeter
C	voltmeter	ammeter	voltmeter
D	voltmeter	voltmeter	voltmeter