

**ADVANCED SUBSIDIARY GCE
ELECTRONICS**

Foundations of Electronics

FRIDAY 16 MAY 2008

2526

Morning

Time: 1 hour 30 minutes

Candidates answer on the question paper

Additional materials (enclosed): None

Additional materials (required):

Calculator



Candidate
Forename

Candidate
Surname

Centre
Number

--	--	--	--	--

Candidate
Number

--	--	--	--

INSTRUCTIONS TO CANDIDATES

- Write your name in capital letters, your Centre Number and Candidate Number in the boxes above.
- Use blue or black ink. Pencil may be used for graphs and diagrams only.
- Read each question carefully and make sure that you know what you have to do before starting your answer.
- Answer **all** the questions.
- Do **not** write in the bar codes.
- Write your answer to each question in the space provided.

INFORMATION FOR CANDIDATES

- The number of marks for each question is given in brackets [] at the end of each question or part question.
- The total number of marks for this paper is **120**.
- You may assume, unless otherwise stated, that:
 - (i) the p.d. across a forward-biased silicon diode is 0.70V,
 - (ii) the power supplies for operational amplifiers are +15V and –15V,
 - (iii) the saturation levels for operational amplifiers are +13V and –13V,
 - (iv) logic 1=5V and logic 0=0V.
- The quality of written communication will be assessed in your answers to all questions.

FOR EXAMINER'S USE

1	
2	
3	
4	
5	
6	
7	
8	
QWC	
TOTAL	

This document consists of **15** printed pages and **1** blank page.

- 1 (a) Complete the truth table for an EXCLUSIVE-OR gate. Use only 1 and 0.

B	A	Q

- (b) The circuit diagram of Fig. 1.1 shows how an EXCLUSIVE-OR gate can be assembled from NOT, AND and OR gates. [3]

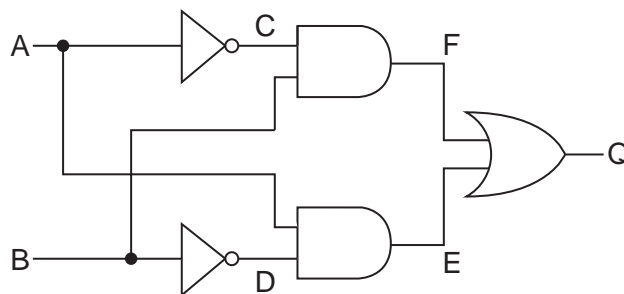


Fig. 1.1

Complete the truth table.

A	B	C	D	E	F	Q
0	0					
1	0					
1	1					
0	1					

- (c) Show how an EXCLUSIVE-OR gate can be assembled from a number of NOR gates. [4]

- 2 The circuit of Fig. 2.1 contains a capacitor in parallel with a resistor.

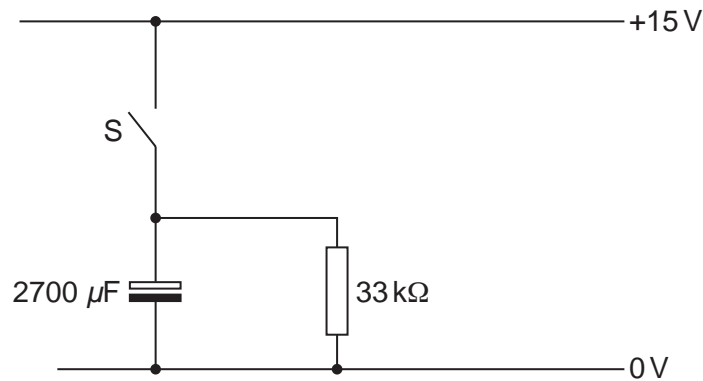


Fig. 2.1

- (a) The switch S is closed.
Explain why the voltage across the resistor suddenly rises to 15V.
-
-
-[2]
- (b) On Fig. 2.1, show how a voltmeter should be connected to measure the voltage across the resistor. [2]
- (c) When the switch is opened, the voltage across the resistor drops slowly to 0V.
- (i) Calculate the time constant of the circuit when the switch is open.

time constant = s [3]

- (ii) Explain why the voltage drops slowly.

.....

.....

.....

.....[3]

- (iii) Calculate the time delay between the opening of the switch and the reading of the voltmeter becoming 2.0V.

time delay = s [2]

3 The circuit of Fig. 3.1 uses an LDR to control an LED.

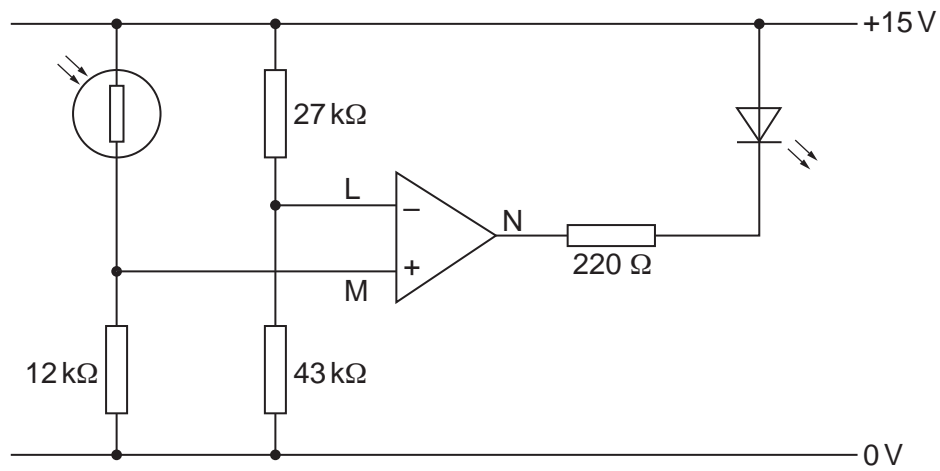


Fig. 3.1

(a) (i) Label the LDR [1]

(ii) Describe the electrical properties of an LDR.

.....

[3]

(iii) Explain why the circuit of Fig. 3.1 needs a resistor in series with the LDR.

.....

[2]

(b) The pair of resistors connected to L keep it a steady voltage.

(i) Calculate the total resistance of these resistors.

resistance = $\text{k}\Omega$ [1]

(ii) Calculate, in μA , the current in the resistors.

current = μA [3]

(iii) Show that the voltage at L is about 9V.

voltage = V [2]

(c) Explain why the LED glows brightly whenever the voltage at M goes below about +9V.

.....

.....

.....

.....

.....

.....

.....[5]

- 4 The circuit of Fig. 4.1 contains a NOR gate bistable.

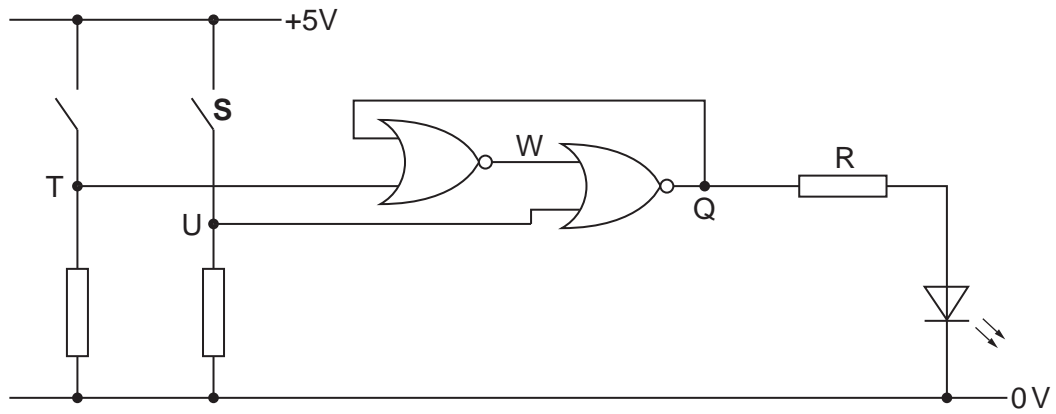


Fig. 4.1

- (a) Complete the truth table for a NOR gate.

W	U	Q
0	0	
0	1	
1	0	
1	1	

[2]

- (b) Explain why the LED stops glowing when the switch **S** is closed.

.....

[3]

- (c) Describe and explain what happens to the LED when the switch **S** is opened again.

.....

[4]

(d) When the LED glows, the voltage across it is 1.8V and it has a power of 5 mW.

(i) Show that the current in the glowing LED is about 3 mA.

[3]

(ii) Calculate the resistance of resistor R.

resistance = Ω [3]

(iii) By describing the electrical properties of an LED, explain why the series resistor is necessary.

.....
.....
.....
.....[3]

- 5 The circuit of Fig. 5.1 produces a steady 5V supply from the a.c. mains supply.

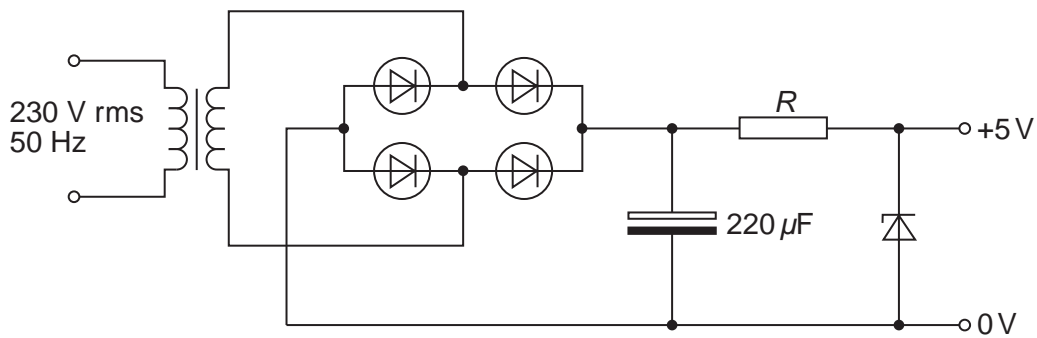


Fig. 5.1

- (a) Complete the block diagram of Fig. 5.2 for the circuit of Fig. 5.1.

Choose words from the list.

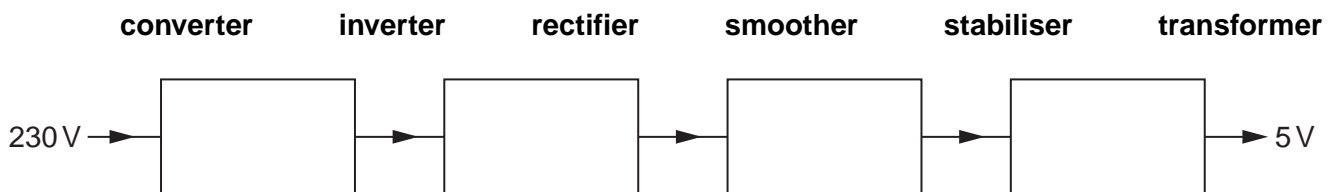


Fig. 5.2

[4]

- (b) The mains supply has a frequency of 50 Hz.

- (i) Explain why this means that the capacitor is charged up at intervals of 10 ms.

.....

[4]

- (ii) Draw on Fig. 5.1 to show how an oscilloscope should be connected to measure the voltage across the capacitor. [2]

- (iii) The voltage across the capacitor has a peak voltage of 9.0V and a ripple of 2.0V.

Draw on Fig. 5.3 to show this voltage on the screen of the oscilloscope.

The timebase is set at 5 ms / division and the vertical amplifier is at 5V / division.

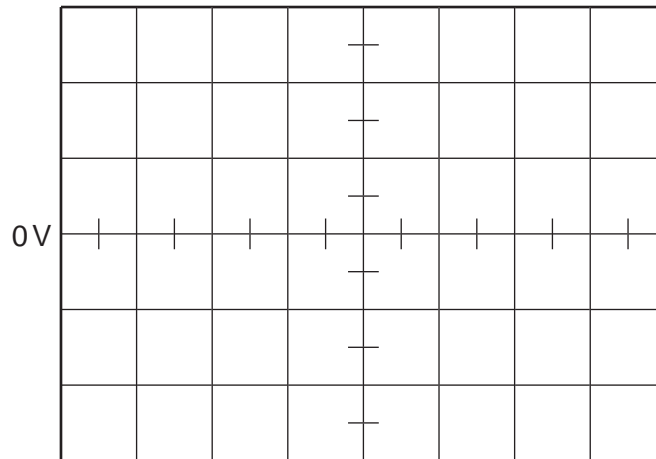


Fig. 5.3

[4]

- (c) The circuit of Fig. 5.1 contains a zener diode.

- (i) Put a ring around the zener diode.

[1]

- (ii) On the axes of Fig. 5.4 draw the current-voltage characteristic of the zener diode.

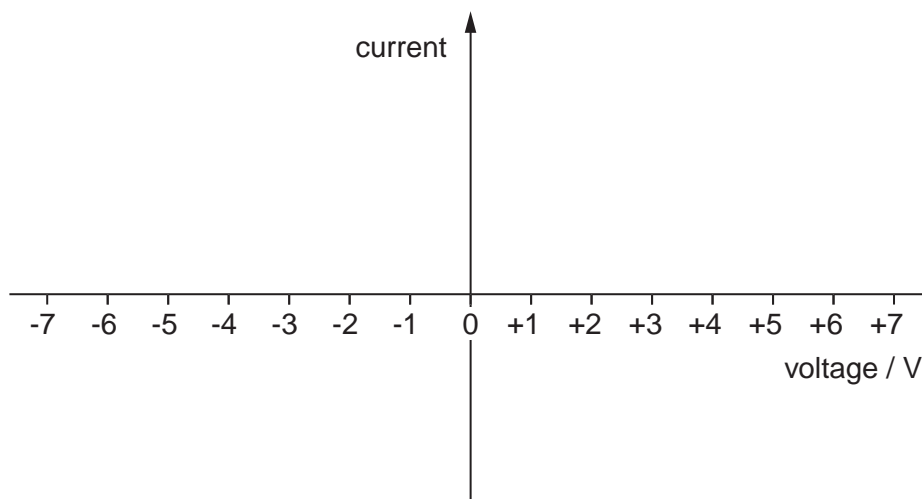


Fig. 5.4

[3]

6 The circuit of Fig. 6.1 is a low-temperature alarm for a refrigerator.

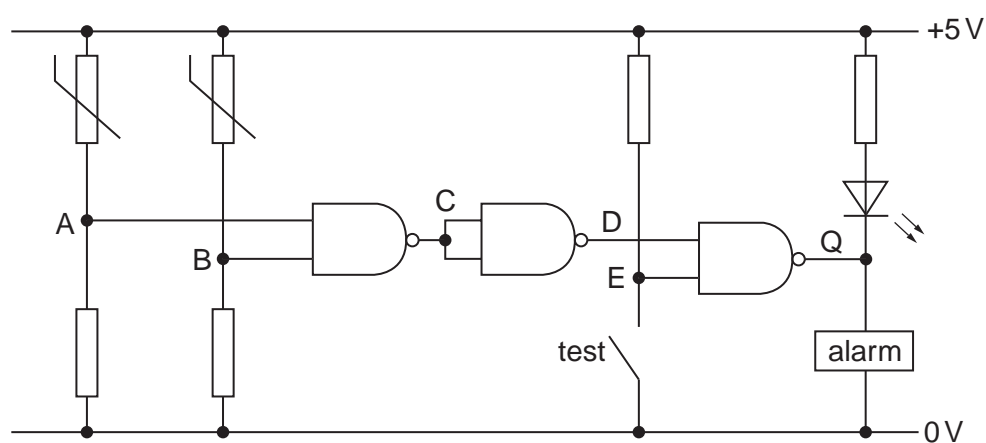


Fig. 6.1

(a) The circuit contains NAND gates.

(i) Describe the behaviour of a NAND gate.

.....

[2]

(ii) Complete the truth table for the circuit of Fig. 6.1.

E	B	A	C	D	Q
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

[5]

- (b) The circuit contains a pair of identical thermistors. The graph of Fig. 6.2 shows how the resistance of a thermistor varies with temperature.

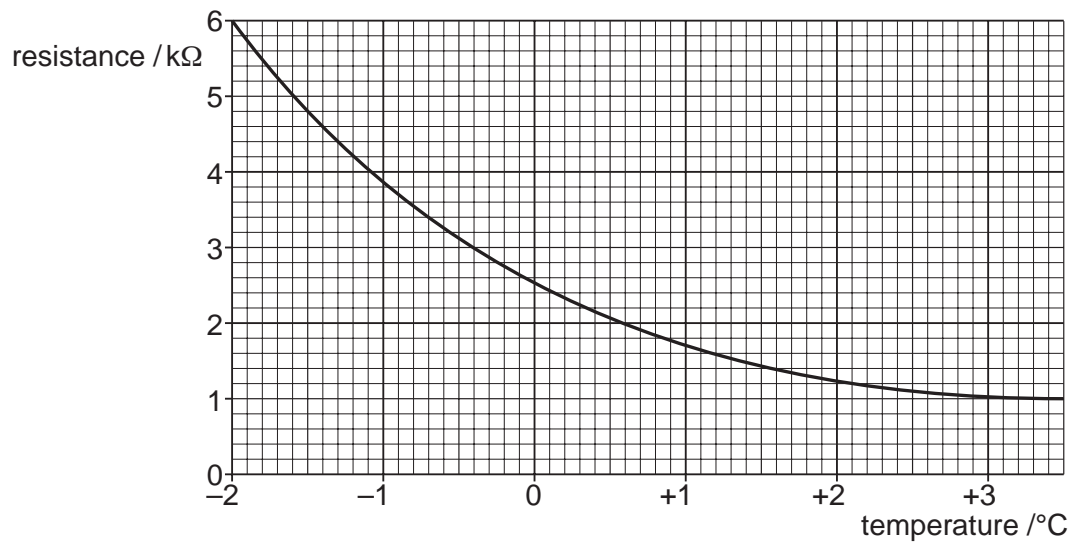


Fig. 6.2

- (i) Explain why the voltage at A **rises** as the temperature of the thermistor rises.

.....

[3]

- (ii) The voltage at A is +2V when the temperature of the thermistor is 0°C.

Calculate the resistance of the resistor in series with the thermistor.

resistance = kΩ [4]

- (c) The circuit of Fig. 6.1 contains a test switch.

Explain what happens when the switch is closed.

.....

[4]

7 The circuit of Fig. 7.1 shows an inverting amplifier.

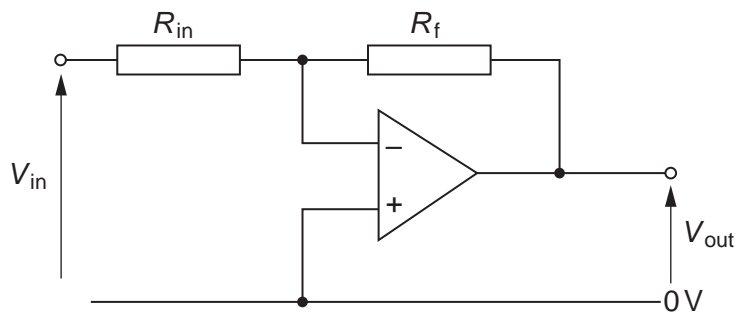


Fig. 7.1

- (a) (i) State the voltage of the inverting input of the op-amp.

Give a reason for your answer.

voltage = V

.....
[2]

- (ii) Here are some expressions for the current I in the resistor R_{in} .

$$I = (V_{in} - 0) \times R_{in} \quad I = \frac{V_{in} - 0}{R_{in}} \quad I = \frac{R_{in}}{V_{in} - 0}$$

Put a ring around the correct expression.

[1]

- (iii) Write down a different expression for the current I in the resistor R_f .

[2]

- (iv) By equating the two expressions for I , show that the voltage gain G of the circuit is given by

$$G = -\frac{R_f}{R_{in}}$$

[2]

- (b) On the graph of Fig. 7.2, sketch the transfer characteristic for the amplifier of Fig. 7.1 when $R_{in} = 4.7\text{ k}\Omega$ and $R_f = 8.2\text{ k}\Omega$.

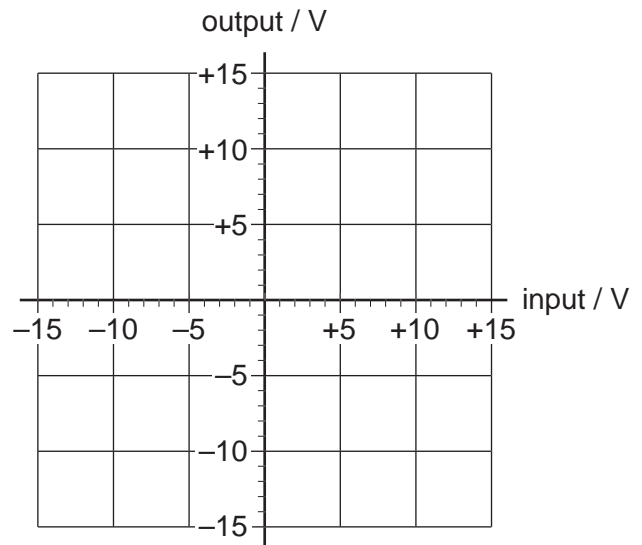


Fig. 7.2

[4]

- (c) (i) On Fig. 7.3, show how an op-amp can be connected so that it has a voltage gain of +1 and an input resistance of $100\text{ k}\Omega$.

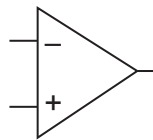


Fig. 7.3

[3]

- (ii) An op-amp with a voltage gain of +1 is sometimes called a power amplifier.

Explain why the circuit of Fig. 7.3 is a power amplifier.

.....

[2]

- 8 The circuit of Fig. 8.1 contains a D-type flip-flop.

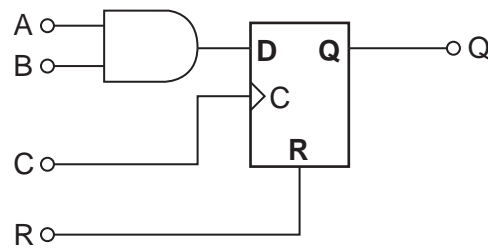


Fig. 8.1

- (a) State the signals required at A and B to make D go high.

.....
[1]

- (b) The timing diagram of Fig. 8.2 shows the signals at the flip-flop inputs R, C and D.

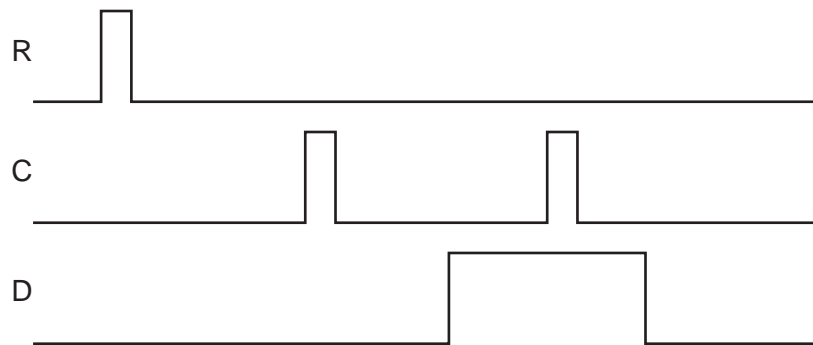


Fig. 8.2

The sentences below describe these signals and their effect on the D-type flip-flop.

A	Q goes low.
B	D starts off low.
C	The signal at A goes low.
D	The signals at A and B both go high.
E	A clock pulse at C leaves Q unchanged.
F	A clock pulse at C changes the state of Q.
G	A short pulse is applied to the reset terminal.

Put letters in the boxes below to show the correct order.

The first one has been done for you.

B						
---	--	--	--	--	--	--

[5]

15
BLANK PAGE

PLEASE DO NOT WRITE ON THIS PAGE

PLEASE DO NOT WRITE ON THIS PAGE

Permission to reproduce items where third-party owned material protected by copyright is included has been sought and cleared where possible. Every reasonable effort has been made by the publisher (OCR) to trace copyright holders, but if any items requiring clearance have unwittingly been included, the publisher will be pleased to make amends at the earliest possible opportunity.

OCR is part of the Cambridge Assessment Group. Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.

© OCR 2008